
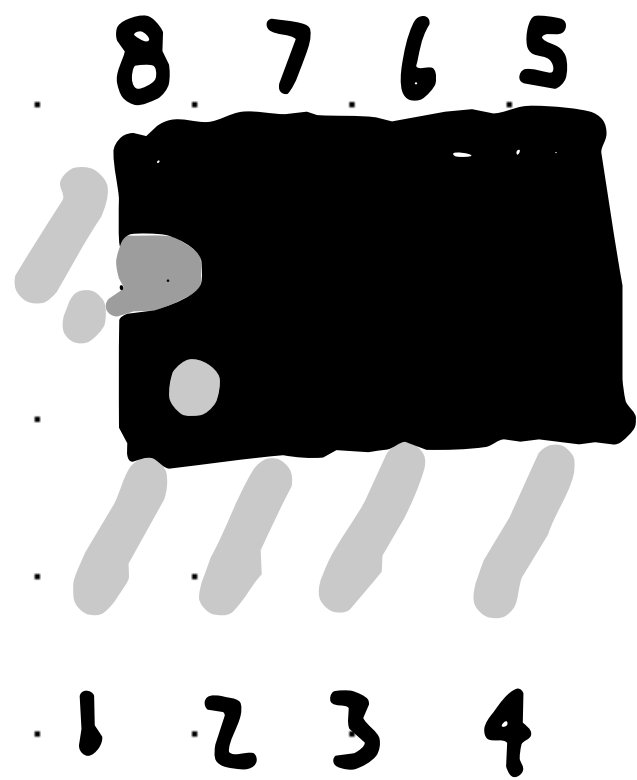


# Operational Amplifiers (OP-Amps)

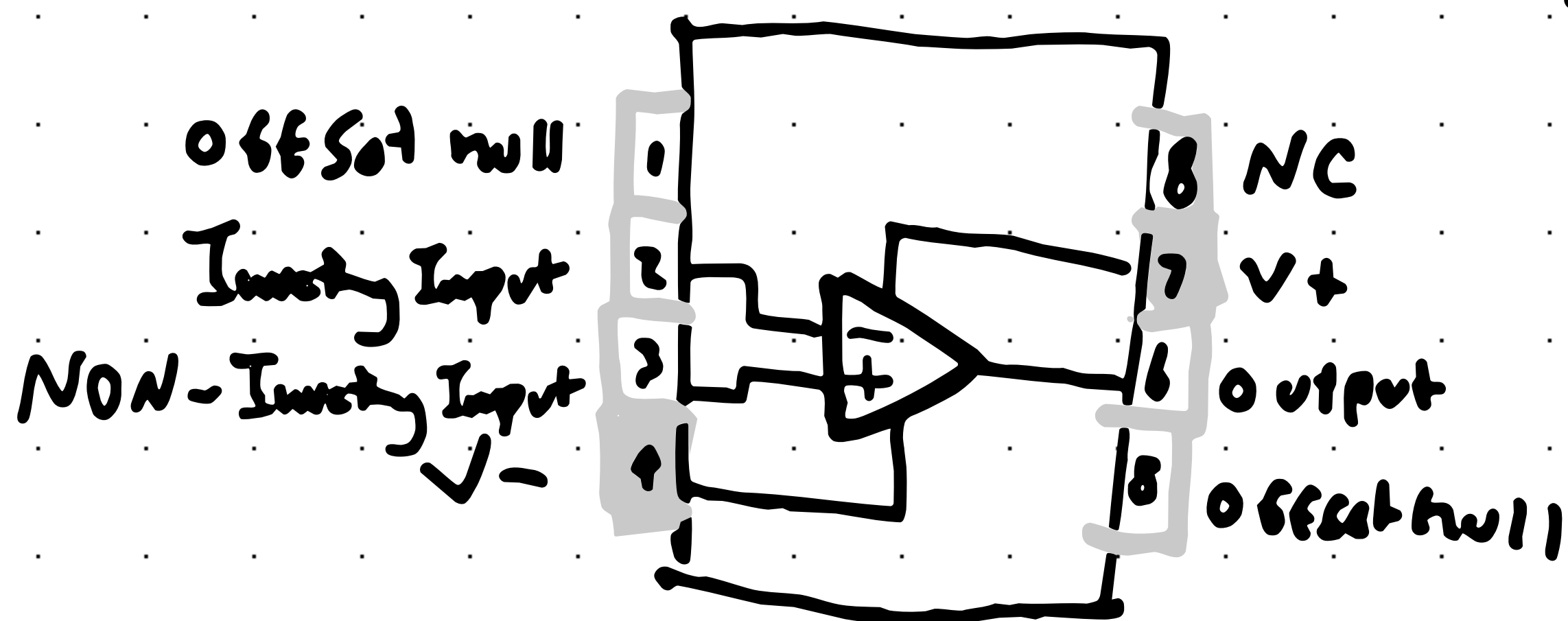


Type 741




741 IC Pinout  
(Integral Circuit)

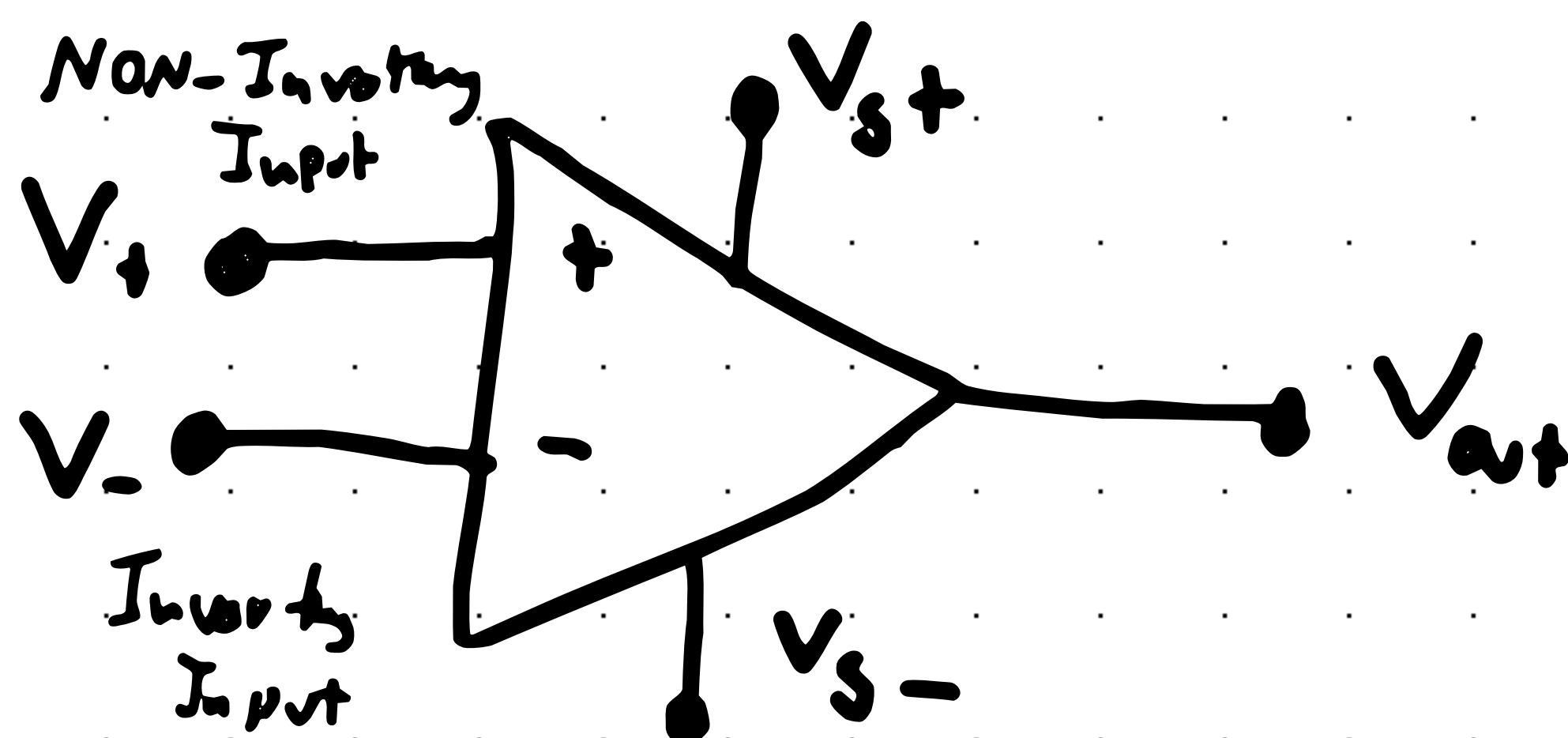- Purpose: Add, Subtract, divide, Multiply, adjust voltage




**NON-Inverting Input:** If I'd like to Amplify a voltage, without changing the polarity, use the Non-Inverting Input.

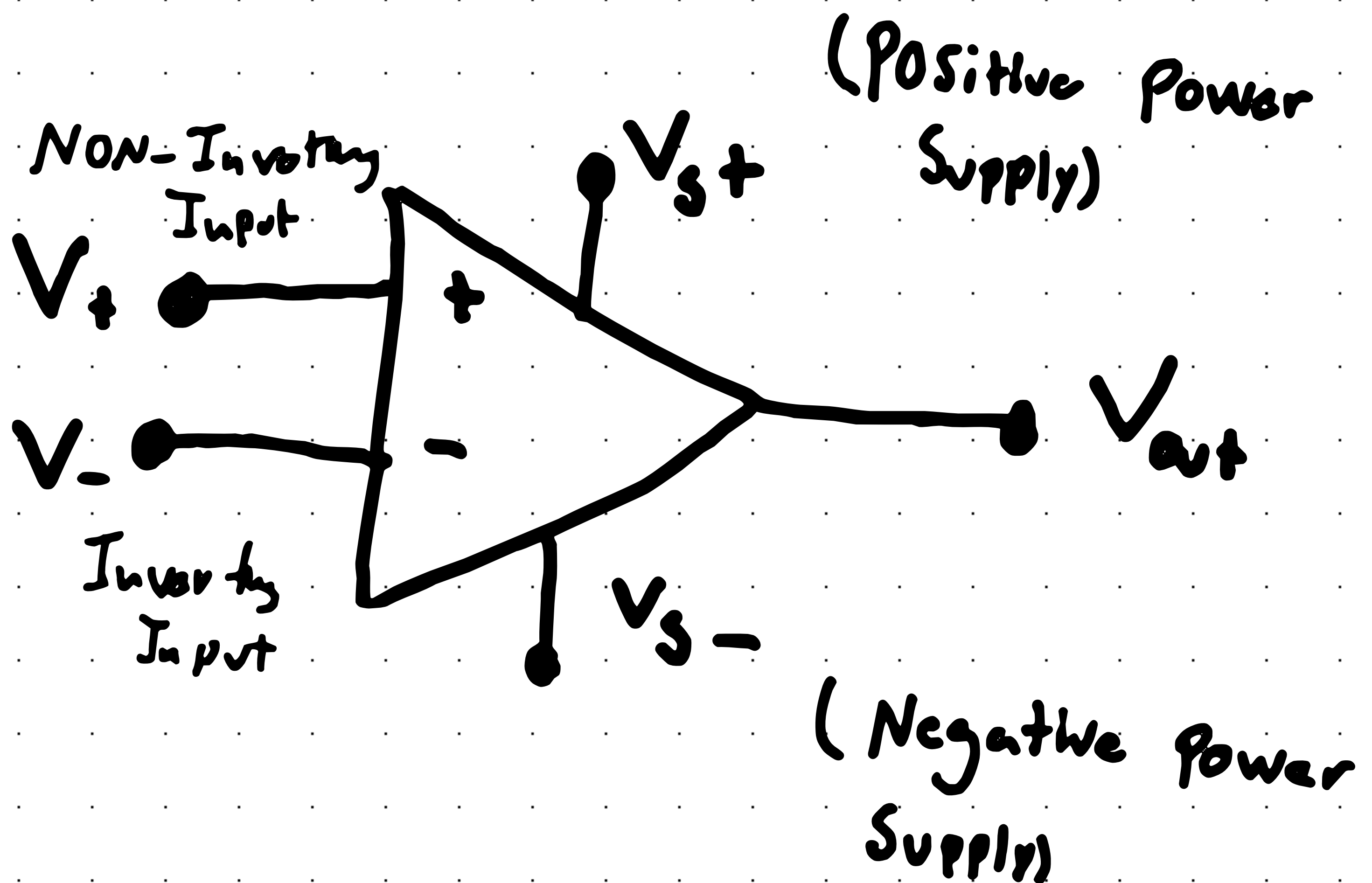**Inverting Input:** If I'd like to Amplify a voltage, AND Change the polarity, use the Inverting Input.



# Terminal Voltages and Currents

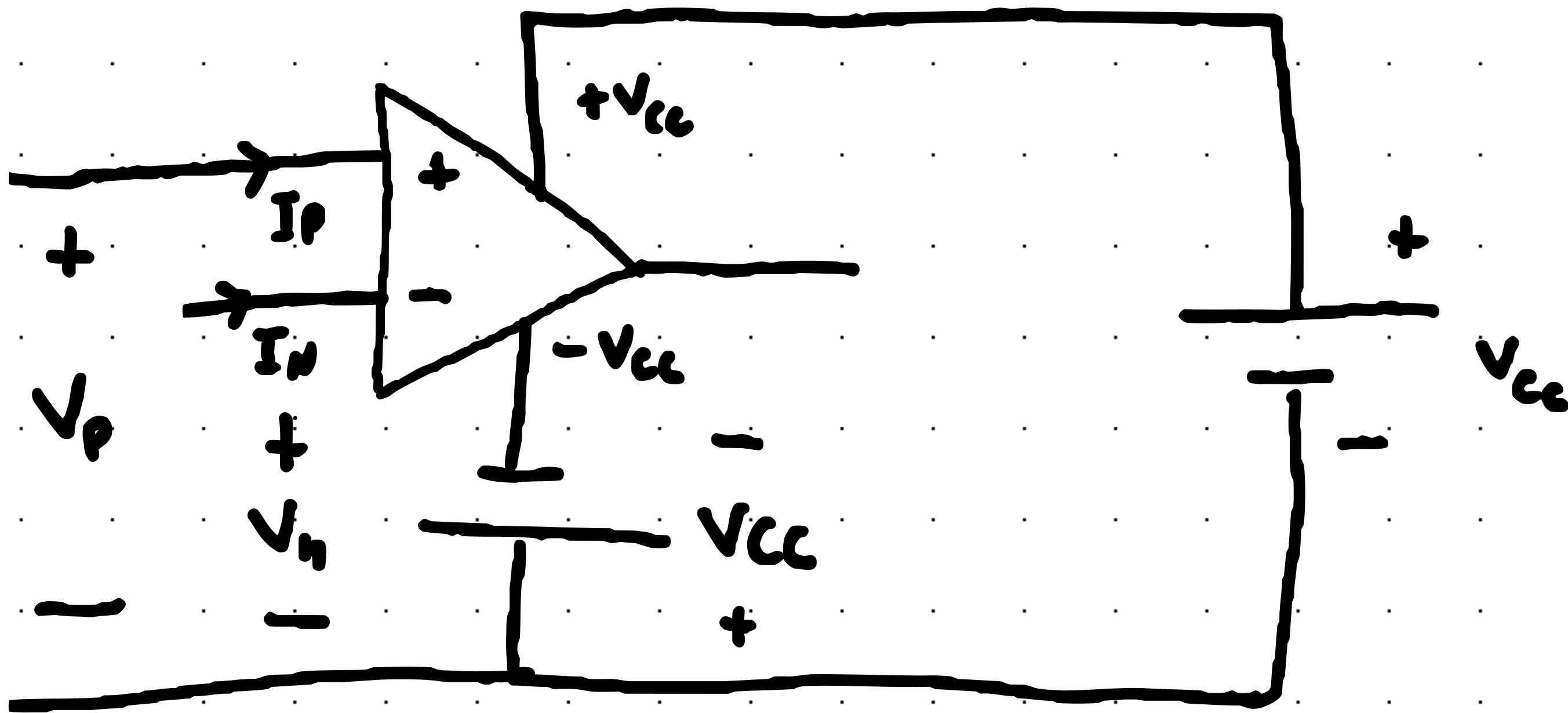

$V_p$ : Positive Voltage

$V_n$ : Negative Voltage

$I_P$ : Positive Current


$I_n$ : Negative Current

# Ideal Op Amp

$$i_p = i_n = 0$$

and

$$V_p = V_n$$

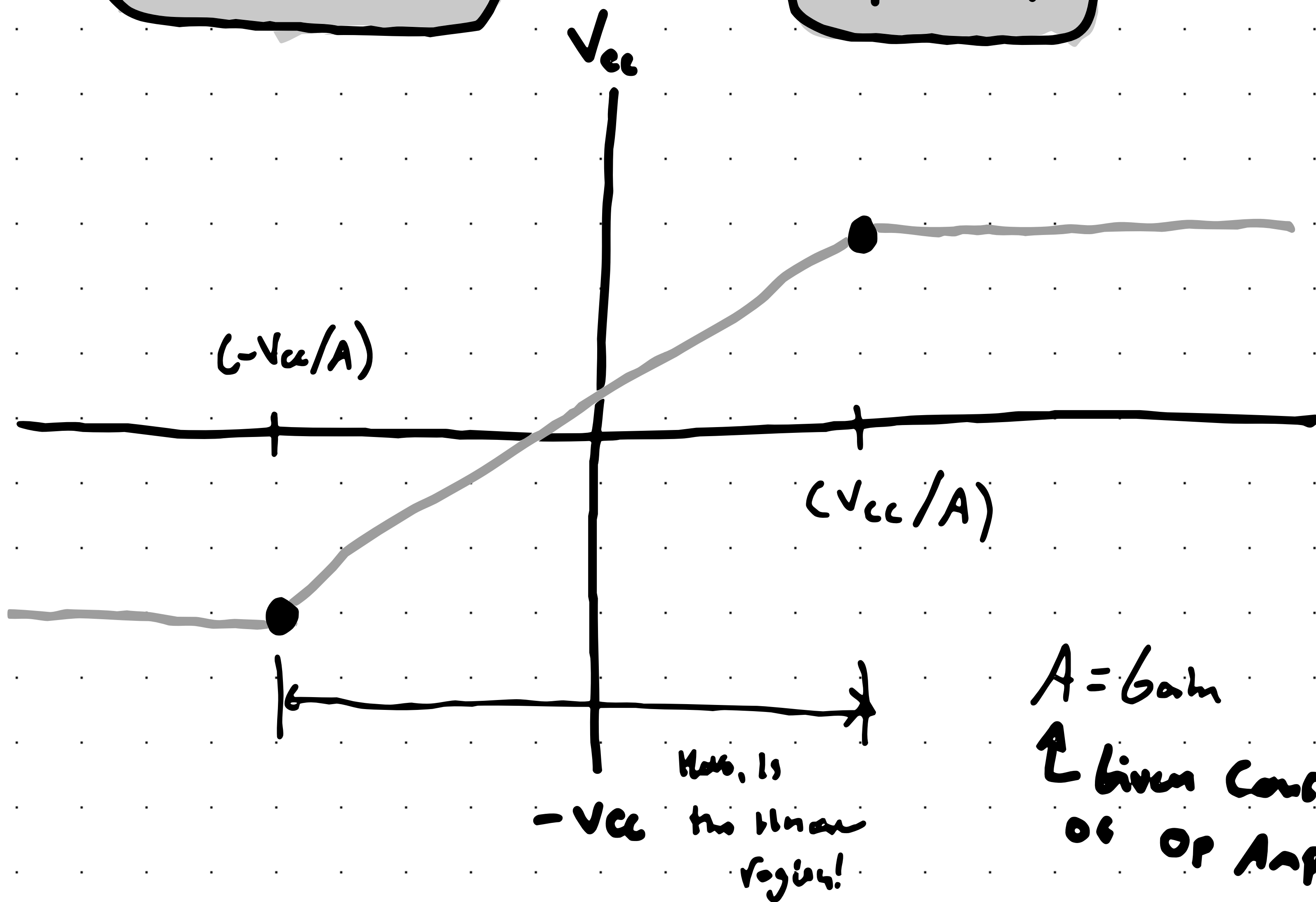

$A = \text{Gain}$

↑ Given Constant of Op Amp


$$V_o = \begin{cases} -V_{cc} & \text{if } V_p - V_n < -V_{cc}/A \\ A(V_p - V_n) & \text{if } -V_{cc}/A \leq V_p - V_n \leq V_{cc}/A \\ +V_{cc} & \text{if } V_p - V_n > V_{cc}/A \end{cases}$$

$$-V_{cc} \leq A(V_p - V_n) \leq V_{cc}$$

Range of Op Amp operation

- If we are not in the range of the linear region, or above or below  $-V_{cc}$  or  $V_{cc}$ , the  $V_o$  just becomes  $-V_{cc}$  or  $+V_{cc}$

Example

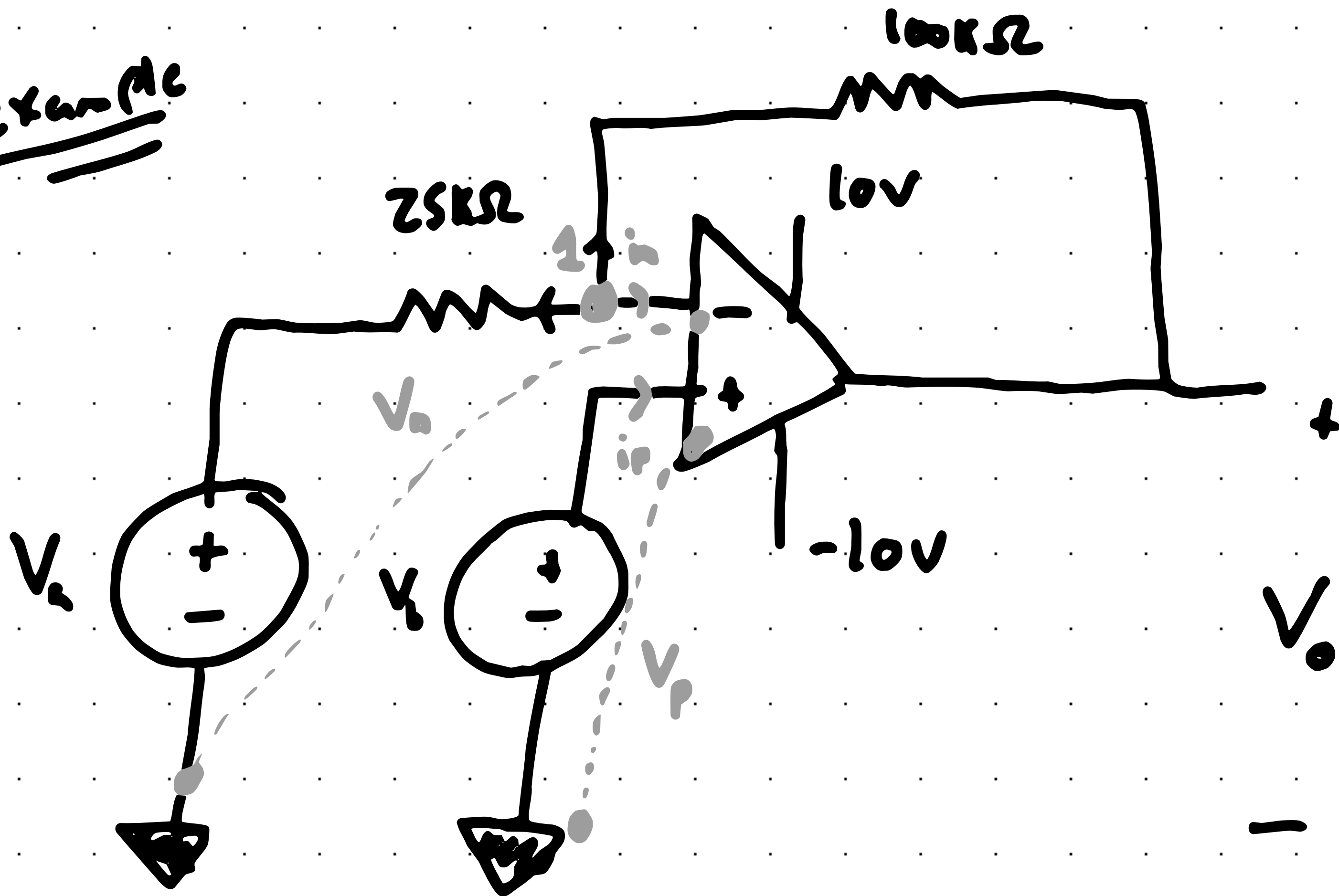

- Calculate  $V_o$  if  $V_a = 1$  and  $V_b = 0$
- Repeat @ for  $V_a = 1V$  and  $V_b = 2V$
- If  $V_a = 1.5V$ , Specify the range of  $V_b$  that avoids amplifier saturation

Solution

$$i_P = i_n = 0, \quad V_P = V_n$$

$$V_P = V_b \rightarrow V_P = V_n = V_b$$

$$\sum_{Node 1} I = 0 \quad \frac{V_n - V_a}{25k} + \frac{V_n - V_o}{100k} + I_N = 0$$

Case a)

$$V_a = 1, \quad V_b = 0 \quad \text{Calculate } V_o$$

$$V_p = V_n = V_b$$

$$\frac{V_n - V_a}{25k} + \frac{V_n - V_o}{100k} \rightarrow \frac{0 - 1}{25,000} + \frac{0 - V_o}{100,000} = 0$$

$$V_o = -4V$$

$$V_o = -4V$$

$$-10 \leq -4 \leq 10$$

In effective range!

Case b

$$V_a = 1 \quad V_b = 2$$

$$\frac{2 - 1}{25,000} + \frac{2 - V_o}{100,000} = 0$$

$$V_o = 6V$$

$$V_o = 6V$$

$$-10V \leq 6V \leq 10V$$

In effective region!

Case C

$$V_R = 1.5V$$

$$V_b = ?$$

Range?

If  $V_o = -10V$

(min)

$$\frac{V_b - 1.5}{25,000} + \frac{V_b - (-10)}{100,000}$$


If  $V_o = 10V$

(max)

$$\frac{V_b - 1.5}{25,000} + \frac{V_b - (10)}{100,000}$$

$$-0.8 \leq V_b \leq 3.2$$

# Inverting Amplifier Circuit

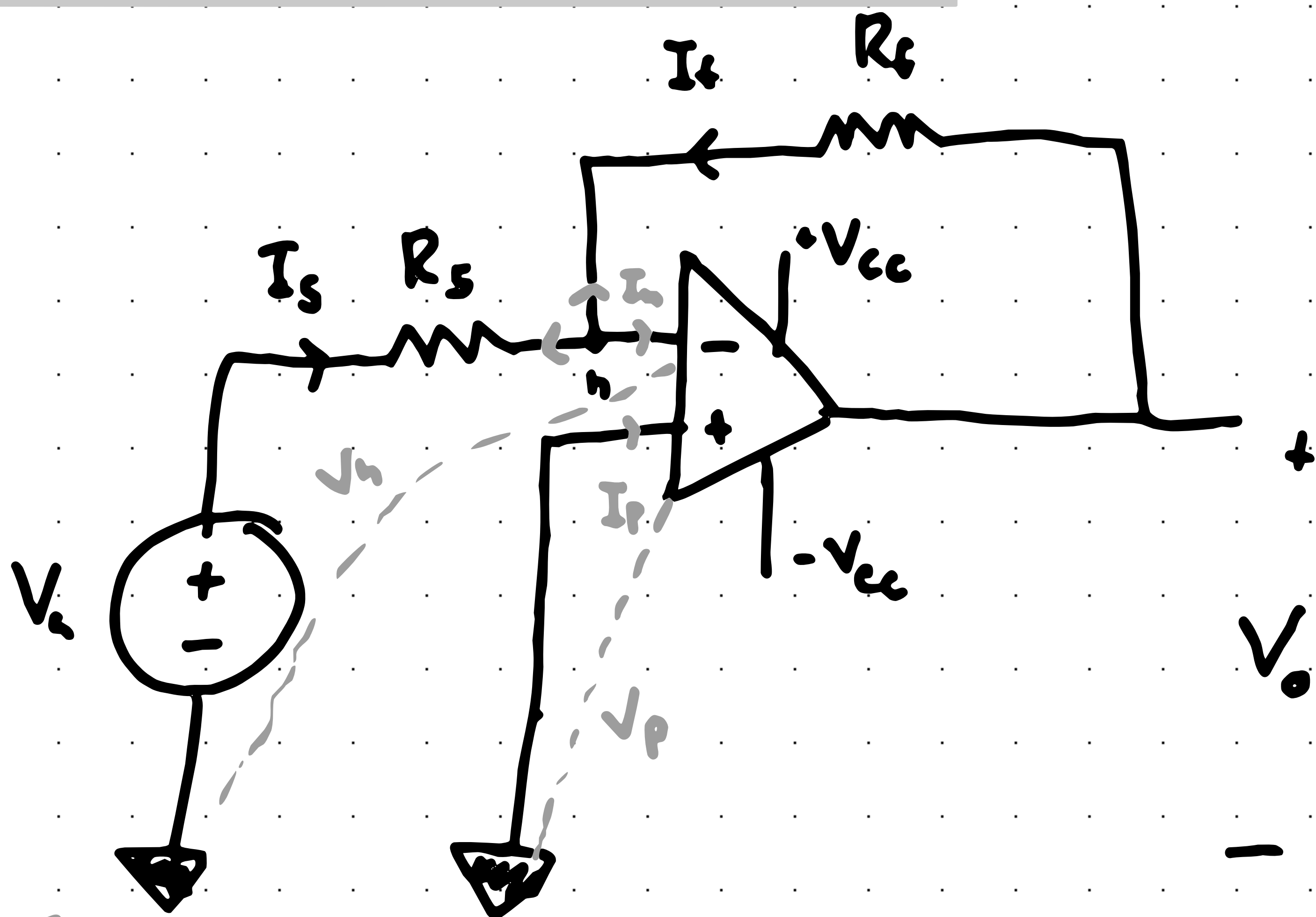

$$I_p = I_n = 0, \quad V_p = V_n$$

Since  $V_p = 0$ , then  $V_h = 0$

$$\sum I = 0 \quad \text{Node } \odot \quad \frac{V_h - V_s}{R_s} + \frac{V_h - V_o}{R_f} + I_p = 0$$

$$\frac{-V_s}{R_s} = \frac{V_o}{R_f}$$

Inverting Amplifier In/out Relation

$$V_o = -\frac{R_f}{R_s} V_s$$

↑                      ↑  
Output                  Input

$$\text{Gain} = \frac{R_f}{R_s}$$