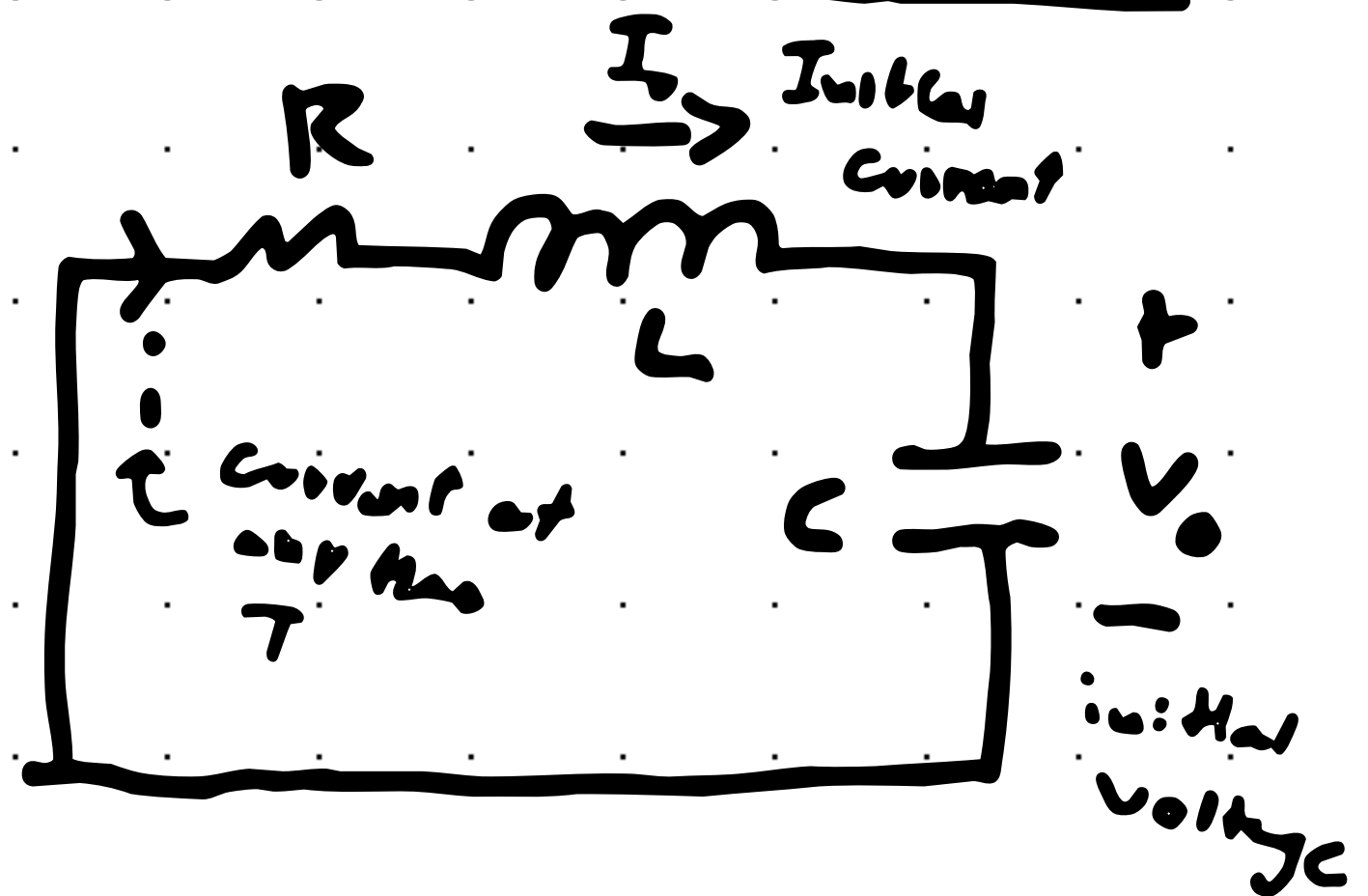


Tutorial 9

The Natural and Step Response of a series RLC

Natural Response, RLC Series



$$\sum_{\text{Loop}} V = 0$$

$$iR + L \frac{di}{dt} + \frac{1}{C} \int i dt = 0$$

$$R \frac{di}{dt} + L \frac{d^2 i}{dt^2} + \frac{1}{C} i = 0$$

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = 0$$

Solve the above eqn by the same way by assuming $i(t) = A e^{st}$

$$s_{1,2} = \frac{-R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

where

$$\alpha = \frac{R}{2L}$$

Series

In Series

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

The same eqn as parallel

There are two different solutions based on α and ω_0

Case ① $\alpha^2 > \omega^2$, Overdamped

$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

Case ② $\alpha^2 < \omega^2$, Underdamped

$$i(t) = \beta_1 e^{-\alpha t} \cos \omega_d t + \beta_2 e^{-\alpha t} \sin \omega_d t$$

Case ③ $\alpha^2 = \omega^2$, Critically damped

$$i(t) = D_1 t e^{-\alpha t} + D_2$$


If it is a step response, there are another set of cases.

$V_c(t)$ is over the Capacitor

$i(t)$ is over everything (as it is in series)

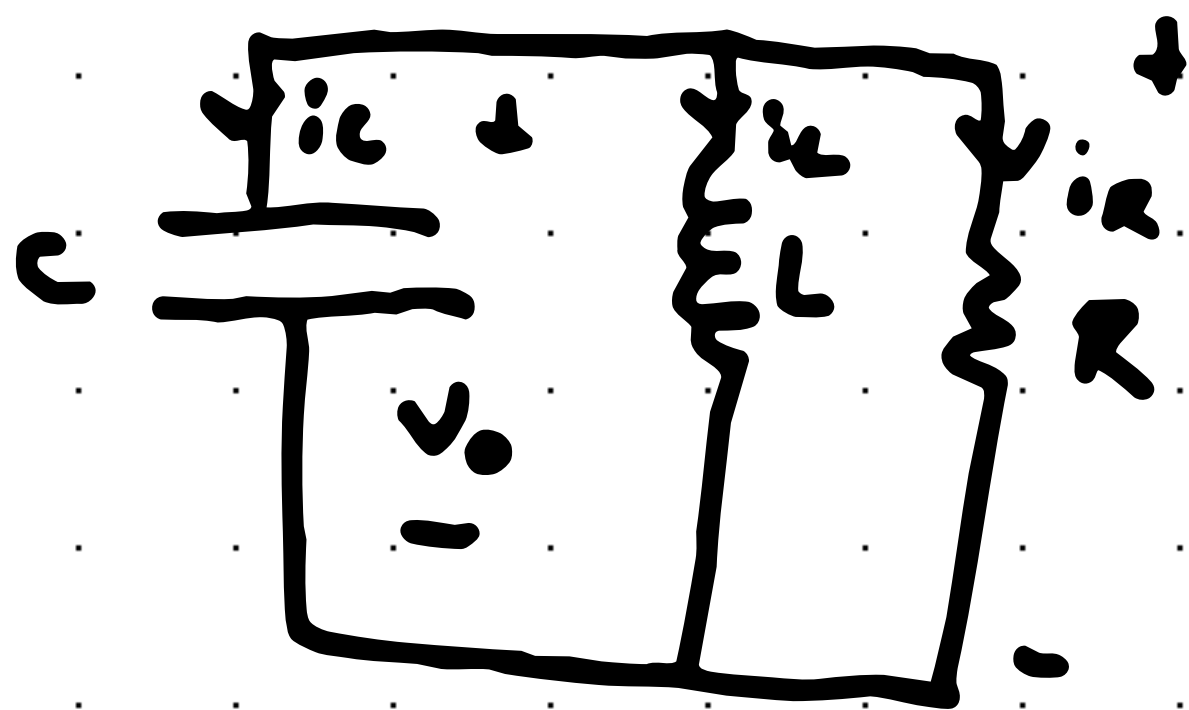Example

Find the roots of the characteristic equation



$$R = 200\Omega, L = 50\text{mH}, C = 0.2\mu\text{F}$$

- b) overdamped, underdamped?
 - c) What value of R causes the response to be critically damped.
-

$$\alpha = \frac{1}{2RC} = \frac{1}{2(200)(0.2 \times 10^{-6})} = 1.25 \times 10^4 \text{ rad/sec}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(50 \times 10^{-3})(0.2 \times 10^{-6})}} = 10^4 \text{ rad/sec}$$

α^2 is greater than ω_0^2

Over damped, two real solutions

Use Case ①

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} = -5000$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} = -20000$$

⑥

Over damped

⑦

For
critically damped

"when $\alpha^2 = \omega_0^2$ "

$$\left(\frac{1}{2RC}\right)^2 = \frac{1}{LC}$$

$$\frac{1}{2RC} = \sqrt{\frac{1}{LC}}$$

$$R = \frac{\sqrt{LC}}{2C} = \frac{\sqrt{L}}{2\sqrt{C}} = \frac{1}{2} \sqrt{\frac{L}{C}}$$


$$= \frac{1}{2} \sqrt{\frac{50 \times 10^{-3}}{0.2 \times 10^{-6}}} = 250 \Omega$$

Example 2

Initial Voltage

$$V_C(0^+) = 12V \quad i_L(t) = 30mA$$

0.2 MF

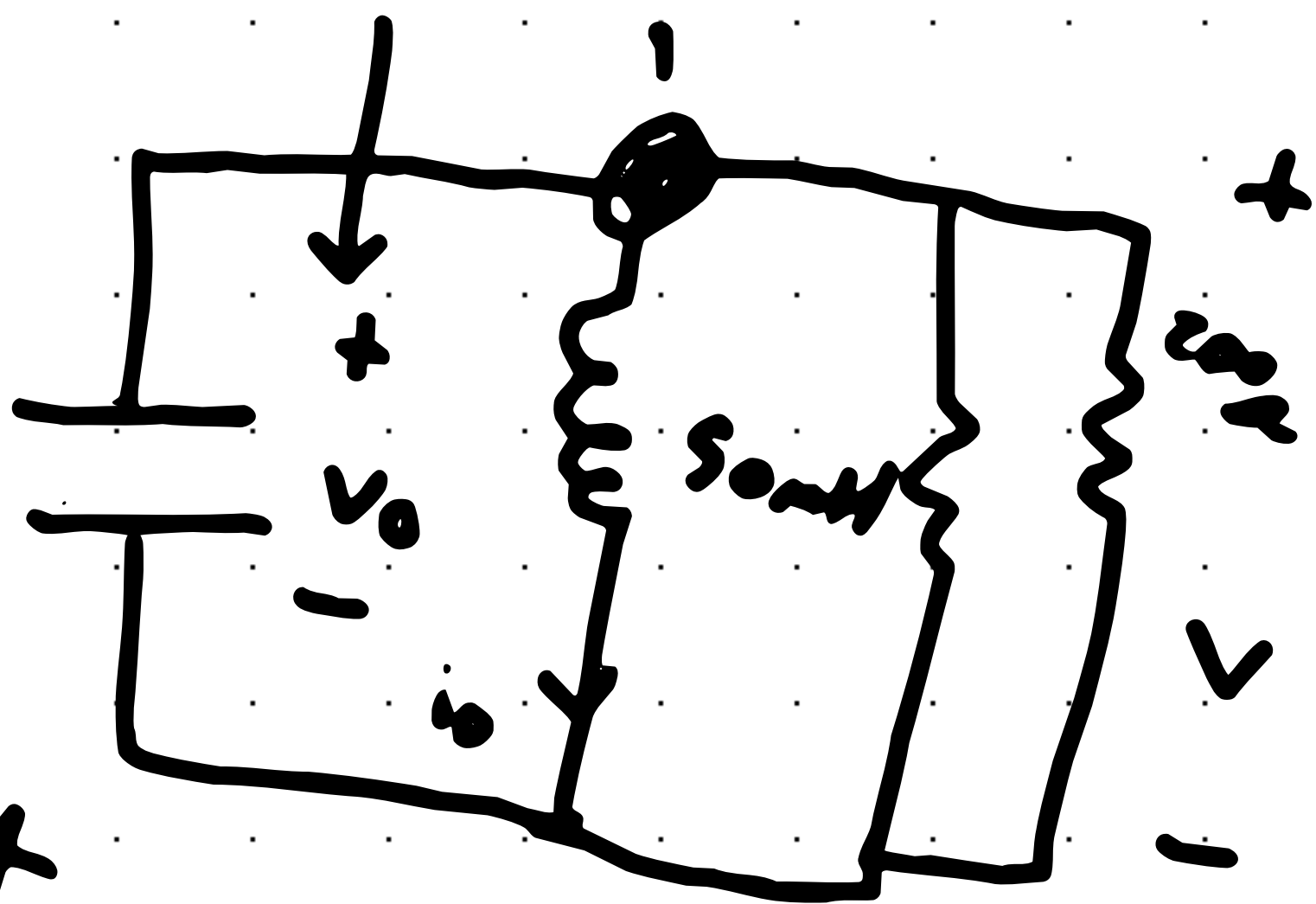

- Calculate the initial current in each branch of the circuit
- Find the initial value of $\frac{dV}{dt}$
- Find the expression for $V_C(t)$
- Derive the expression for i_R, i_L, i_C at any time.

Solution

a) $i_L(0^+) = 30mA$

$$i_R(0^+) = \frac{V_C(0^+)}{R} = \frac{12}{200} = 60mA$$

$$\sum I = 0$$

Nodal

$$I_R + I_L + I_C = 0$$

$$I_C(0^+) = -i_L(0^+) - I_R(0^+) = -90mA$$

$$b) \quad i_c = C \frac{dv}{dt}$$

$$\frac{dv(0^+)}{dt} = \frac{i_c(0^+)}{C} = \frac{-90 \times 10^{-3}}{0.2 \times 10^{-6}} = -450$$

$$c) \quad \alpha = \frac{1}{2RC} = 1.25 \times 10^4 \quad \omega_0 = \frac{1}{\sqrt{LC}} = 1 \times 10^4$$

$$\alpha^2 > \omega_0^2 \quad (\text{overdamped})$$

$$V(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$s_1 = -\alpha + \sqrt{(\alpha)^2 + \omega_0^2} = -5000$$

$$s_2 = -\alpha - \sqrt{(\alpha)^2 + \omega_0^2} = -20000$$

$$V(t) = A_1 e^{-5000t} + A_2 e^{-20000t}$$

missing A_1 and A_2

So, must solve...

For Calculating A_1 and A_2 , use Initial conditions.

$$\begin{cases} V_{(0)} = A_1 + A_2 = 12 \end{cases} \quad \text{Eqn (1)}$$

$$\begin{cases} \frac{dV_{(t)}}{dt} = -450 = -5000A_1 - 20000A_2 \end{cases} \quad \text{Eqn (2)}$$

→ Solve for A_1 and A_2

$$A_1 = -14$$

$$A_2 = 26$$

So,

$$V(t) = -14e^{-5000t} + 26e^{-20000t}$$

d) derive the expression

$$V = IR$$

$$I_R(t) = \frac{V_C(t)}{R} = -70 e^{-5000t} + 130 e^{-20000t} \text{ mA}$$

$$I_C(t) = C \frac{dV}{dt} = 0.2 \times 10^{-6} [-14(-5000) e^{-5000t} + 26(-20,000) e^{-20000t}]$$

$$I_C(t) = 14 e^{-5000t} - 104 e^{-20000t} \text{ mA}$$

$$I_L(t) = -i_C(t) - i_R(t) = 56 e^{-5000t} - 26 e^{-20000t} \text{ mA}$$


Example 3

The initial energy stored in the circuit is zero

At $t=0$ a dc current is applied to the circuit

The value of the resistor is 400Ω

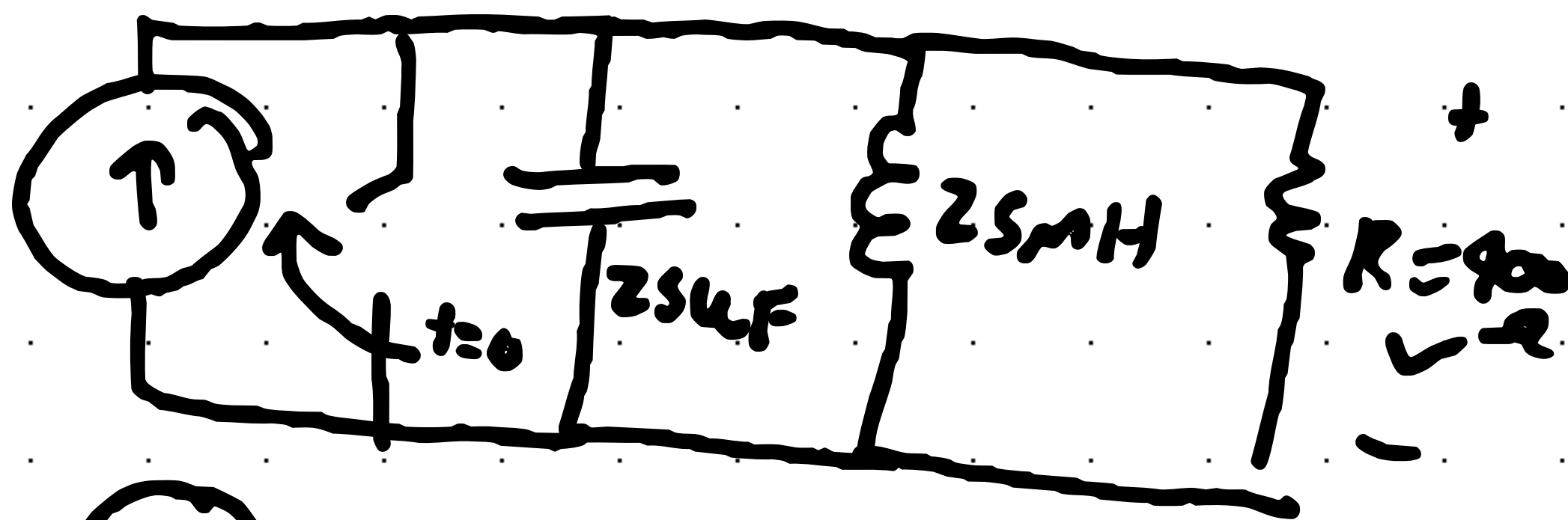- (a) What is the initial value of i_L ?
- (b) What is the initial value of di/dt ?
- (c) What are the roots of the characteristic Eq?
- (d) What is the numerical expression of $i_L(t)$ when $t \geq 0$?



Solution

(a)

Initial energy stored is zero

Capacitor $V_C(0) = 0$

Inductor $I_L(0) = 0$

⑥

$$V_L = L \frac{di}{dt} \rightarrow \frac{di_L(0)}{dt} = \frac{0}{L} = 0$$

⑦

$$\alpha = \frac{1}{2\tau c}, \quad \omega_0 = \frac{1}{\sqrt{Lc}}$$

$$\alpha = 25 \times 10^4$$

$$\omega_0 = 4 \times 10^4$$

$$\alpha^2 > \omega_0^2 \quad (\text{over damped})$$

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} = -20000 \text{ rad/sec}$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} = -80000 \text{ rad/sec}$$

$$i_L(t) = I_f + A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$I_L(t) = 24 + A_1 e^{-20000t} + A_2 e^{-80000t}$$

For finding A_1 and A_2 , use I.C

$$I_L(0) = 0 = A_1 + A_2 + 24 \times 10^3 \quad (1)$$

$$\frac{di_L(t)}{dt} = 0 = 0 + A_1(-20,000) + A_2(-80,000) \quad (2)$$

$$A_1 = -32 \text{ mA}$$

$$A_2 = 8 \text{ mA}$$



$$\underline{I_L(t) = 24 + (-32)e^{-20000t} + 8e^{-80000t} \text{ mA}}$$