

Recall:

$$V(t) = V_m \cos(\omega t + \phi)$$

Max phasor Domain

RMS Phasor Domain

$$V = V_m \angle \phi$$

$$V = \frac{V_m}{\sqrt{2}}$$

↑ Only true for
Sin and Cos waves!
Other RMS waves must
use general RMS

- When representing items in the phasor domain,
all laws even as KVL, KCL, Thev, Nodal,
all still work.

Step one

Transform Sinusoids into phasors

Step Two

Do arithmetic on phasors

Step Three



Remember to transform back!

- When converting to RMS, you should be using Cos. It's not wrong to do that do so, but good practice. Also, all functions must be one or the other. No mixing.

$$\sin(\omega t + 45^\circ) \rightarrow \cos(\omega t + 45^\circ - 90^\circ)$$

In phasor, you
by the angle.

Can tell who is leading

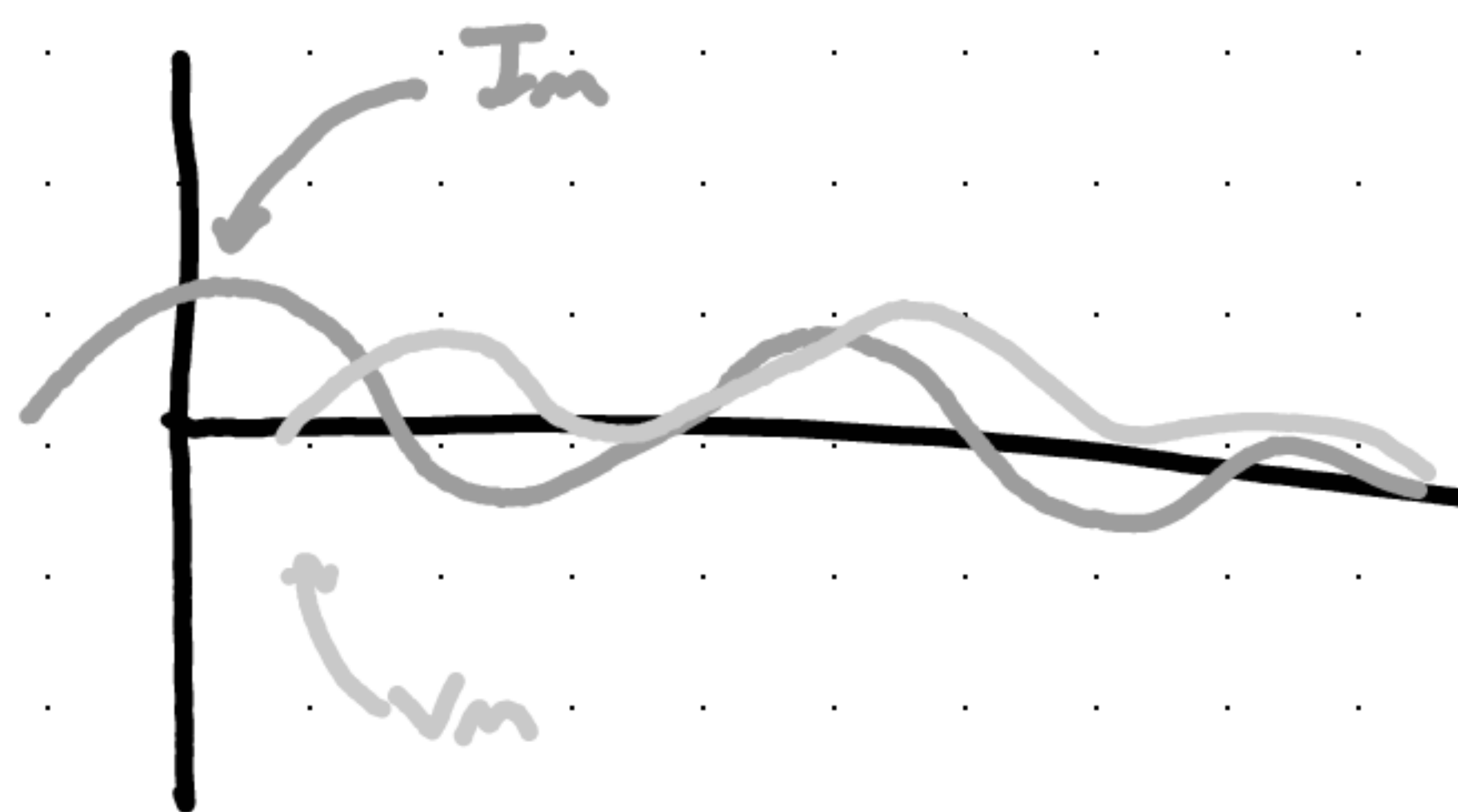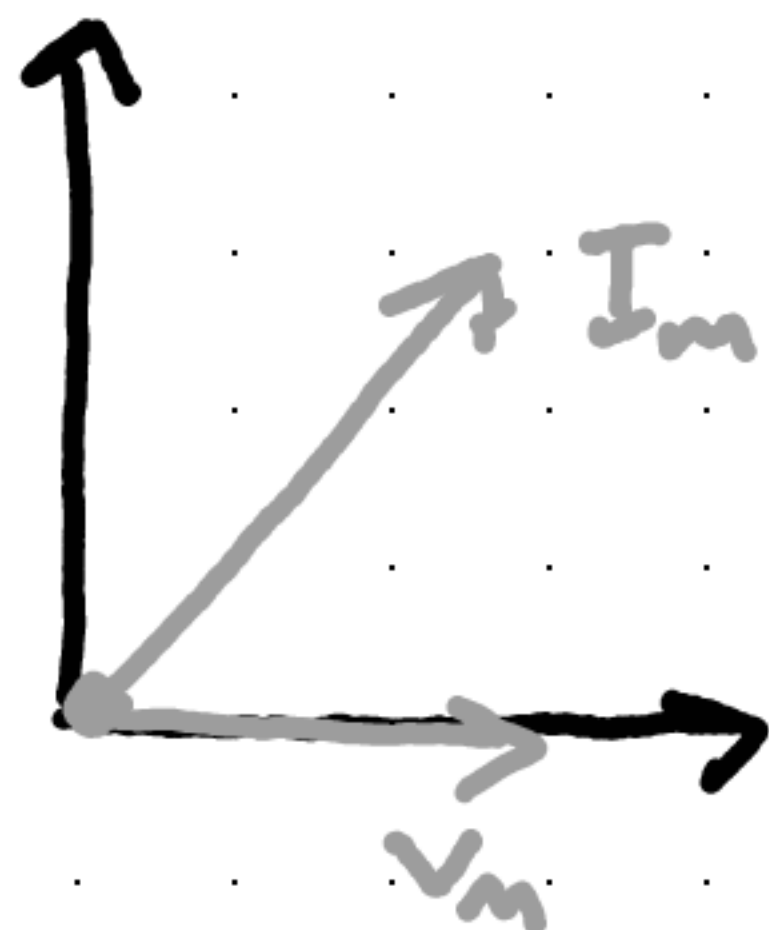


Example

$$i_1 = 20 \cos(\omega t)$$

$$i_2 = 10 \cos(\omega t + 90^\circ)$$

$$i_3 = 30 \cos(\omega t - 90^\circ)$$

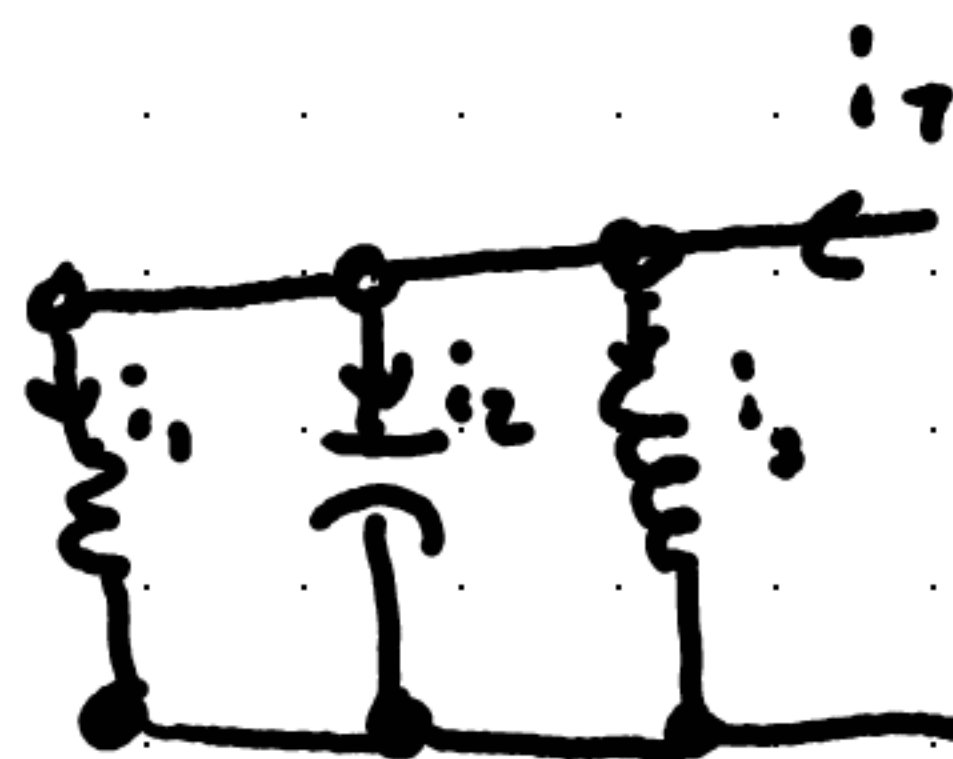

Soln

$$i_1 = \frac{20}{\sqrt{2}}$$

$$i_2 = \frac{10}{\sqrt{2}} \angle 90$$

$$i_3 = \frac{30}{\sqrt{2}} \angle -90$$

RMS values

$$i_1 + i_2 = 5\sqrt{10} \angle 26.565$$

$$5\sqrt{10} \angle 26.565 + i_3$$

$$= 20 \angle -45$$

↓ Convert back to time

$$20\sqrt{2} \angle -45$$

↓ Convert back to time

$$20\sqrt{2} \cos(\omega t - 45)$$

Time Domain to phasor domain element Conversion:

Time

Phasor

Resistor:

$$V_R = IR$$

$$V = IR$$

Inductor:

$$V_L(t) = L \frac{di}{dt}$$

$$V_L = \overset{Z(\text{impedance})}{(j\omega L)} \underset{\text{Current}}{I}$$

Capacitor

$$i_C(t) = C \frac{dv_C}{dt}$$

$$V_C = \left(\frac{1}{j\omega L} \right) I$$

Complex Impedance

$$Z_R = R$$

Resistance

(Real)

$$Z_L = j\omega L$$



Reactance

(Complex)

$$Z_C = \frac{1}{j\omega L}$$

Reactance

(Complex)

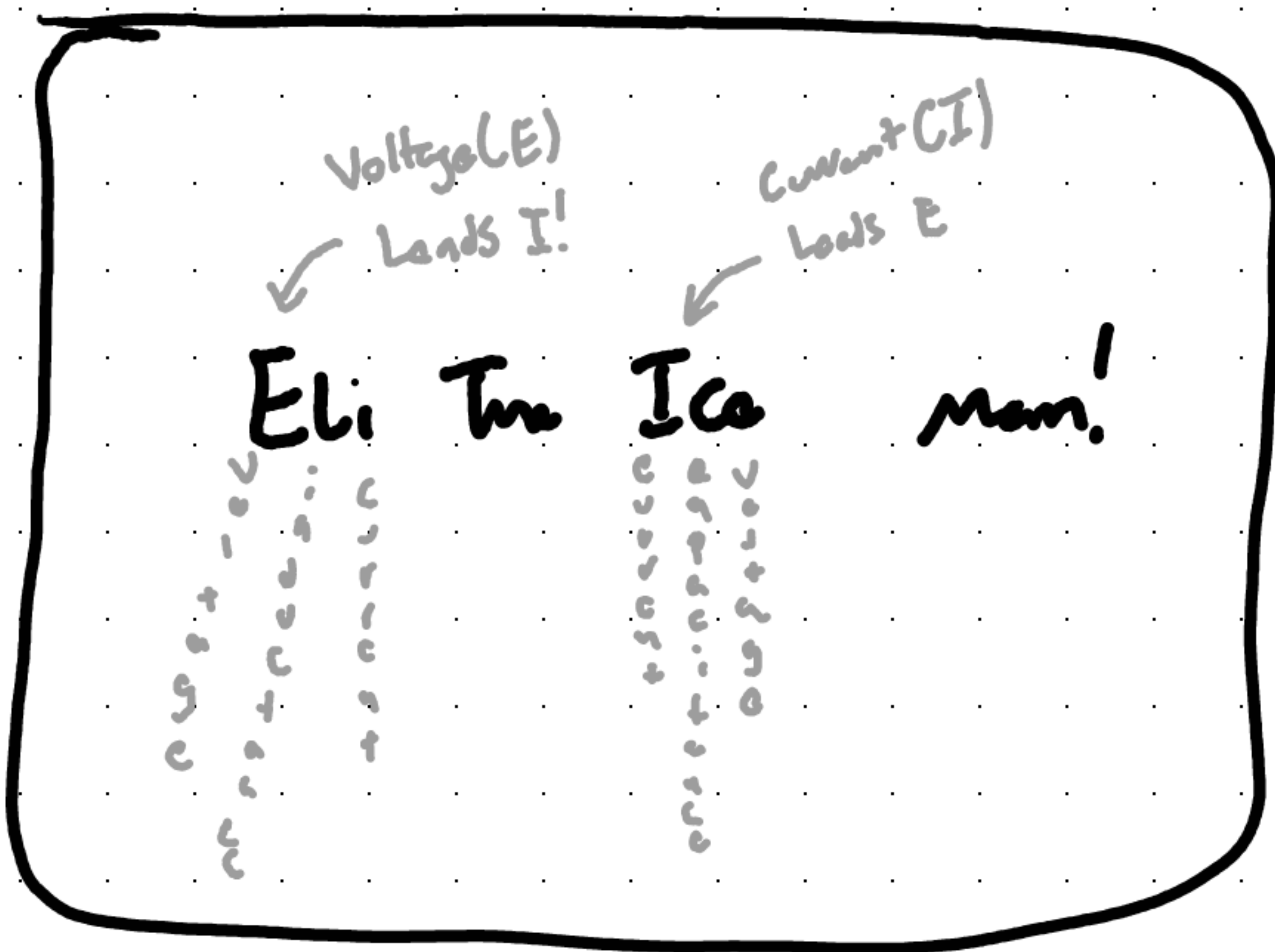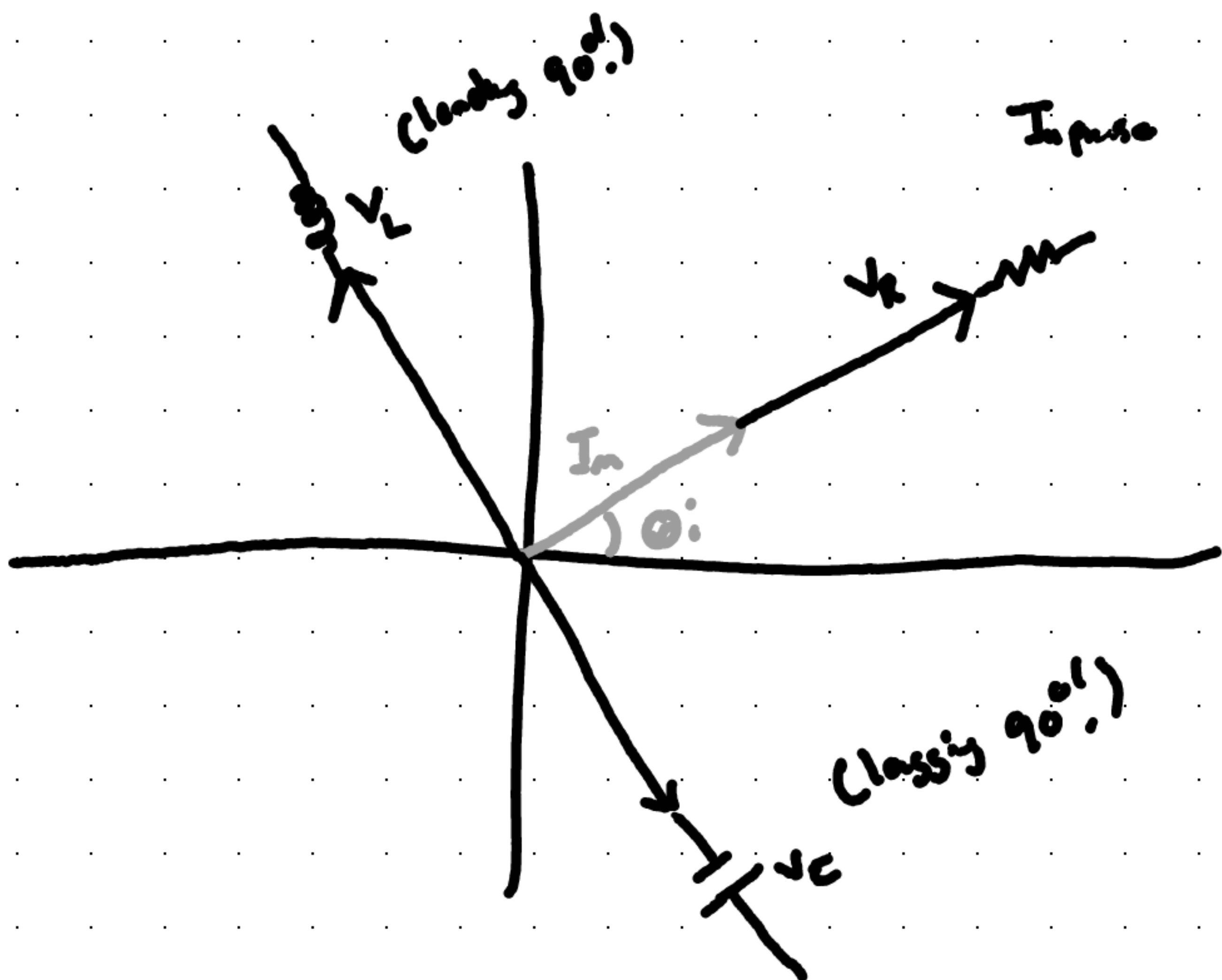

⚡ Voltage
can be
written as
E sometimes

Now, when $f=0$ ($\omega=2\pi f$), obviously we are working in DC conditions.

- Resistors aren't affected by this, so that's why we use them in DC.
- However, Inductors and Capacitors VERY MUCH are! $V_L = (j\omega L)I$. When $f=0$, you have no V_L .
 \downarrow
 $2\pi f$
- This is why these elements appear as Zero in DC!
- On the contrary, as you increase the frequency, the voltage changes proportionally!