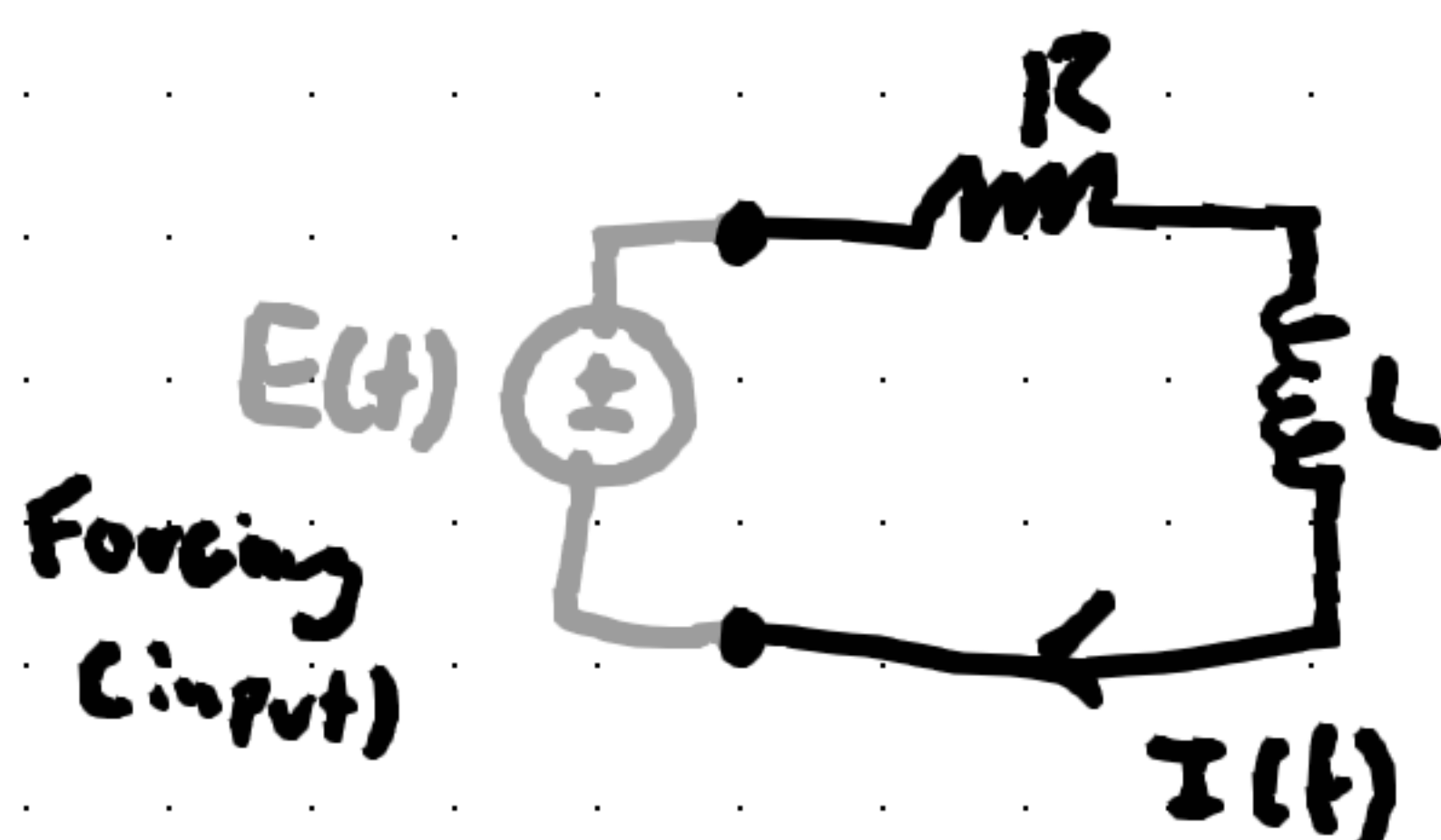


## First order LTI Systems

Consider a Series RL Circuit with a voltage supply  $E(t)$ :



• These  $R$ 's and  $L$ 's  
in differential Equations  
are our parameters

Response (output)

In DE, we take a system,  
and drive them with an input.  
We then get a corresponding  
output.

From KVL, we have the model

$$\underbrace{L \frac{dI}{dt} + RI}_{\text{LTI "System"}} = \underbrace{E(t)}_{\text{Forcing}}$$

L<sub>inear</sub>

model only involves linear terms in  $I$

$$I, \frac{dI}{dt}, \frac{d^2 I}{dt^2}$$

Time-Invariant "constant coefficient"

Parameters are static in time

No matter if  $I$  power in circuit  
at 8am, or 8pm, it will  
be the same.

Assume DC Voltage Source

$$E(t) = E_0$$

and initial conditions

$$I(0) = I_0$$

$$\dot{I} = \frac{dI}{dt}$$

$$L\dot{I} + RI = E_0, \quad I(0) = I_0$$


# State Space

The state of the system at time  $t$  is given by  $(I(t), \dot{I}(t))$

If we re-arrange our DE,

$$\dot{I}(t) = \frac{E_0}{L} - \frac{R}{L} I(t)$$

## State Space Diagram

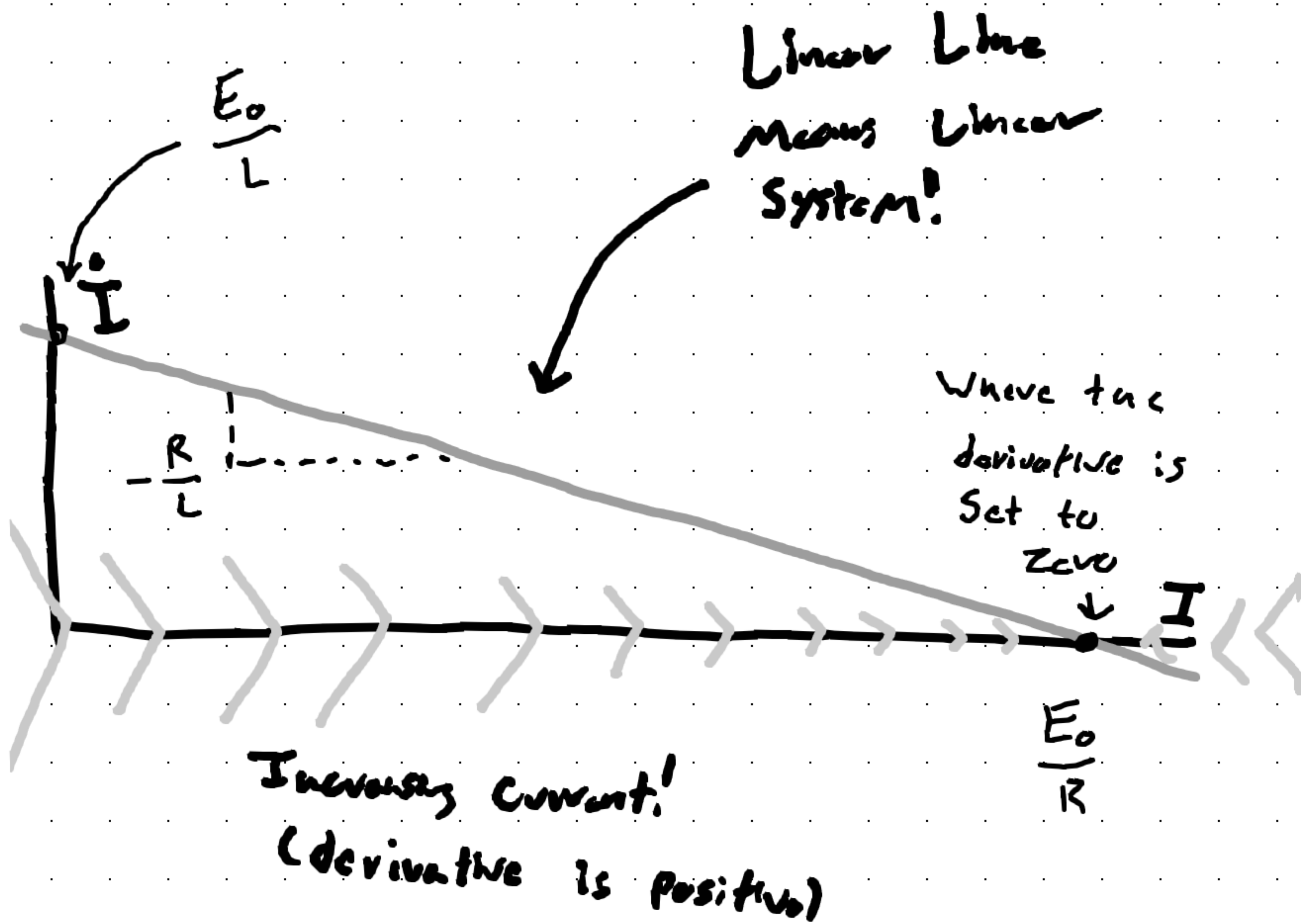


$I = \frac{E}{R}$  is a Stable Fixed point of the system.

↑  
The zero point on the graph

(i) Fixed point  $\dot{I} = 0 \rightarrow$  No change in  $I$ .  
 $\rightarrow$  System in Steady State

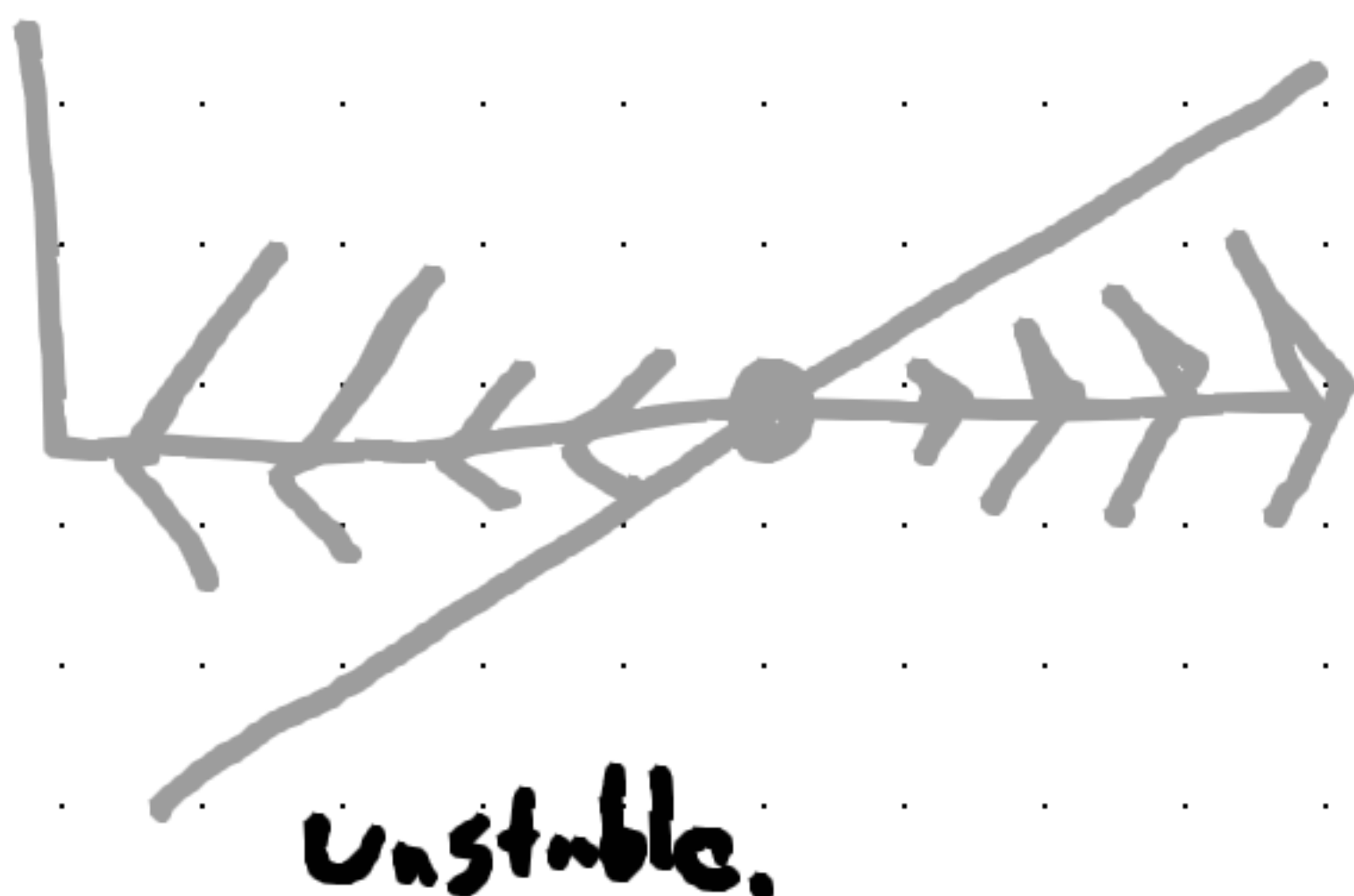(ii) Stable: The System is attracted to this fixed point

$\hookrightarrow$  This System can be unstable  
This means it is repelled from the point.



Money is unstable can increase!

---

Now, let's Solve this dE!

we are searching for some current that makes

$$L\dot{I} + RI = E_0$$

True!

(This is hard!)

Method of undetermined coefficients (MUC)

$$L\dot{I} + RI = E_0, \quad I(0) = I_0$$

1. Get homogeneous solution  $I_h$  (natural response)

$$L\dot{I}_h + RI_h = 0$$

↑ Zero forcing.

(What happens if we do nothing to the system?)

Exponentials are really good for first order LTI Systems!

They grow and decay exponentially!

Assume  $I_h = C e^{\lambda t}$

$\uparrow$  Free Coefficient

differentiating

$$\dot{I}_h = \lambda C e^{\lambda t}$$

$\nwarrow$  Eigenvalue  
 $\underbrace{\hspace{1.5cm}}$  Eigenfunction

We got the same thing! This is why this works!

Any multiple of the Eigenfunction is the same!



Plugging back in...

$$L(\lambda C e^{\lambda t}) + R(C e^{\lambda t}) = 0$$

$$C e^{\lambda t} (L\lambda + R) = 0$$

This is  
the

Characteristic  
Equation

$$\rightarrow L\lambda + R = 0$$

$$\lambda = -\frac{R}{L}$$

~~~~~ Stable

$$I_h = C e^{-\frac{R}{L} t}$$

↑ rate [S<sup>-1</sup>]

This is a decaying  
Exponential

This because time is linear!  
You cannot have time in an  
exponential.

Is also

↖ equal to

$$I_h = C e^{-t/\tau}$$

↑ PTC ↓

# Process Time Constant

$$\tau = \frac{L}{R}$$

$\uparrow$   
[S]

\* This characterizes the speed of the system's response.

$$L \dot{I} + RI = E_0$$

$$\tau \dot{I} + I = \frac{E_0}{R}$$

[S] [A/s] [A]      [A]

## 2. Get Particular Solution

$$L\dot{I}_p + RI_p = E_0$$

(This is kind of the same, but without the  $+C$  from the homogeneous)

Linear systems mimic their forcings.

Have we made...

Constant forcing  $E_0 \Rightarrow$  Constant Response  $I_p = D$

↑  
Undetermined Coefficient.

So now we have...

$$L(0) + RD = E_0$$

$$D = \frac{E_0}{R}$$

$$I_p = \frac{E_0}{R}$$

... Hey... This looks like our fixed point on the graph...

### 3. Satisfy Initial Condition

$$I(0) = I_0$$

$$L\dot{I} + RI = E$$

$$L(\dot{I}_p + \dot{I}_h) + R(I_p + I_h) = \underline{E_0} + 0$$

- A mix of the particular, and homogeneous system!

$$I = I_h + I_p$$

$$I(t) = Ce^{-\frac{R}{L}t} + \frac{E_0}{R}$$

$$\underset{I_0}{I(0)} = \underset{1}{C}e^{-\frac{R}{L}(0)} + \frac{E_0}{R}$$


$$C = I_0 - \frac{E_0}{R}$$

$$I(t) = \left(I_0 - \frac{E_0}{R}\right)e^{-\frac{R}{L}t} + \frac{E_0}{R}$$

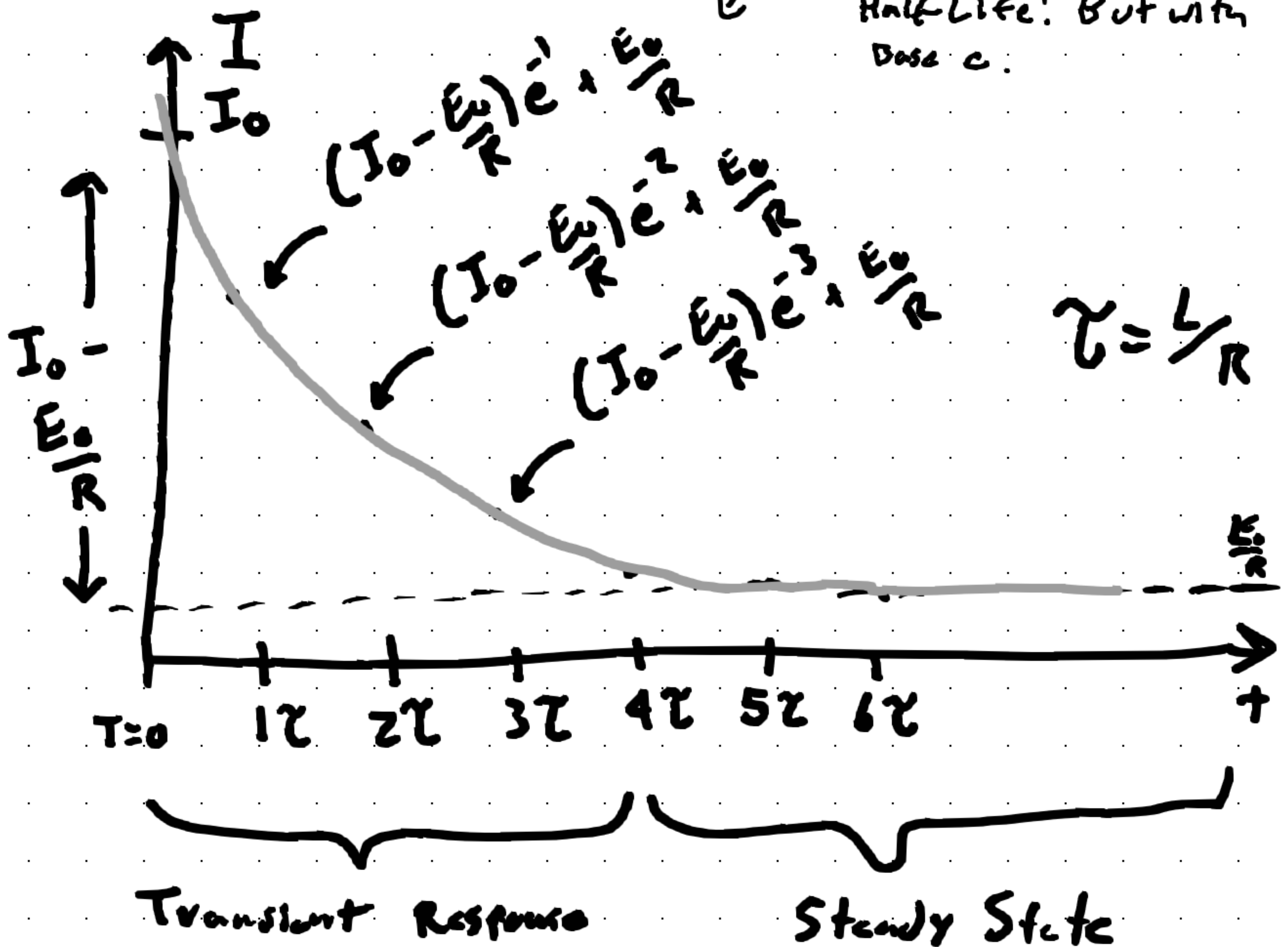4. Sketch  $I(t)$   $I(t) = (I_0 - \frac{E_0}{R})e^{-\frac{R}{L}t} + \frac{E_0}{R}$

$T \geq 3\tau$ ,  $I(t) = I_p$ , response in Steady State.

This is known as e-folding.  
Very similar to Half-Life! But with Dose  $c$ .




This is really just a decaying exponential!  
Shifted up.

$$I(t) = \underbrace{\left(I_0 - \frac{E_0}{R}\right)e^{-\frac{R}{L}t}}_{\text{Transient Response}} + \underbrace{\frac{E_0}{R}}_{\text{Steady Response}}$$

Past about  $3\tau$ , the system has  
no memory of its initial state.
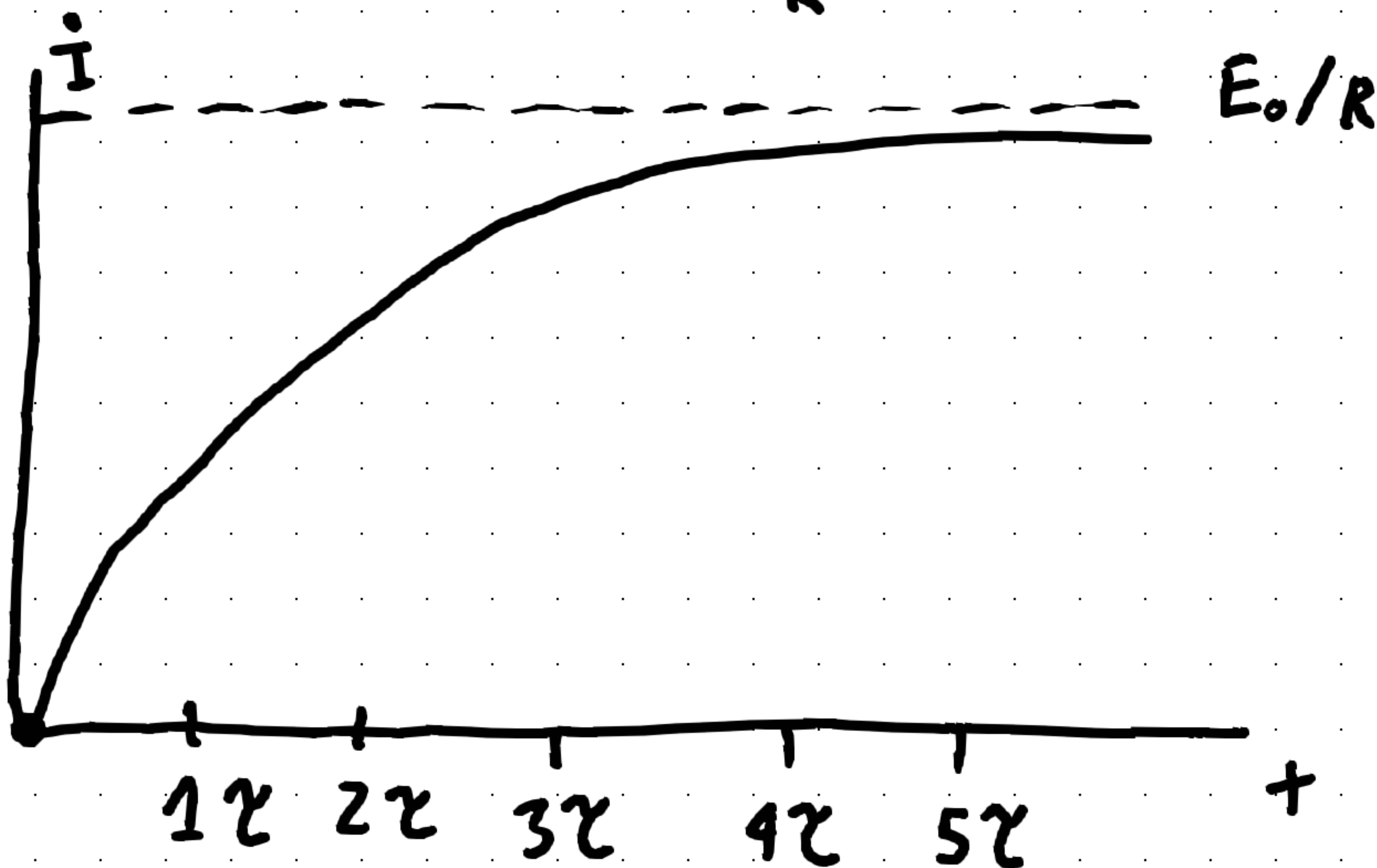
$$I_0 = 0 \quad I(t) = \frac{E_0}{R} \left( 1 - e^{-\frac{R}{L}t} \right)$$




| $t$     | $I(t)$       |              |
|---------|--------------|--------------|
| $1\tau$ | $0.63 E_0/R$ | Transient    |
| $2\tau$ | $0.86 E_0/R$ |              |
| $3\tau$ | $0.95 E_0/R$ |              |
| $4\tau$ | $0.98 E_0/R$ | Steady State |
| $5\tau$ | $\sim E_0/R$ |              |

$$\underbrace{LI}_{\text{Voltage drop across inductor}} + \underbrace{RI}_{\text{Voltage drop across resistor}} = \underbrace{E_0}_{\text{Total voltage to allocate across L and R}}$$

Voltage drop across inductor

Voltage drop across resistor.

Total voltage to allocate across L and R

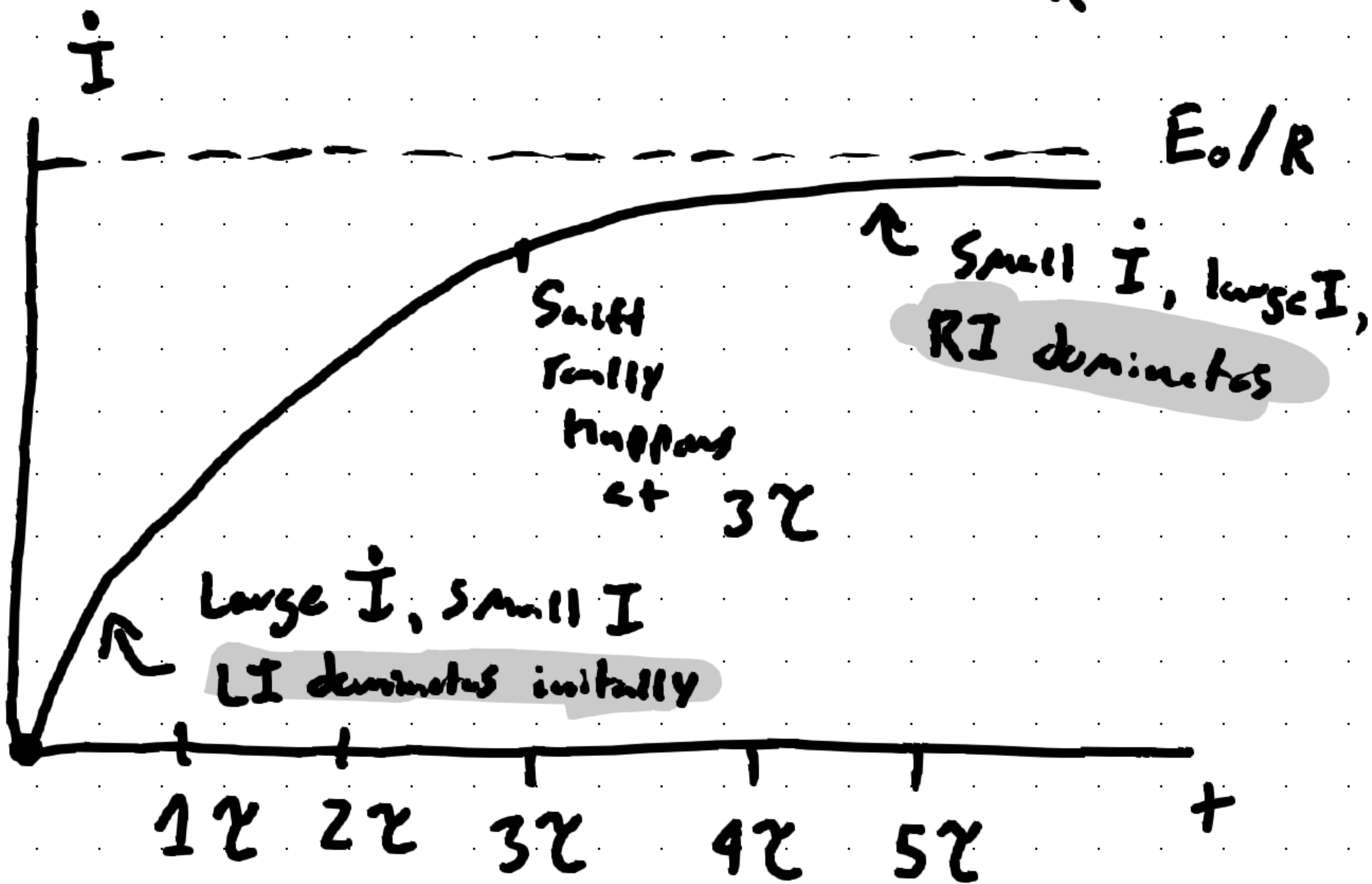



So initially, the fed Voltage is  
being used by mostly the inductor!

Where as past  $3\tau$ , or at a  
later time the resistor dominates.

At small time:

$$e'' = 1 + \ddot{u}$$

near

$$\ddot{u} = 0$$

$$I(t) \approx \frac{E_0}{R} \left[ 1 - \left( 1 - \frac{R}{L} t \right) \right]$$

$$\approx \frac{E_0}{L} t \quad \text{linear approximation}$$