

Digital Circuits 1: EEED 2200

Lecture 2

Bit = 1 bit

nibble = 4 bits

byte = 8 bits

Switch Logic

TTL

CMOS, 3.3V Logic
most circuits now

Dynamic Memory

on chip non
volatile memory

Binary 0

Binary 1

Circuit open

Circuit
closed

0-0.8V

2.0-5.0V

0-0.8V

2.0-3.3V

Capacitor
discharged

Capacitor
charged


Not
Blown

Blown

Ideal Switches - Mos Transistors


Nmos - Requires positive "High gate" voltage to close

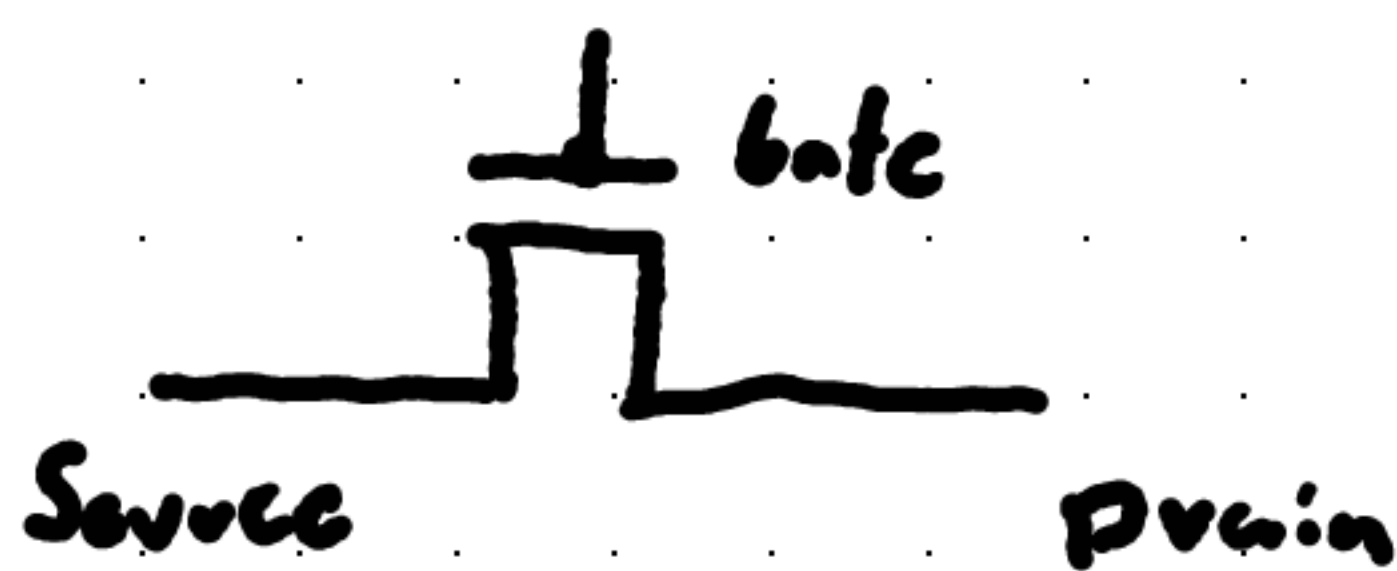Pmos - Requires negative "low gate" voltage to close



Nmos and Pmos Transistors can be put on the same chip. They can be complementary to each other this way! one turns another off!

PNP Inverter Diagram

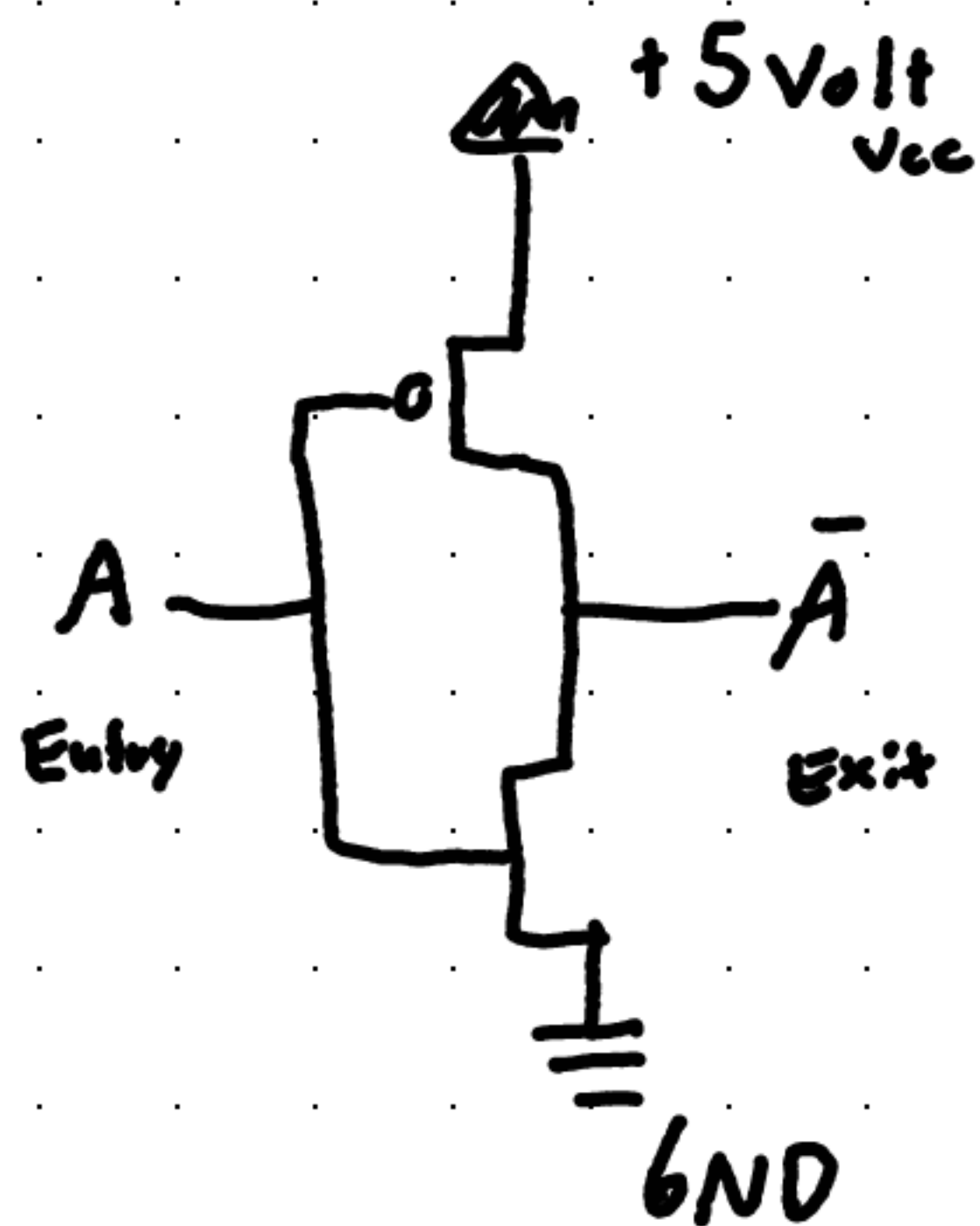

◦ ← This little bubble represents negation

Logic Gates



NOT gate



AND



OR

Fundamental
gates!



NAND



NOR



XOR



XNOR

"Odd number of
Inputs High, output
should be high"

"Even number of
Inputs high,
output is high"

Truth Tables - For Gates

NOT

A	\bar{A}
0	1
1	0

AND

B	A	AB
0	0	0
0	1	0
1	0	0
1	1	1

NAND

B	A	\overline{AB}
0	0	1
0	1	1
1	0	1
1	1	0

OR

B	A	A+B
0	0	0
0	1	1
1	0	1
1	1	1

NOR

B	A	$\overline{A+B}$
0	0	1
0	1	0
1	0	0
1	1	0

XOR

B	A	$A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

XNOR

B	A	$\overline{A \oplus B}$
0	0	1
0	1	0
1	0	0
1	1	1


Boolean Addition

$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 1 = 1$$

Significance of Model Numbers

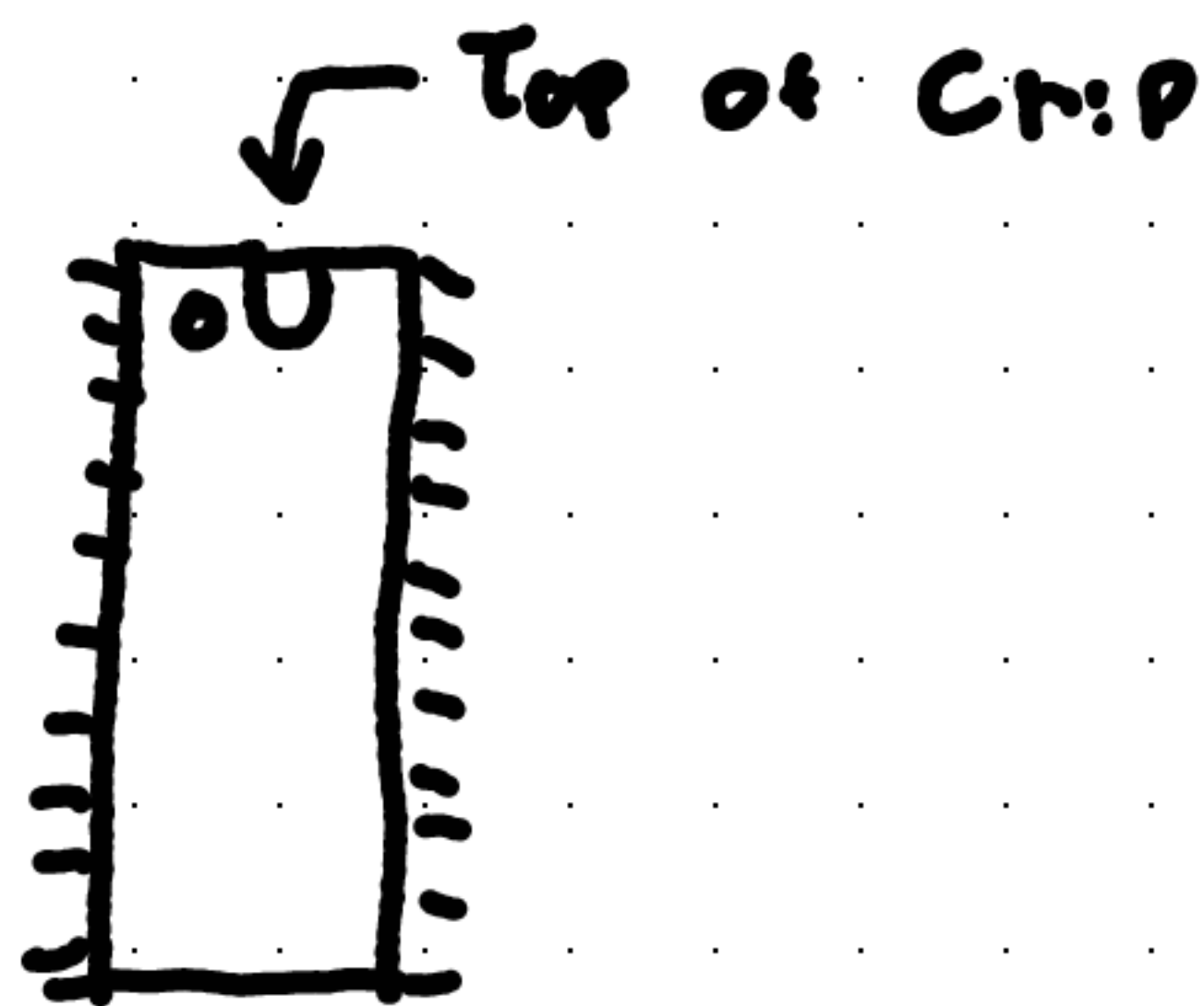

Prefix

74: Commercial Temperature Range

54: Military Temperature Range

Number

Significance

7400	→	NAND gate
7408	→	AND gate
7402	→	NOR gate
7486	→	XOR gate
7432	→	OR gate
7404	→	INV gate

