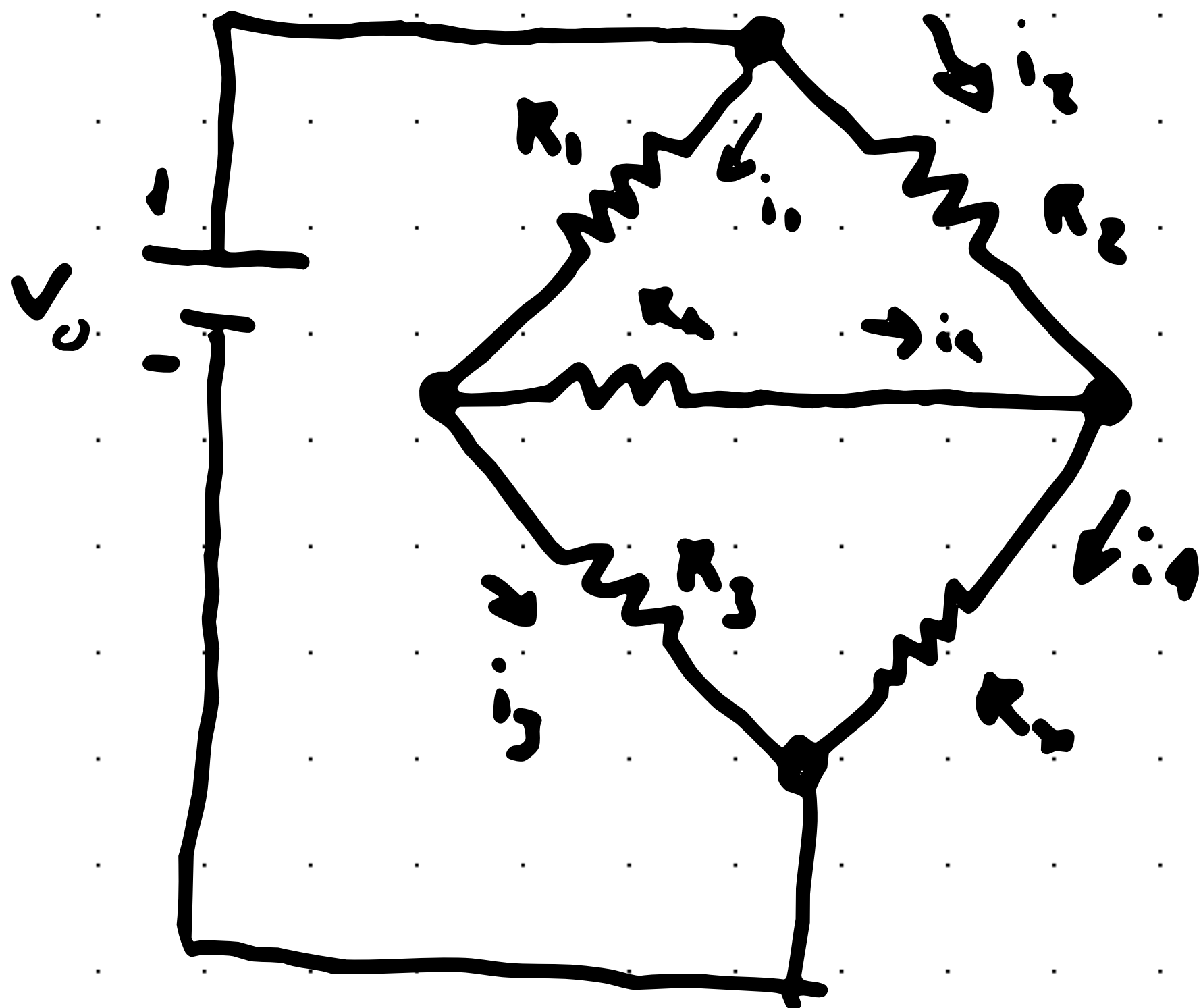


Tutorial 3 Solutions

ECED2000

- a) If $R_1 = 1\Omega$ and $R_2 = 2\Omega$ and $R_x = 3\Omega$ what value should R_3 be adjusted so as to ensure a balanced condition?



- a) Use ^{Wheatstone} Bridge equation

$$R_x R_1 = R_2 R_3$$

$$(3)(1) = (2)R_3$$


$$R_3 = \frac{3}{2} = 1.5\Omega$$

- b) If $V_0 = 6V$, $R_1 = 0.1\Omega$ and R_x is connected to be 3.01Ω , what would be reading on the Ammeter?

KVL and KCL will

be here

Mesh Analysis

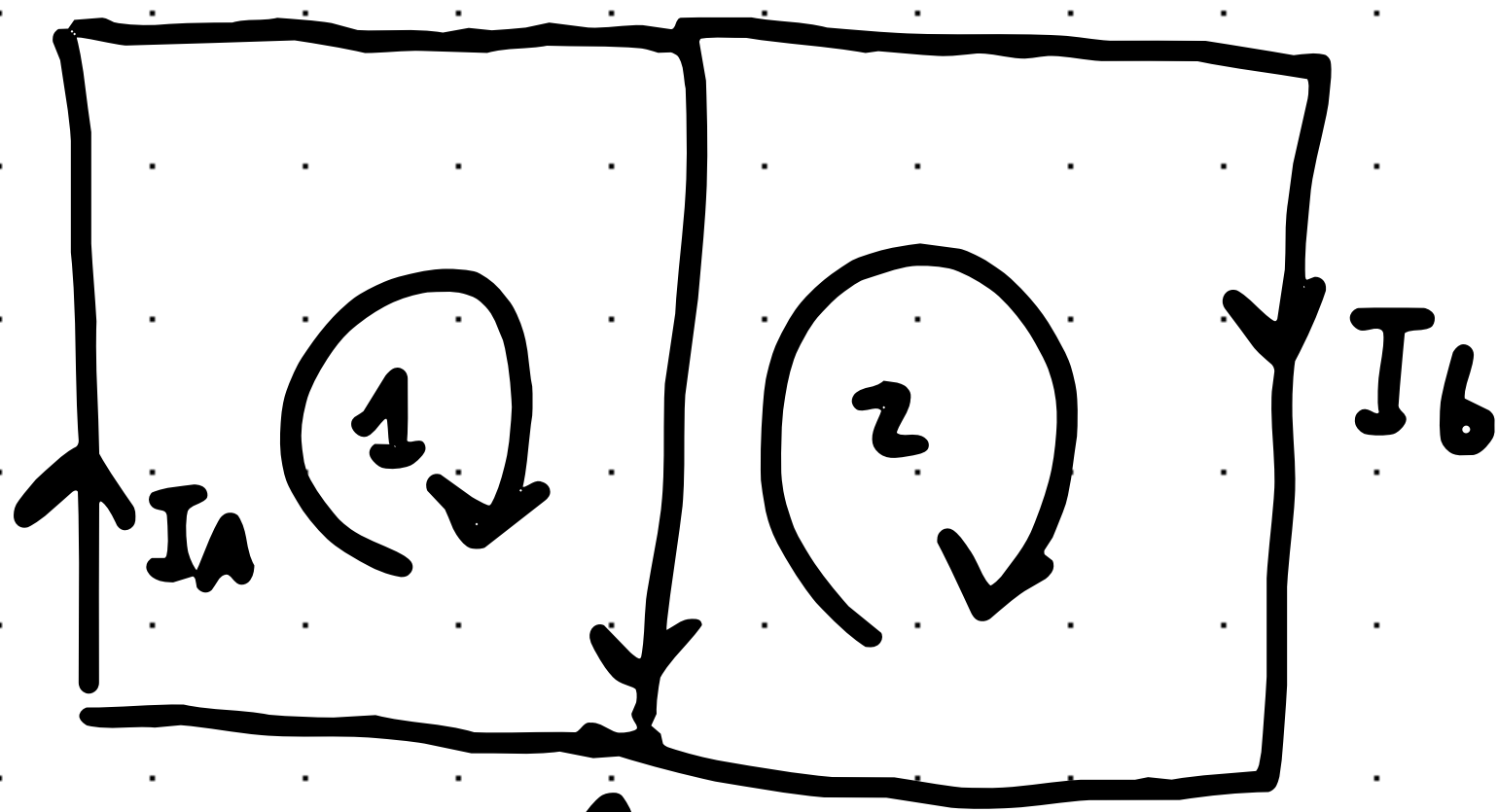


↖ This would be
 $I_A - I_B!$

- Both loops have to be going the same way!
- Fundamentally very similar to KCL and KVL.

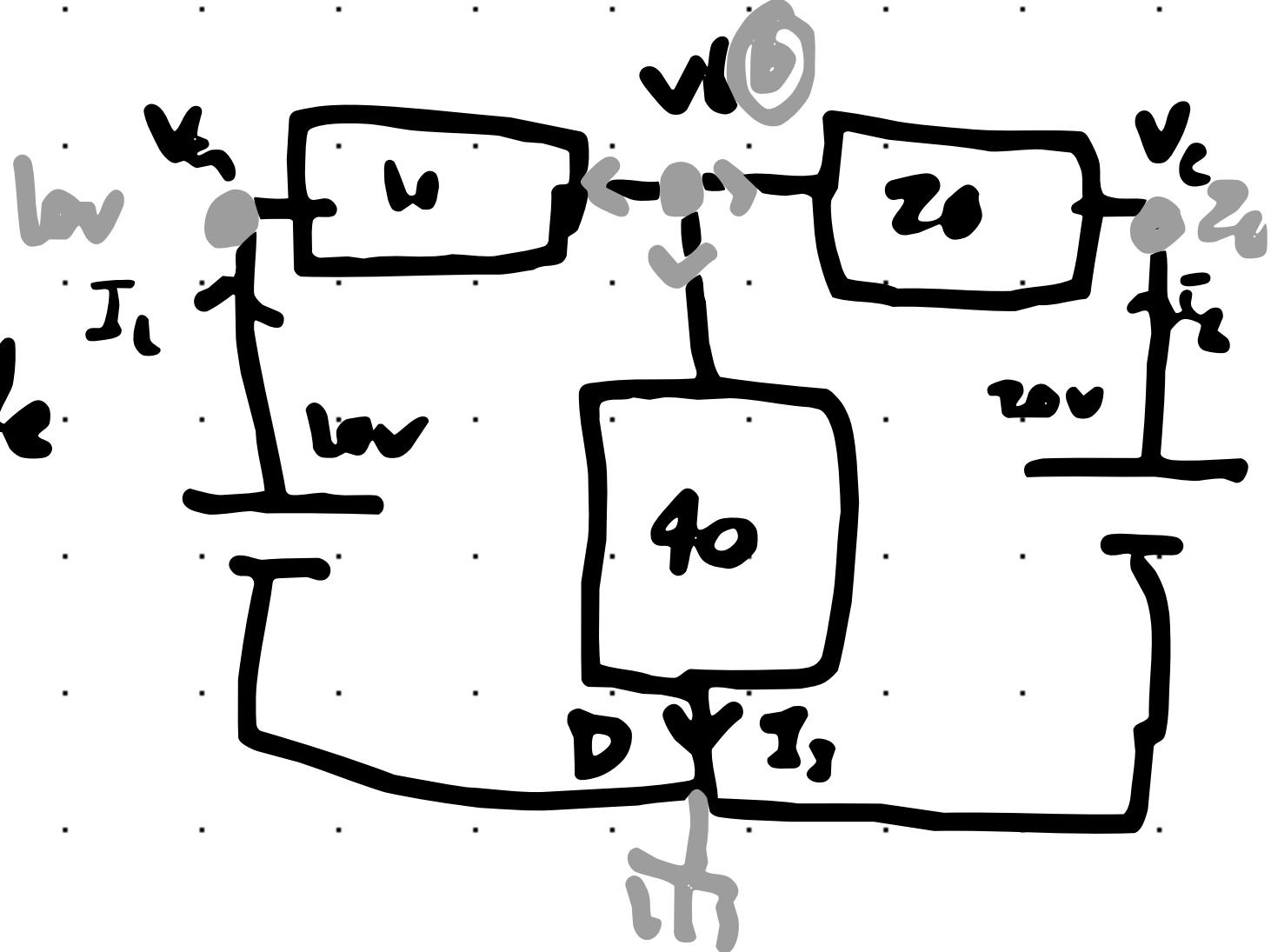Problem 2

Calculate I_1 , I_2 , I_3 and calculate the total power dissipated.



Node Analysis

$$\sum I = 0 \quad \text{Node b} \quad \frac{V_b - 10}{10} + \frac{V_b - 20}{20} + \frac{V_b}{40} = 0$$


$$V_b = \frac{80}{7} \text{ V}$$

$$V = I R$$

$$I_1 = \frac{10 - \frac{80}{7}}{10} = -0.14 \text{ A}, \quad I_2 = \frac{20 - \frac{80}{7}}{20} = 0.43 \text{ A}$$

$$I_3 = \frac{V_b}{40} = \frac{\frac{80}{7}}{40} = \frac{2}{7} \text{ A}$$

Now, do it with Mesh Analysis

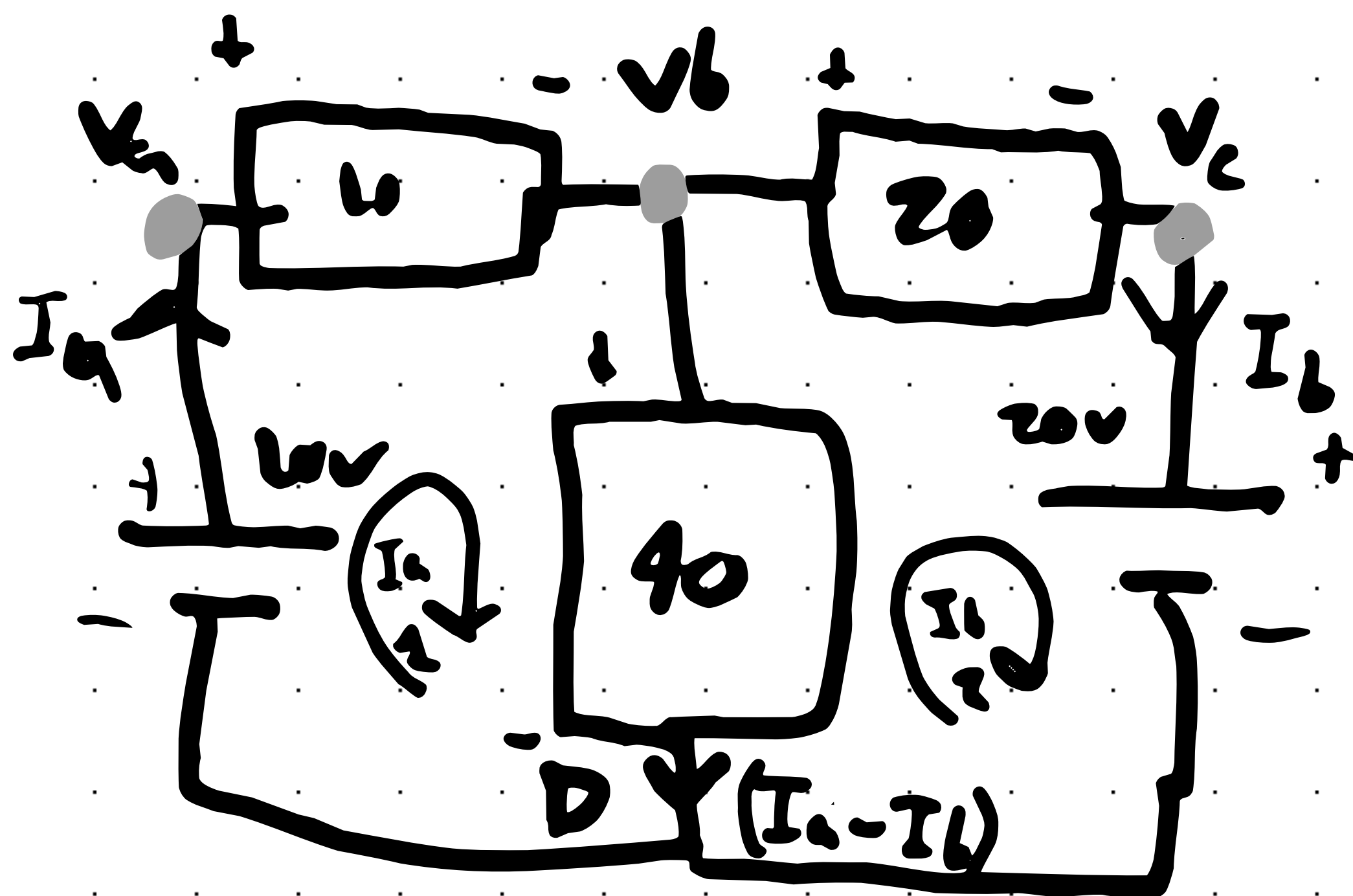

$$\sum_{\text{mesh 1}} V = 0$$

$$10 - 10I_a - 40(I_a - I_b)$$

①


$$\sum_{\text{mesh 2}} V = 0$$

$$40(I_a - I_b) - 20I_b - 20 = 0$$

②

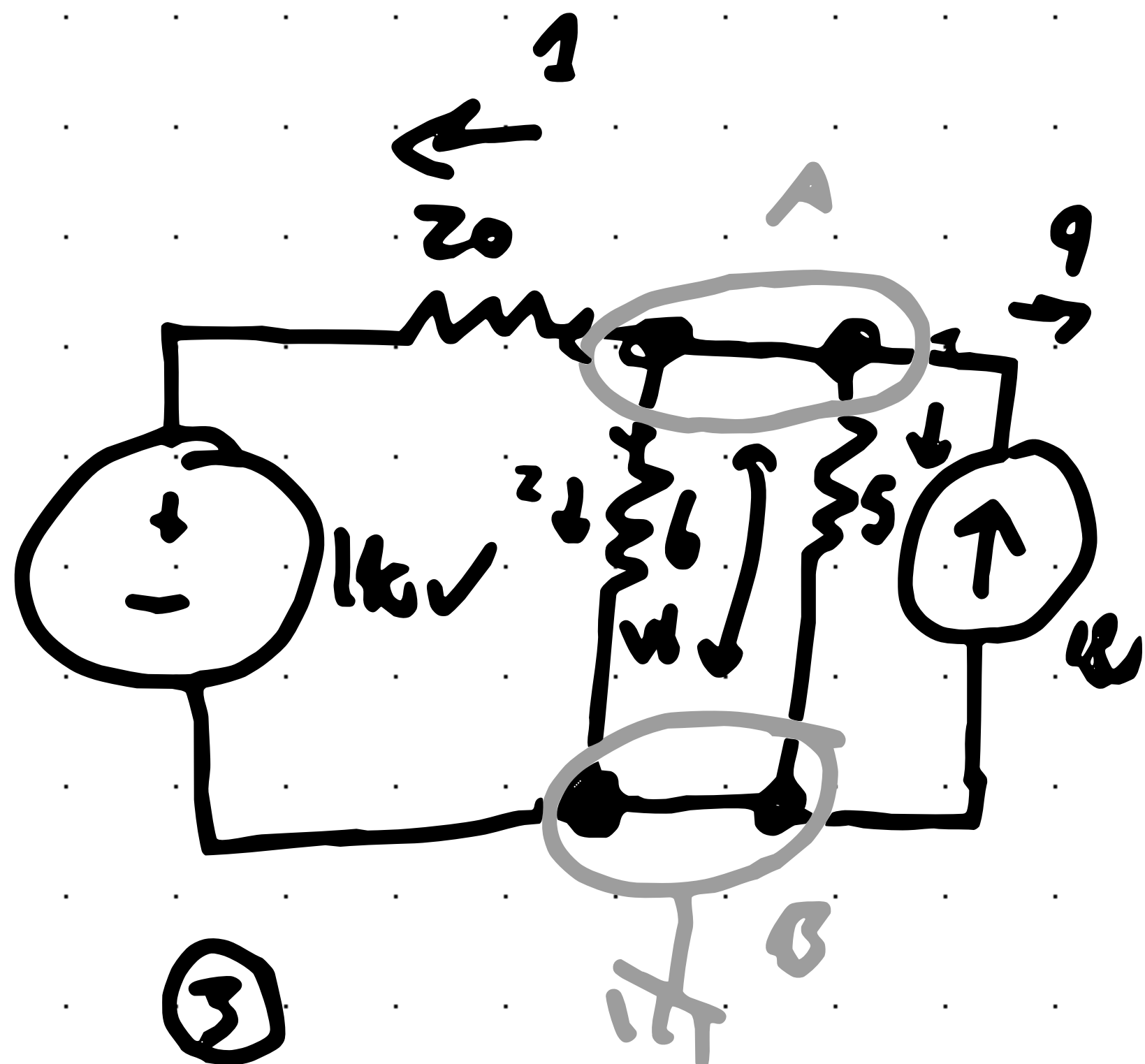Question 3

Use KCL analysis to calculate V_6 and the current in 20Ω




$$\sum I = 0 \text{ Node A}$$

$$\frac{V_6 - 140}{20} + \frac{V_6}{6} + \frac{V_6}{5} + (-18) = 0$$

$$V_6 = 60V$$

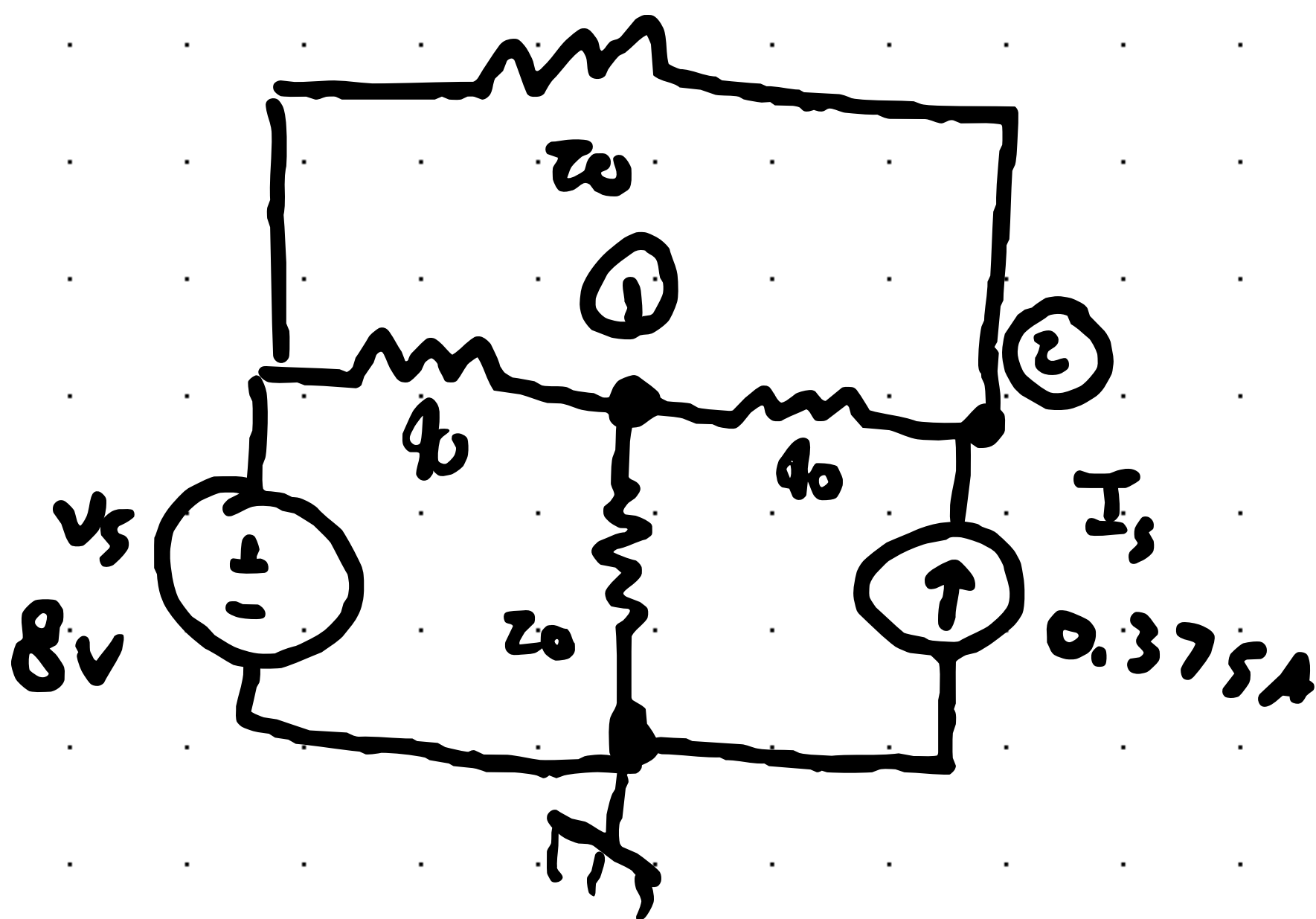Question 4

Use the Node Voltage Method to Calculate the Current in R_1 and R_3



$$\sum I = 0 \quad \text{Node 1} \quad \frac{V_1 - 8}{40} + \frac{V_1 - 0}{20} + \frac{V_1 - V_2}{40}$$

$$\sum I = 0 \quad \text{Node 2} \quad \frac{V_2 - V_1}{40} + \frac{V_1 - 8}{20} + (-0.375) = 0$$

$$V_1 = 5V$$

$$V_2 = 12V$$


$$I_1 = \frac{8 - 5}{40} = \frac{3}{40} A$$

$$I_2 = \frac{V_2 - V_1}{40} = \frac{12 - 5}{40} =$$

$$0.175A$$

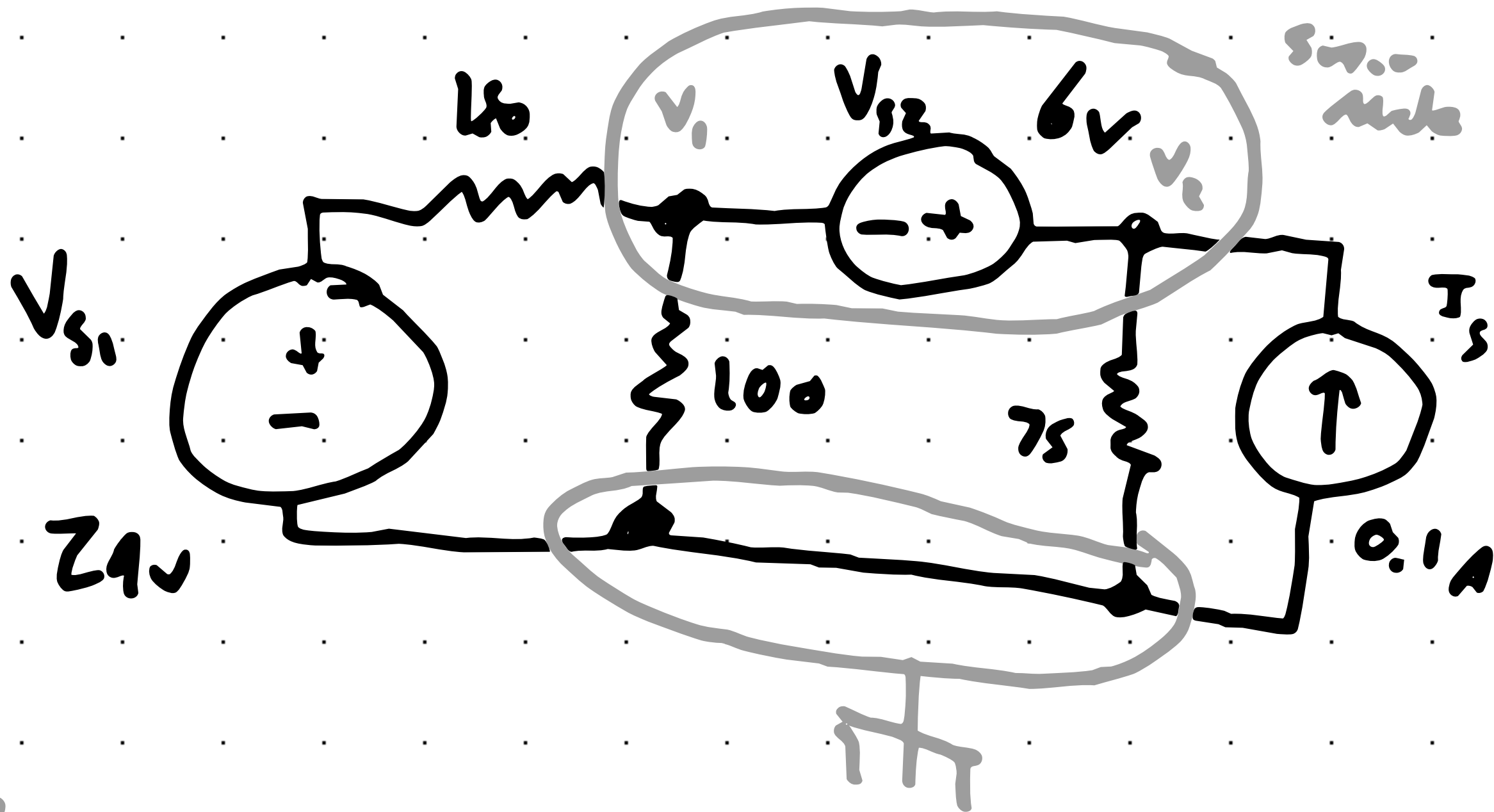Q5

Calculate the current in R_1 and R_2 using nodal analysis



$$\sum I = 0 \quad \frac{V_1 - 24}{150} + \frac{V_1}{100} + \frac{V_2}{75} + (0.1) = 0 \quad (1)$$

$$V_2 - V_1 = 6V, \quad V_2 = 6 + V_1 \quad (2)$$

Sub Eqn 2 into Eqn 1

$$\frac{V_1 - 24}{150} + \frac{V_1}{100} + \frac{6 + V_1}{75} - 0.1 = 0$$

$$V_1 = 6V$$

$$V_2 = 6 + V_1 = 12V$$

$$I_1 = \frac{24 - 6}{150} = \frac{18}{150} A$$

$$I_2 = \frac{V_2}{75} = \frac{12}{75} A$$