

Lec 1

Definitions

1 Charge (Q)

2 voltage (V)

3 Current I

"The rate of charge flow"

$$I = \frac{dQ}{dt}$$

Unit

(C/sec) or
Amps (A)

Electric Circuits

• $Q = 1.6022 \times 10^{-19}$ Coulombs

• voltage is the energy
Per unit charge,
Created by the separation.
It is also known as the
Potential Difference
between the two points.

$$V = \frac{dW}{dQ}$$

W = energy

Quantity	Symbol	Unit
voltage	V	volts
Energy	W or E	joules
Charge	Q	C

4 Power [P]

$$P = V i = \frac{dw}{dQ} \frac{dQ}{dt} = \frac{dw}{dt}$$


(power)

"watts"

5 Energy [E] or [W]

$$W = E = \int P dt$$

Recap

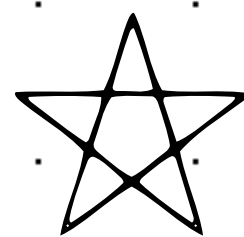

$$V = \frac{dw}{dQ}, \quad i = \frac{dQ}{dt}, \quad P = Vi = \frac{dw}{dt}$$

$$E = \int P dt$$

Power


$I \uparrow$

$$P = +vi$$

Power is
absorbed

$$P = -vi$$


Power is
generated

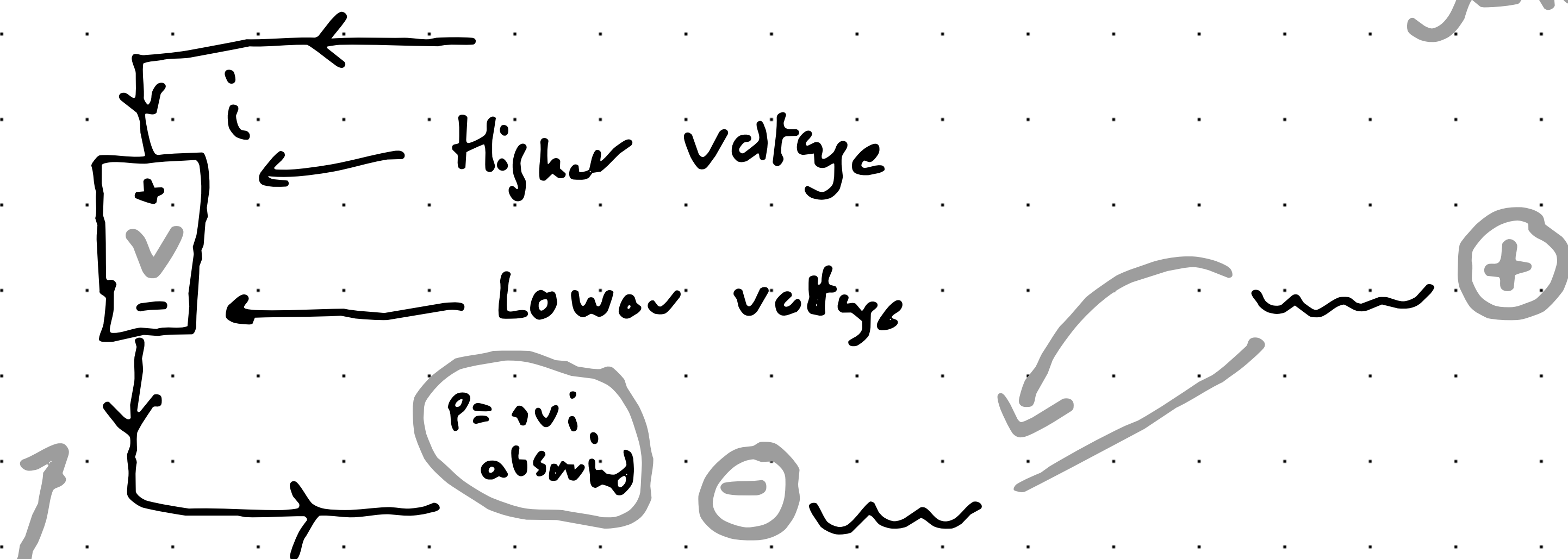

This is probably
a resistor!

Water will naturally
flow down the hill!

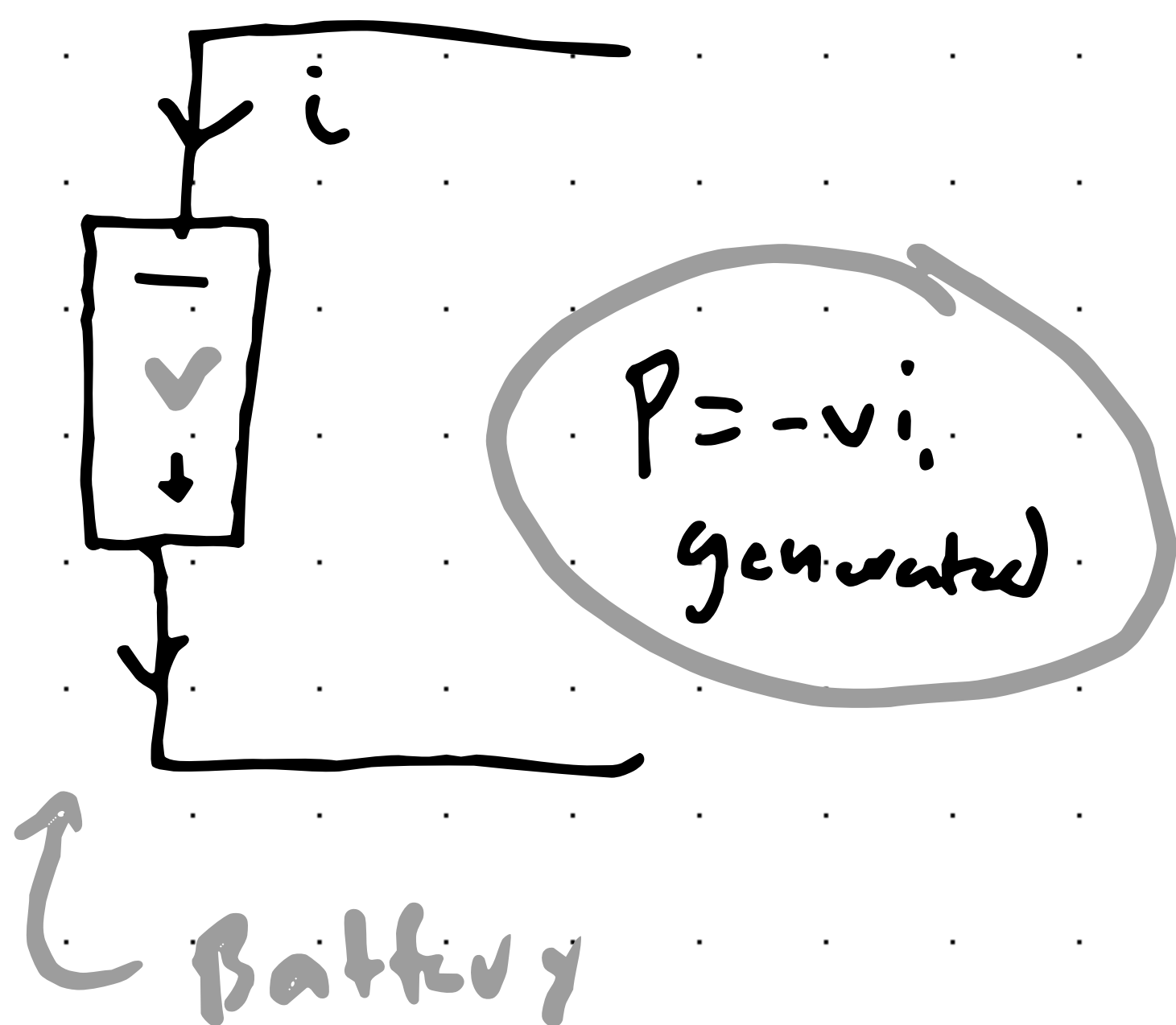To get water to the
top of the hill again,
you need a pump!



Generally Speaking....

If the direction of the current is from positive (high) voltage to negative (low) voltage, then this element is absorbing power

6 The Conservation of Power law


For any closed loop...

$$\sum |P_{\text{gen}}| = \sum |P_{\text{abs}}|$$

(Power generated) (Power Absorbed)

EX

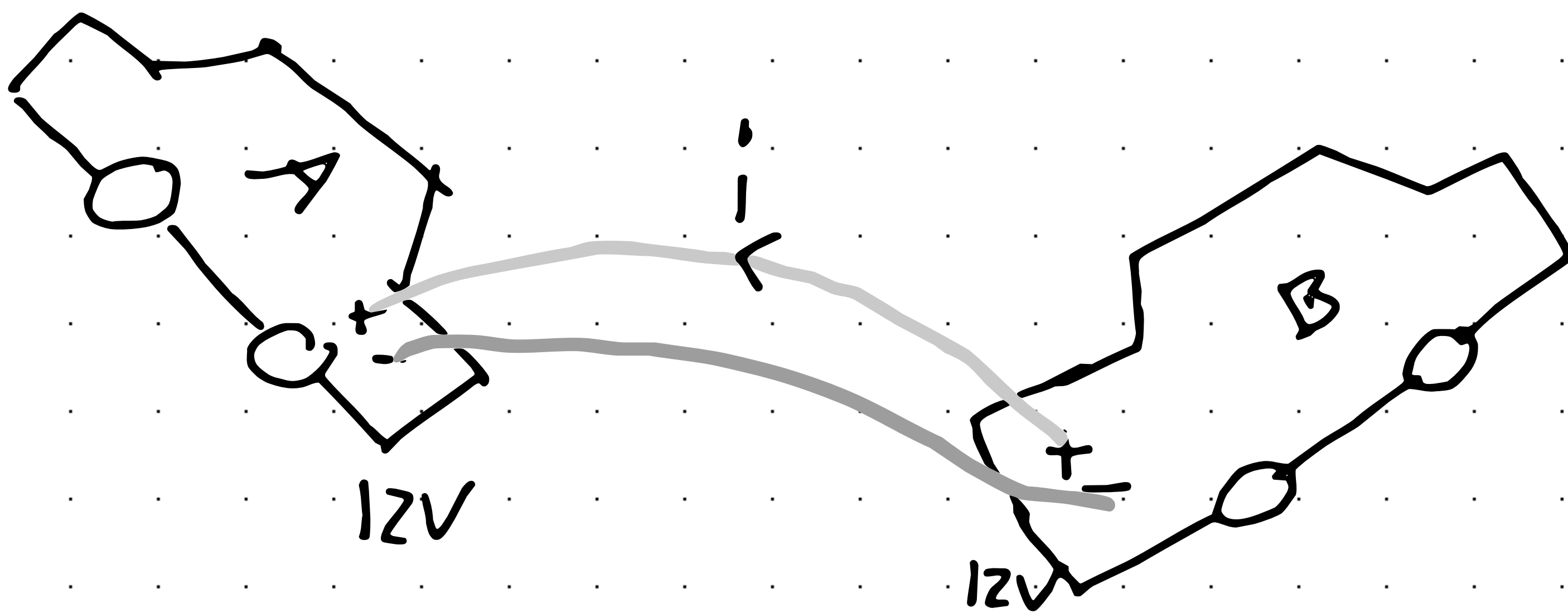When a car has a dead battery, it can often be started by connecting the battery from another car. The positive terminals are connected, as are the negative terminals. The connection is as shown



i) When car has the dead battery?

A). Because the current is flowing from A, to B!

ii) If this into battery equation
is maintained for one minute
how much energy is transferred?

$$V = 12 \text{ V}$$

$$i = 30 \text{ A}$$

Now P first!

$$P = Vi,$$

$$P = (12)(30)$$

$$P = 360 \text{ W}$$

$$W = \int P dt$$



$$W(t) = \int_0^{60} 360 dt = 360t \Big|_0^{60}$$

$$360(60-0)$$

$$21600 \text{ J}$$

EX

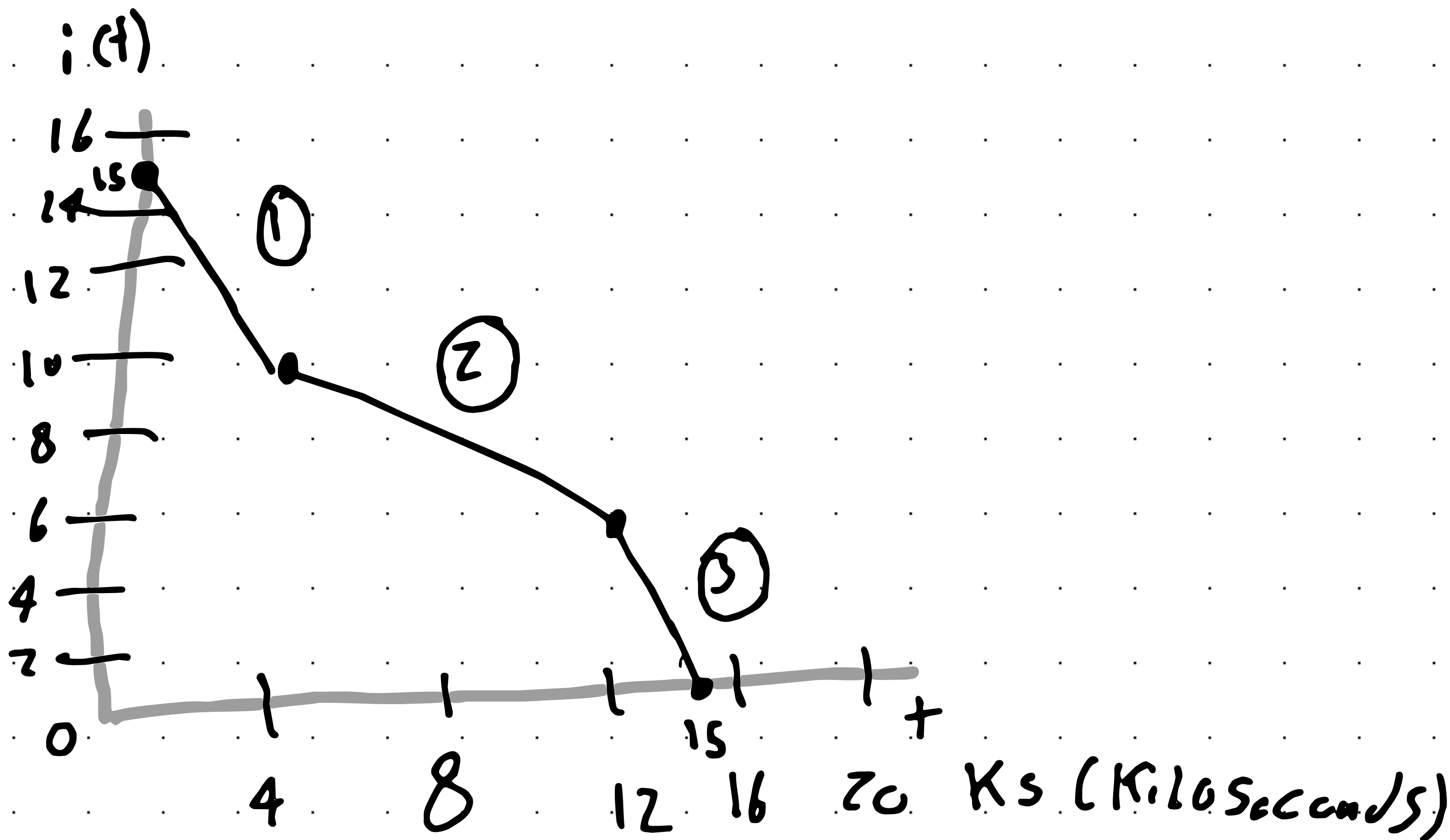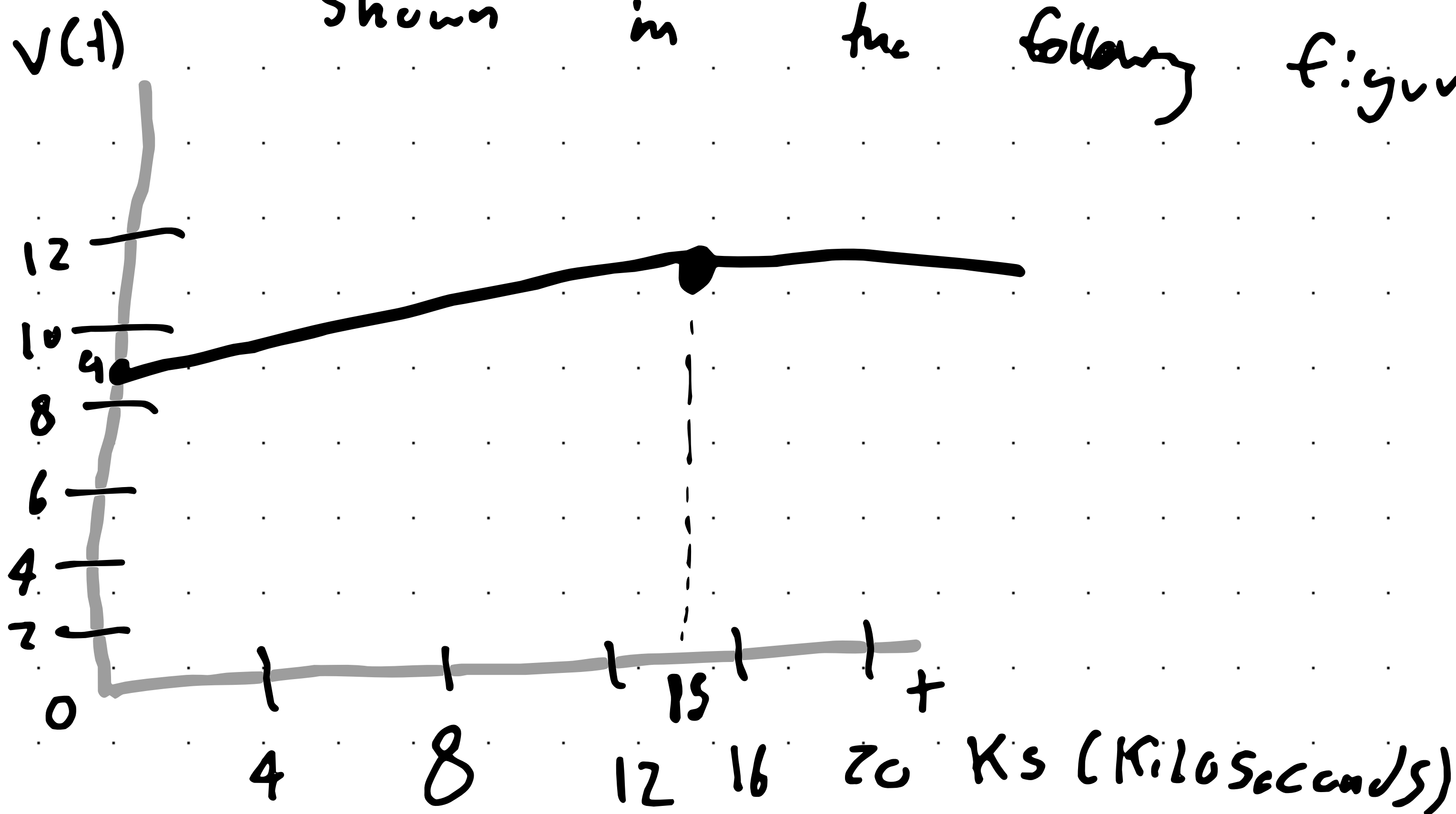The Voltage and Current at the "terminals" of a certain car battery during a charge cycle are shown in the following figures



a) Calculate the total charge transferred to the battery

We know that

$$i = \frac{dQ}{dt}, \text{ so } Q = \int i dt!$$

$Q = \int i dt$, or just the area under the curve... right?

If we section up the graph.

$$= \left[\frac{1}{2}(4)(5) + (4)(10) + \frac{1}{2}(8)(4) + (6)(8) + \frac{1}{2}(3)(6) \right] \times 10^3$$


To get us
out of kiloseconds

$$= 123000 \text{ C}$$

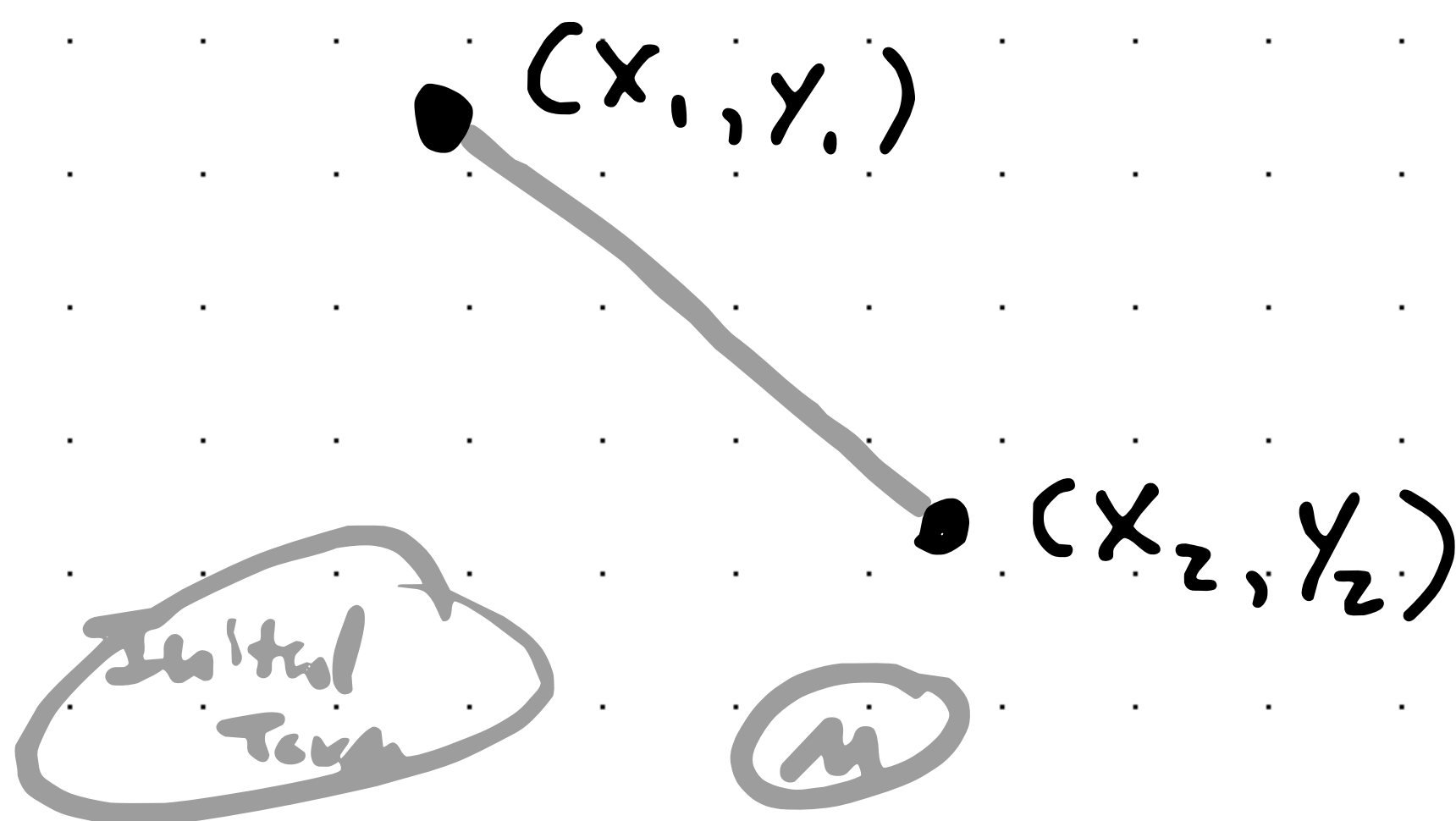b) Calculate the total energy transferred to the battery

Equation of a straight line... Reminder!

$$\frac{y - y_1}{x - x_1} = \frac{y_2 - y_1}{x_2 - x_1}$$



For line 1!

$$\frac{i - 15}{t - 0} = \frac{10 - 15}{4 - 0}$$

$i = \text{Initial Term} - \text{slope}$

$$i_1 = 15 - 1.25 \times 10^{-3} t$$

$$0 \leq t \leq 15 \text{ ks}$$

$$i_2 = 12 - 0.5 \times 10^{-3} t$$

$$4 \text{ ks} \leq t \leq 12 \text{ ks}$$

$$i_3 = 30 - 2 \times 10^{-3} t$$

$$12 \text{ ks} \leq t \leq 15 \text{ ks}$$

Voltage

$$v(t) = 0.2 \times 10^{-3} t + 9$$

$$0 \leq t \leq 15 \text{ ks}$$

Now, we need to calculate the
power for each period

$$\underline{0 < t < 4\text{Ks}}$$

$$P_1 = i_1 v$$

$$W_1 = \int_0^{4\text{Ks}} P_1 dt$$

$$\underline{4\text{Ks} < t < 12\text{Ks}}$$

$$P_2 = i_2 v$$

$$W_2 = \int_{4\text{Ks}}^{12\text{Ks}} P_2 dt$$

$$\underline{12\text{Ks} < t < 15\text{Ks}}$$

$$P_3 = i_3 v$$

$$W_3 = \int_{12\text{Ks}}^{15\text{Ks}} P_3 dt$$

$$\text{Energy}_{\text{Total}} = W_1 + W_2 + W_3$$