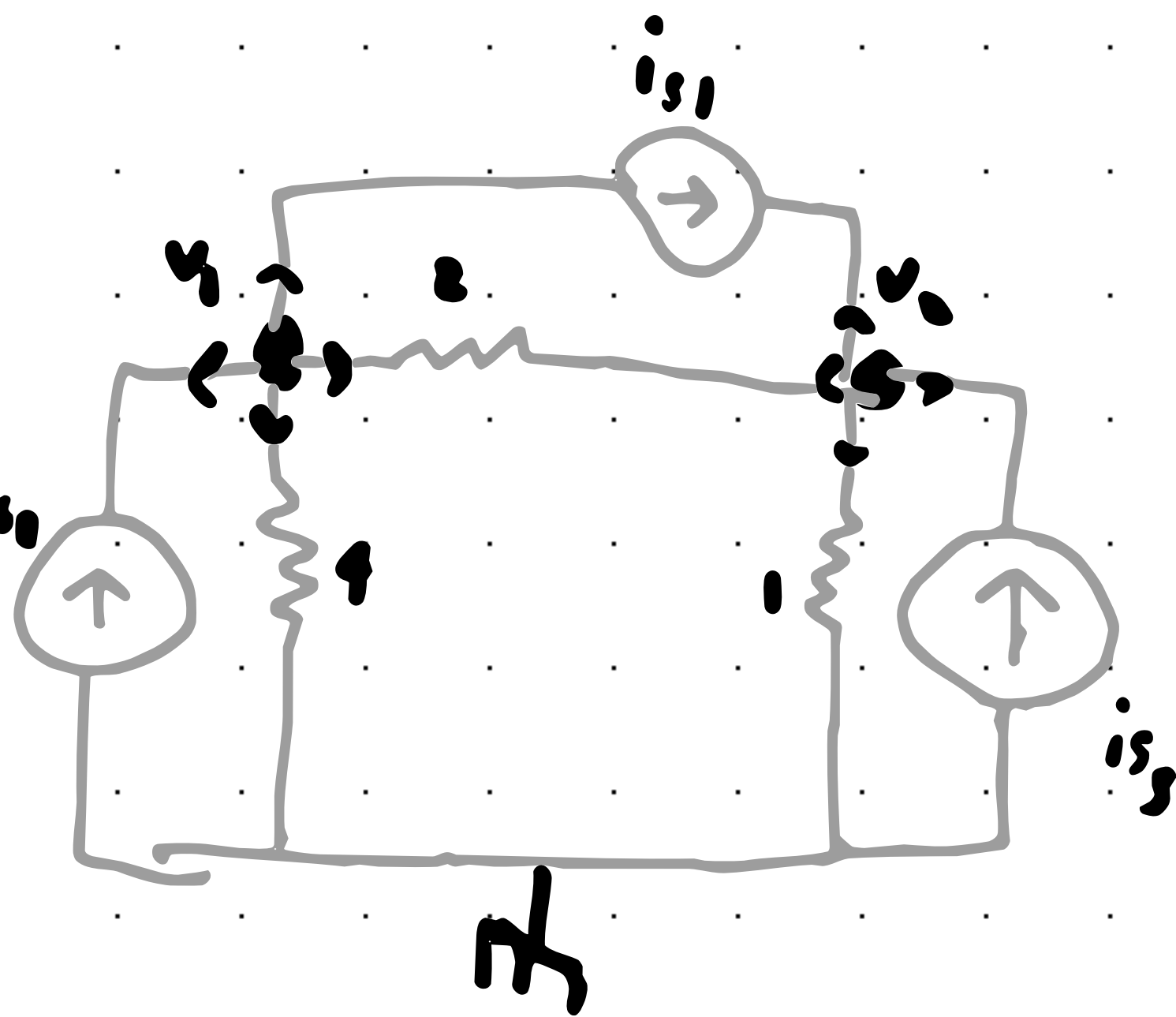


## Nodal Analysis

For the following circuit, write the Node-Voltage equations.

Solution

$$\sum_{\text{Node 1}} I_o - I_{s_2} + I_{s_1} + \frac{v_1}{4} + \frac{v_1 - v_2}{2} = 0$$

$$\sum_{\text{Node 2}} = -I_{s_1} - I_{s_3} + \frac{v_1}{1} + \frac{v_2 - v_1}{2} = 0$$

$$\left(\frac{1}{4} + \frac{1}{2}\right)v_1 + \left(-\frac{1}{2}\right)v_2 = i_{s_2} - i_{s_1} \quad (1)$$

$$\left(-\frac{1}{2}\right)v_1 + \left(\frac{1}{1} + \frac{1}{2}\right)v_2 = i_{s_1} + i_{s_3} \quad (2)$$

$$\left(\frac{1}{4} + \frac{1}{2}\right)v_1 + \left(-\frac{1}{2}\right)v_2 = i_{s_2} - i_{s_1} \quad (1)$$

$$\left(-\frac{1}{2}\right)v_1 + \left(\frac{1}{1} + \frac{1}{2}\right)v_2 = i_{s_1} + i_{s_3} \quad (2)$$


$$\begin{bmatrix} \frac{1}{4} + \frac{1}{2} & -\frac{1}{2} \\ -\frac{1}{2} & \frac{1}{1} + \frac{1}{2} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} i_{s_2} - i_{s_1} \\ i_{s_1} + i_{s_3} \end{bmatrix}$$

This is known as the  
Conductance method!

Conductance ( $G = \frac{1}{R}$  resistors)


→ Aly doesn't  
like this method  
that much, but  
still wants to  
do it.

## Essential Node:

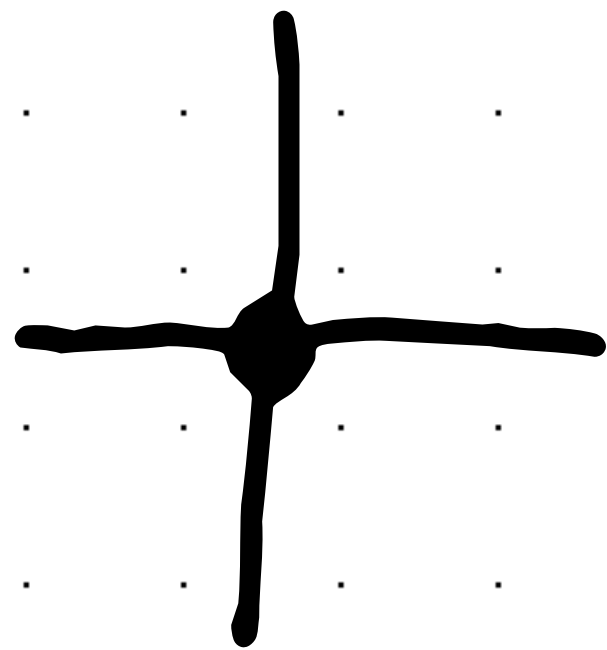

Any node that has three, or more, branches connected together.

## Super Node:

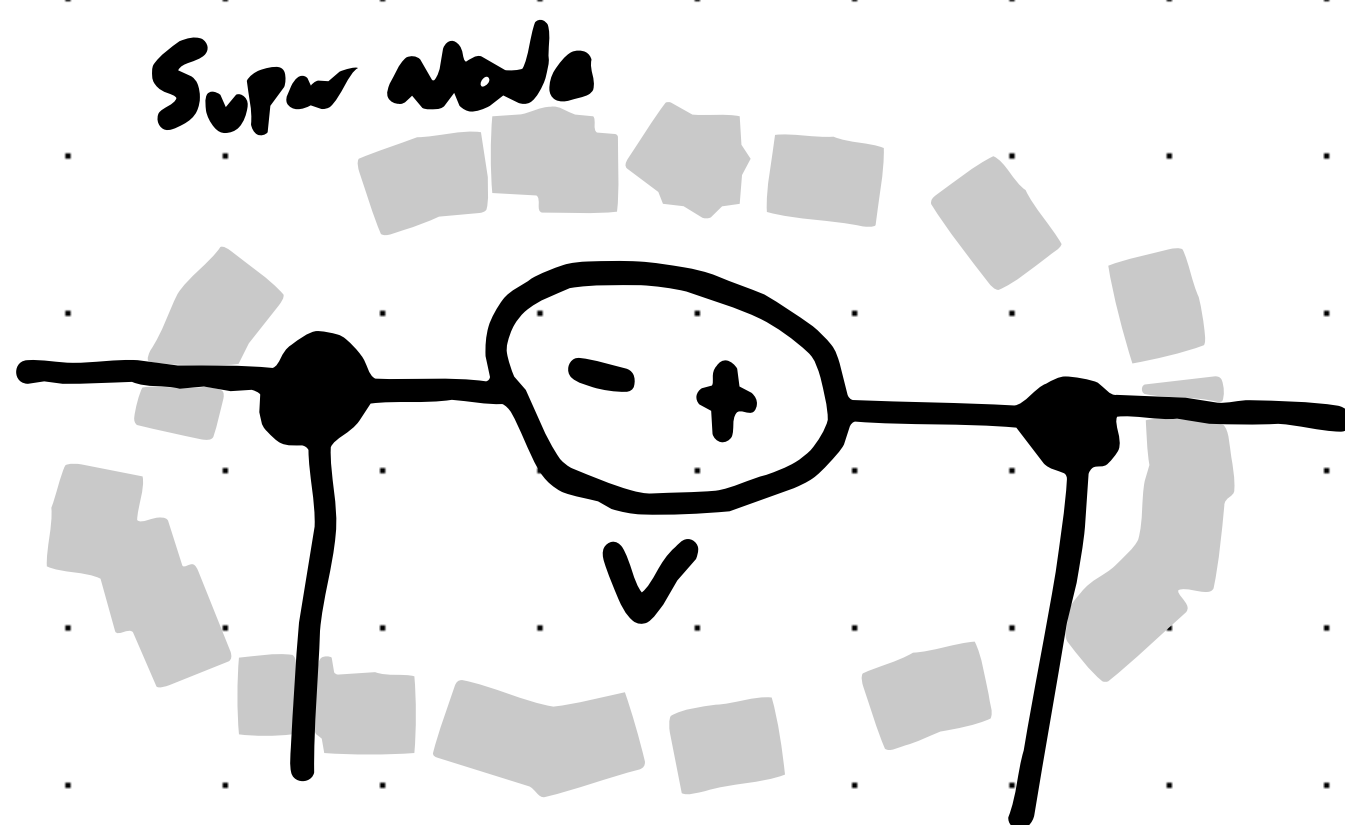


Any two nodes in between a voltage source

There is a proof to say that

$$\sum I = 0 \text{ for the entire Supernode.}$$
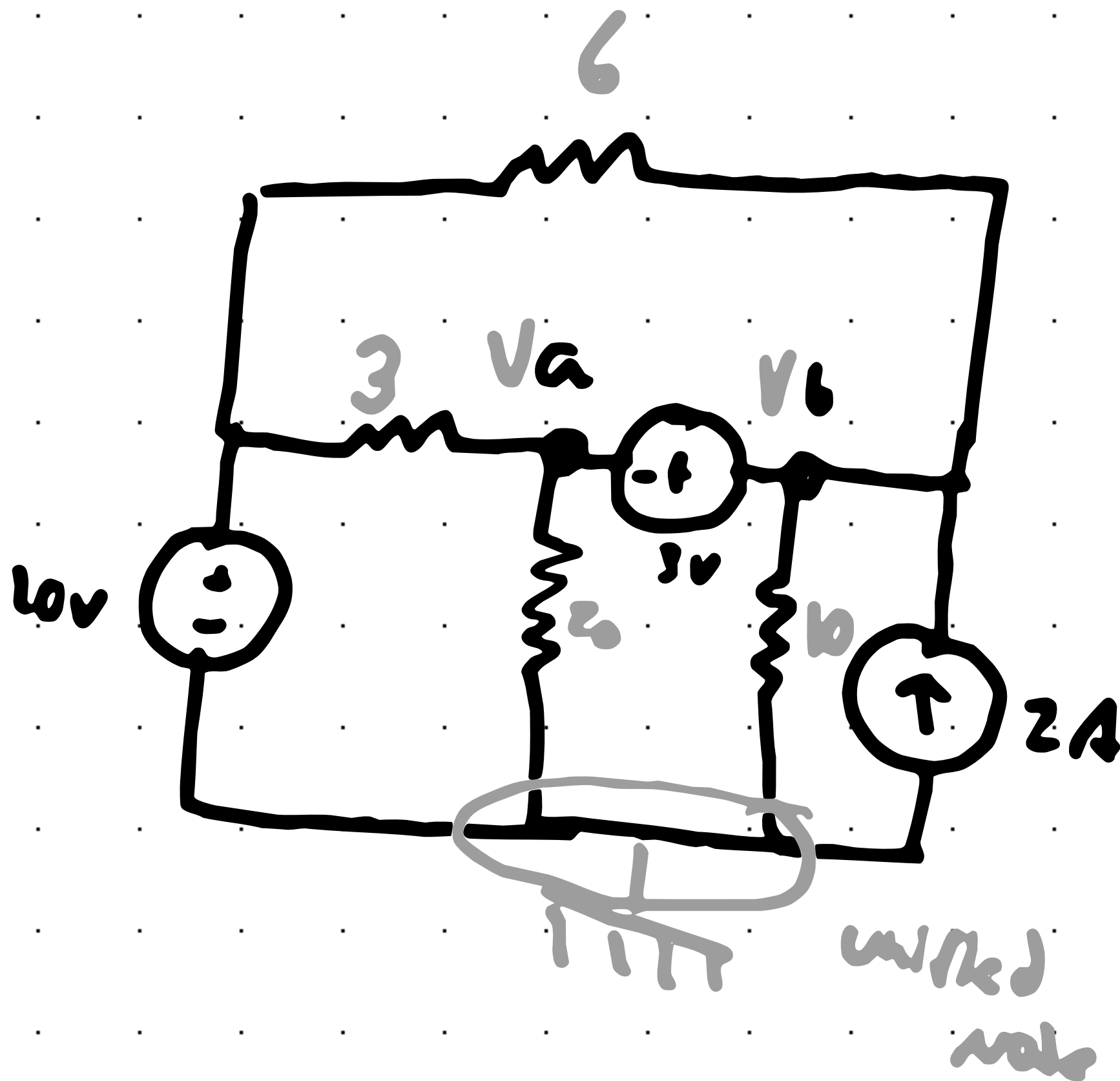
## Example

Use Node Voltage Method to Calculate the Value of  $V_x$



## Solution

$$\sum I = 0 \text{ Node } a = \frac{V_a - 10}{3} + \frac{V_a}{20} + i_s = 0 \quad (1)$$

$$\sum I = 0$$

$$\text{Node } b: -i_s + \frac{V_b}{6} + (-2) + \frac{V_b - 10}{6} = 0 \quad (2)$$

Now substituting  $V_b$  is

$$\frac{V_a - 10}{3} + \frac{V_a}{20} + \frac{V_b}{6} + (-2) + \frac{V_b - 10}{6} = 0 \quad (3)$$

$$V_b - V_a = 3 \quad (4)$$

Now Solving these...

$$\frac{V_a - 10}{3} + \frac{V_a}{20} + \frac{V_b}{10} + (-2) + \frac{V_b - 10}{6} = 0 \quad (3)$$

$$V_b - V_a = 3 \quad (9)$$

$$V_a = 10.91V$$

However, there is an easier way to do this....


Recognize the super node in between  $V_a$  and  $V_b$

$\sum I = 0$ , super node

$$\frac{V_a - 10}{3} + \frac{V_a}{20} + \frac{V_b}{10} + (-2) + \frac{V_b - 10}{6}$$

Wow! That's the same equation as the one from both initial equations!

## Example

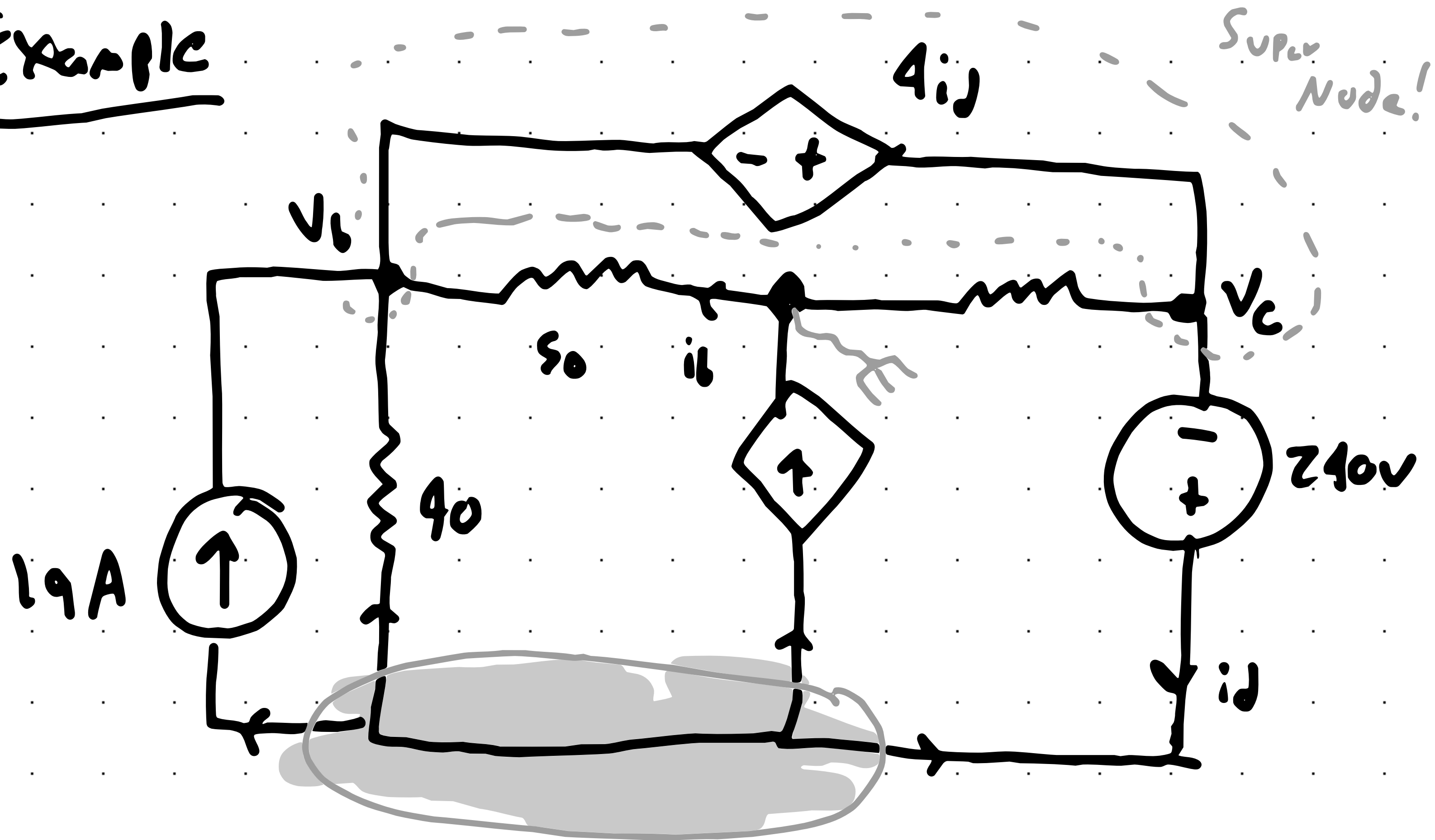

Node  $n$   
( $V_n$ )

## Solution

$$\sum I = 0 \quad \text{at Node A} \quad I_9 + \frac{V_A - V_B}{40} + I_{16} + (-I_7) = 0$$

# Superhero

$$\sum I=0 \quad -19 + \frac{V_1 - V_2}{40} + \frac{V_6 - 0}{5} + i_j + \frac{V_c}{5} = 0$$

$$V_c - V_b = 4j2$$

$$i_b = \frac{0 - V_b}{5}$$

$$\sum I = 0 \quad i_d = 2i_b + \frac{v_a - v_b}{q_0} \quad \text{11g}$$