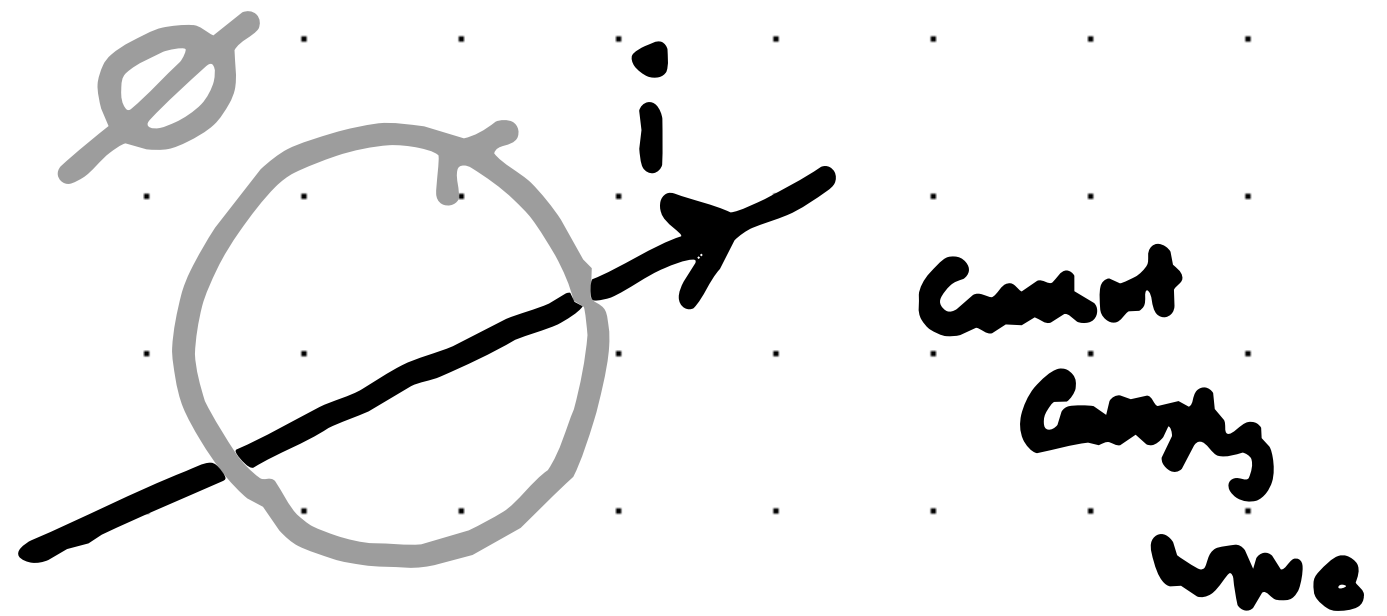


Chapter 6 Energy Storage Elements


① The Inductor



λ : Flux Linkage

$$\lambda = N \emptyset$$

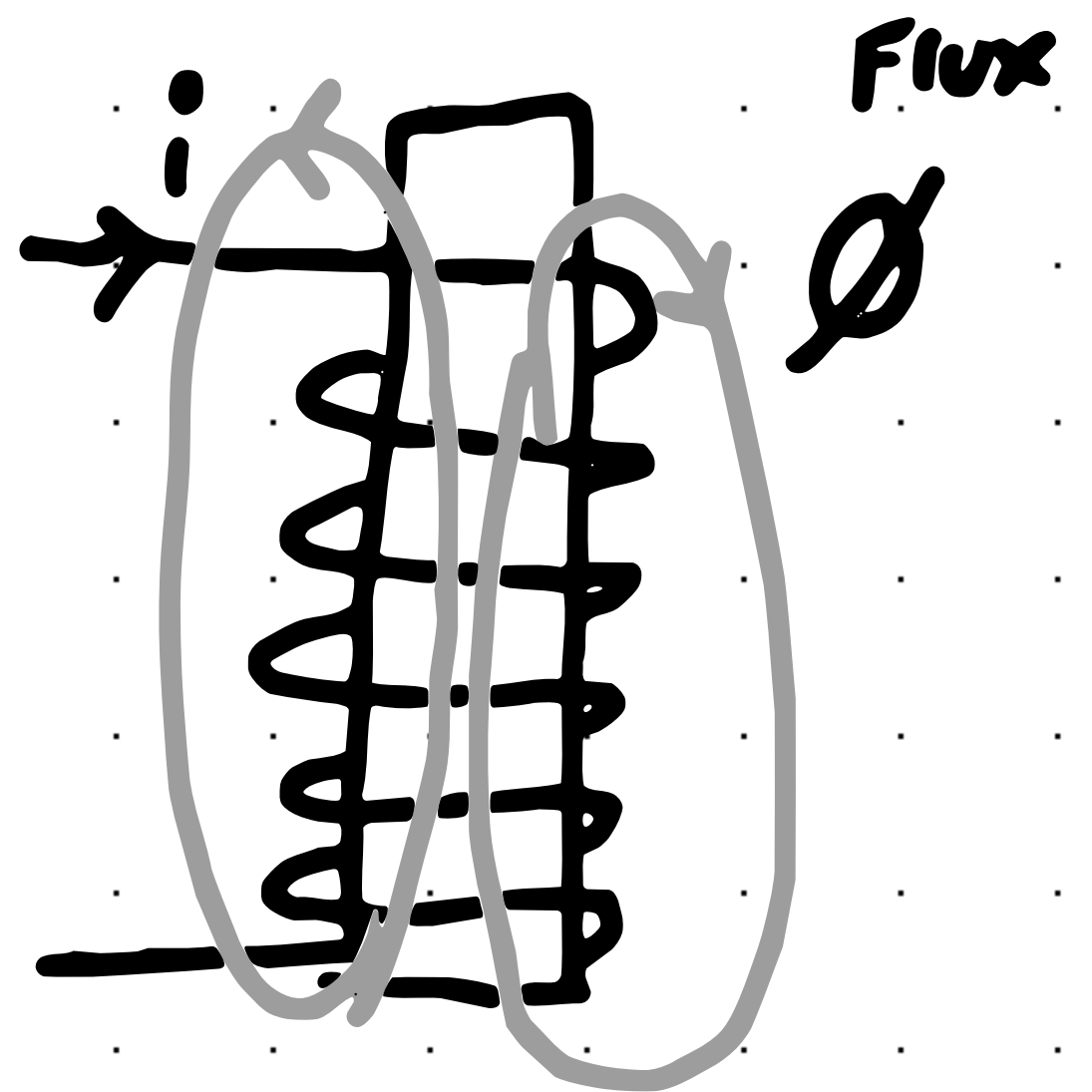\uparrow Magnetic Flux
 \uparrow Number Of Loops




Inductance

$$L = \frac{\lambda}{i}$$

(Inductance)

(Wb/A) or
Henry (H)

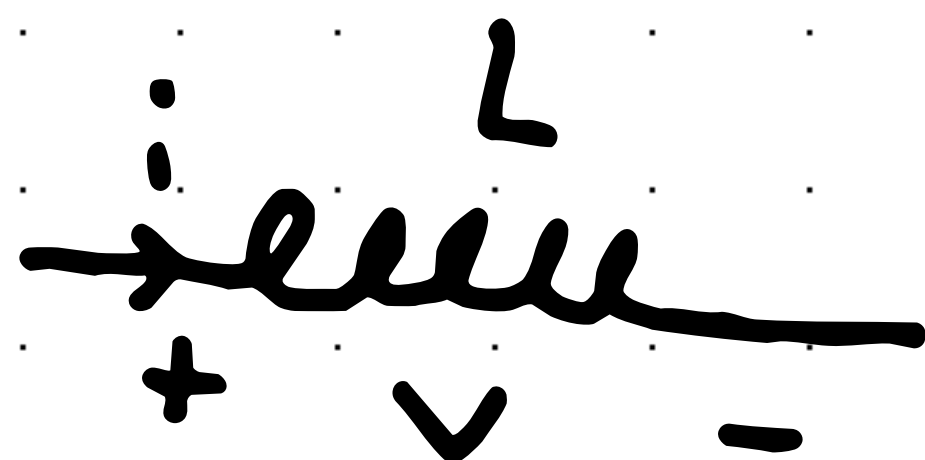

Faraday's Law (one of the Maxwell Equations)

$$V = \frac{d\lambda}{dt} = \frac{d(Li)}{dt} = L \frac{di}{dt}$$

$$V = L \frac{di}{dt}$$

L will be constant for us, but it is variable generally. It relies on Magnetic Flux

For DC Circuits

- The inductor looks like a short circuit.

For the Current at any time

Since $v = L(di/dt)$, There is a proof to say

$$i(t) = \frac{1}{L} \int_{t_0}^t v(t) dt + i(t_0)$$

Current at a time

Power

$$P = v_i = \left(L \frac{di}{dt}\right) i = L i \frac{di}{dt}$$

$$P = L i \frac{di}{dt}$$

Energy

$$W = \frac{1}{2} L i^2, \quad W = \int L i di$$

Summary


$$V(t) = L \frac{di}{dt}$$

$$i(t) = \frac{1}{L} \int_{t_0}^t V(t) dt + i(t_0)$$

$$P = v_i$$

$$W = \int L i di$$


Inductors Connected in Series

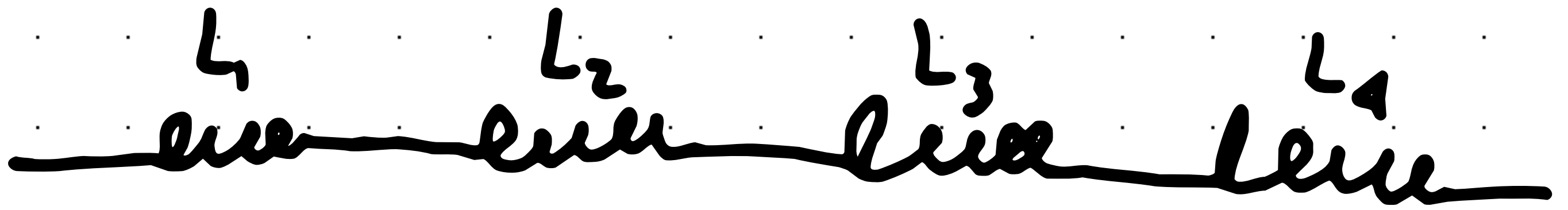

$$L_{eq} = \sum L_i = L_1 + L_2 + L_3 + L_4$$



Inductors Connected in Parallel

$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} \dots$$

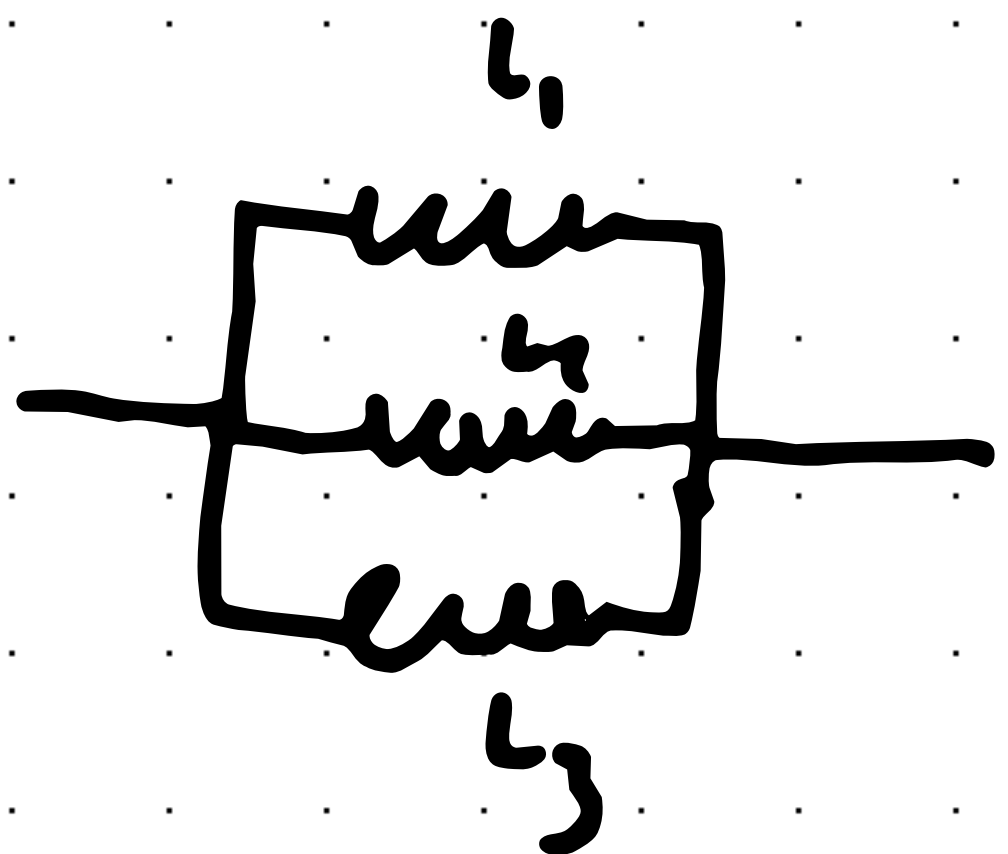

Example 1

(Conversion of photovoltage to AC)

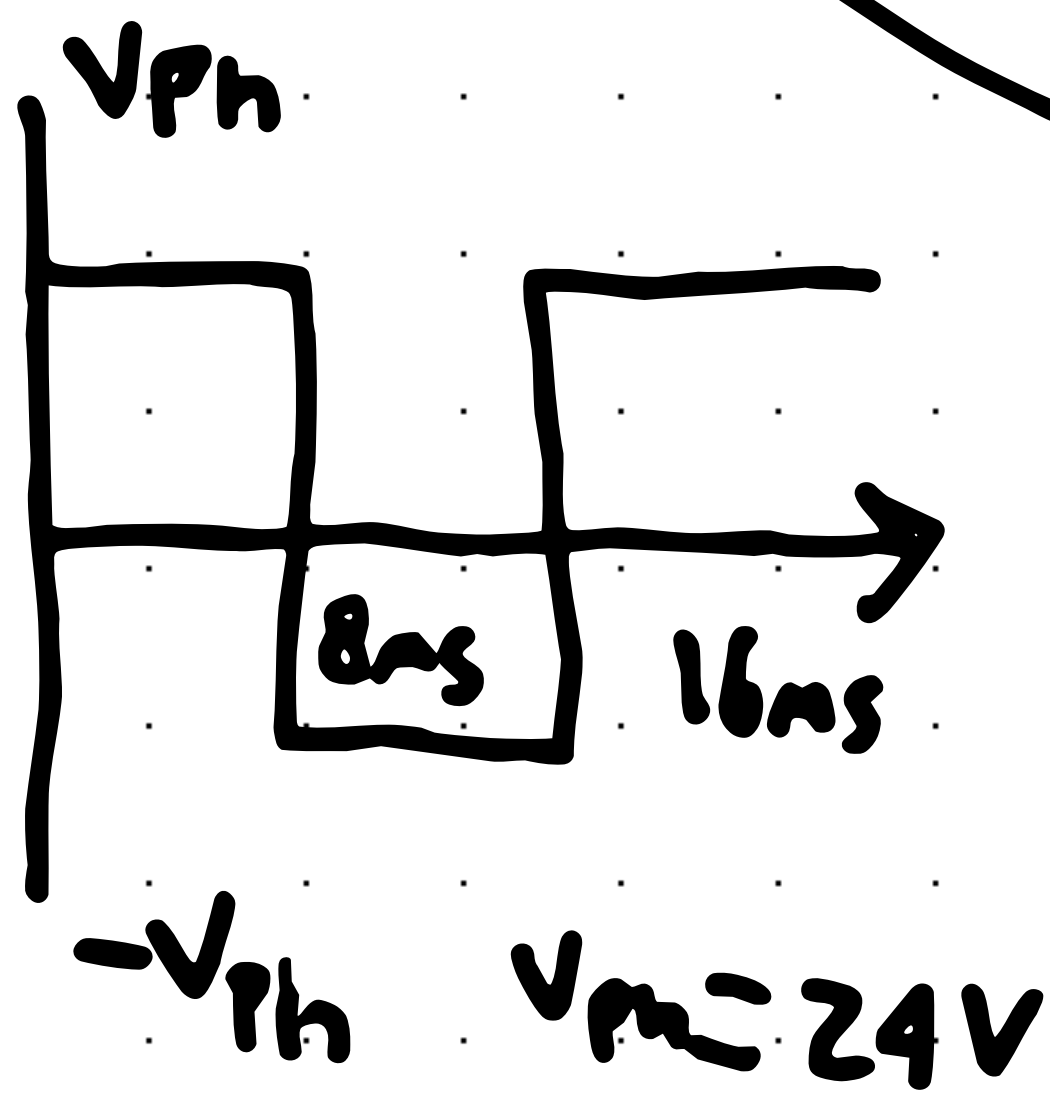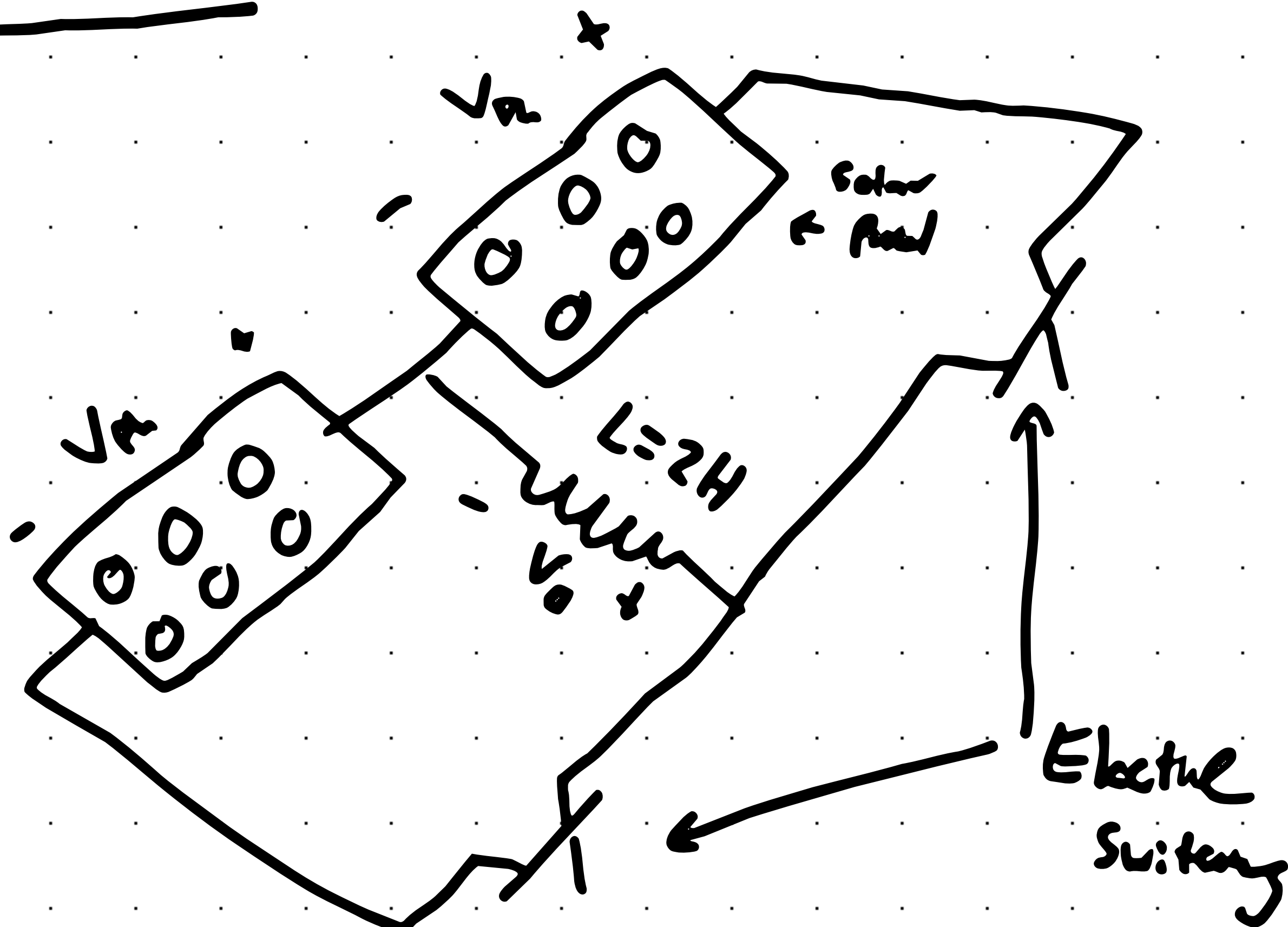

Find the Current Equations and draw the relation between i and t

Solution

$$V_{ph} = \begin{cases} 24 \\ -24 \end{cases}$$

$$0 \leq t \leq 8ms$$

$$8 < t < 16ms$$

$$i(t) = \frac{1}{L} \int_{t_0}^t V_{ph} dt + i(t_0)$$

$$= \frac{1}{2} \int_0^t 24 dt + i_0 = \frac{1}{2} (24)t \Big|_0^t + (-48mA) =$$

$$i(t) = 12t - 48mA \quad 0 < t \leq 8ms$$

For $8 < t \leq 16\text{ms}$

$$V_0 = -24\text{V}$$

$$i(t) = \frac{1}{L} \int_{t_0}^t V_{(t)} dt + i(t_0)$$

\uparrow \uparrow
 -24 $t_0 = 8\text{ms}$

$$I_{(t)} = \frac{1}{2} = \int_{8\text{ms}}^t -24 dt + 48\text{mA}$$

(You'll Need t_{ms} from the other graph!)

$$= \frac{1}{2} [-12t + 48\text{mA}]$$

