

Impedance : Z (Ω)


Admittance

$$Y = \frac{1}{Z} = G + jB$$

Imaginary
Resistor

↑
Capacitor

Example

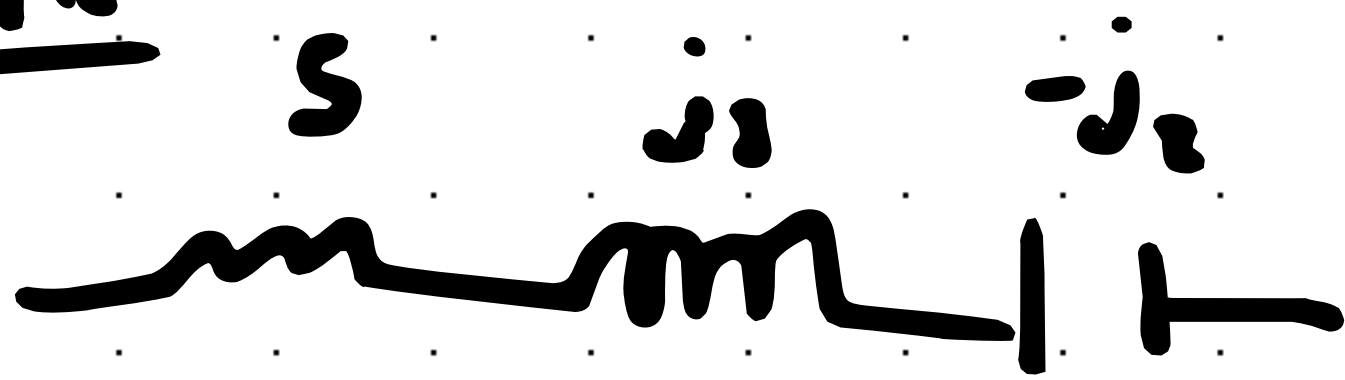


$$\Rightarrow Z = S + j1 - j2 =$$

$$\underline{Z = S + j1 \Omega}$$

Example

Find the total Impedance

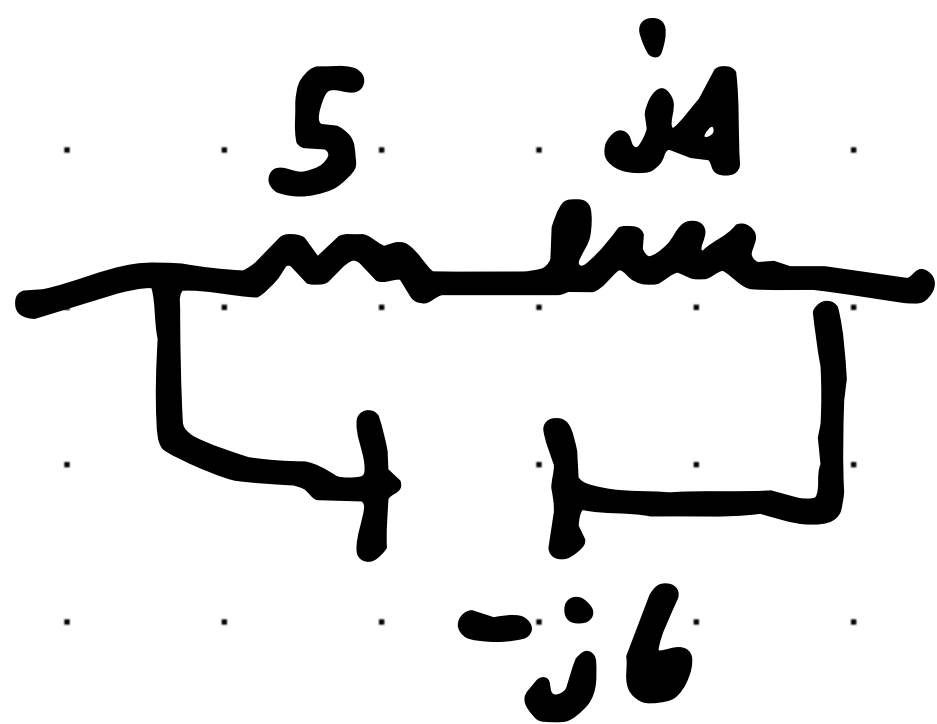

$$Z = \frac{(5+j4)(-j6)}{5+j4-j6} = \frac{-j30 + 24}{5-j2}$$


$$= \frac{24-j30}{5-j2} \left(\frac{5+j2}{5+j2} \right) \quad \leftarrow \begin{array}{l} \text{Complex} \\ \text{conjugate} \end{array}$$

$$= \frac{5(24) + 10j(2) + j2(24) - j30(5)}{5^2 + 2^2}$$

$$= \frac{180}{29} - j \frac{102}{29}$$

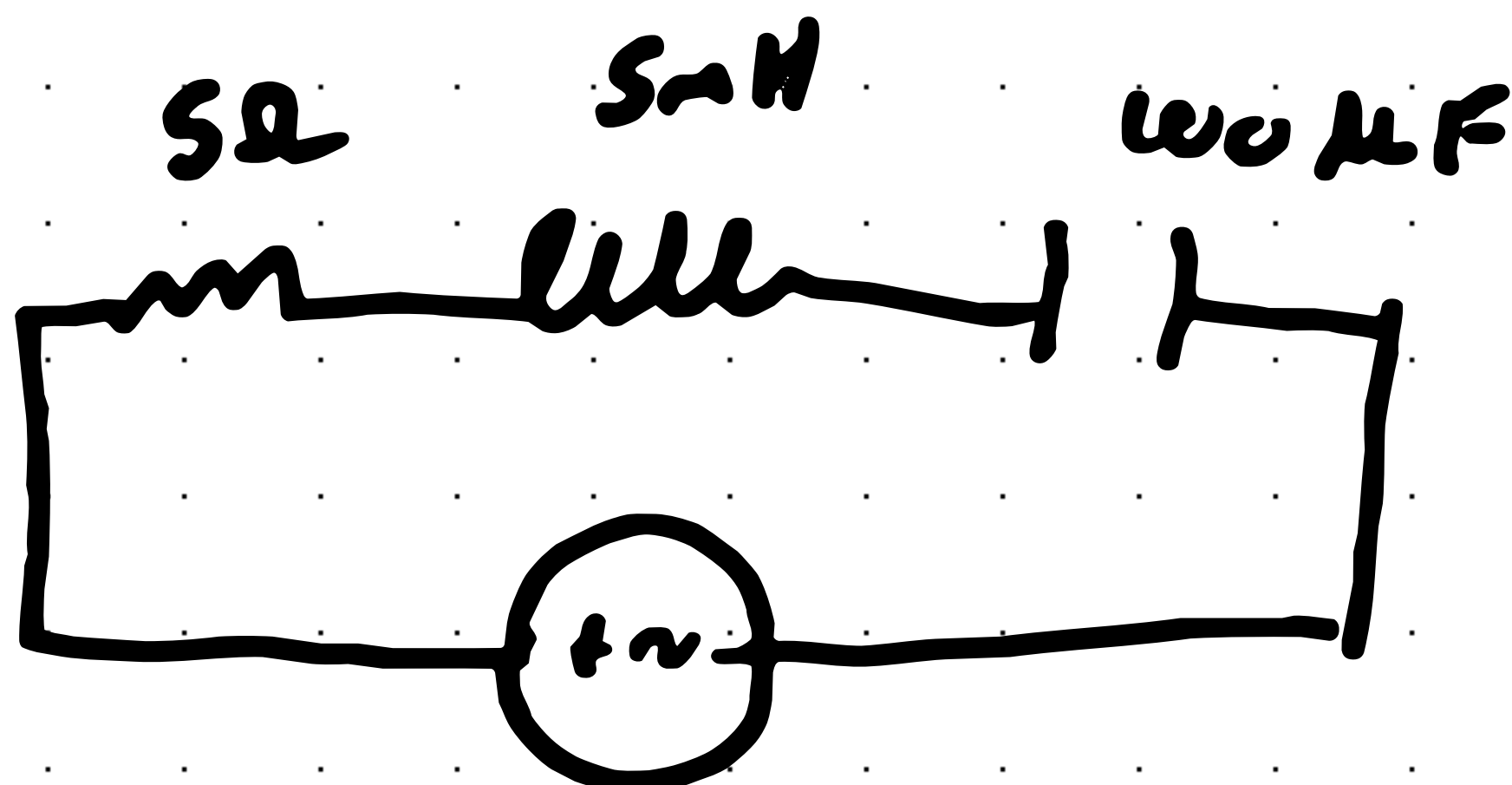Example

Calculate the current i in the following circuit



Solution


$$v = 10 \cos(1000t + 20^\circ)$$

- ① Convert from time domain to phasor domain.


$$L \longrightarrow j\omega L \longrightarrow j(1000)(5 \times 10^{-3}) \longrightarrow j5\Omega$$


$$C \longrightarrow -j\frac{1}{\omega C} \longrightarrow -j\frac{1}{(1000)(100 \times 10^{-6})} \longrightarrow -j10\Omega$$

$$v = 10 \angle 20^\circ$$

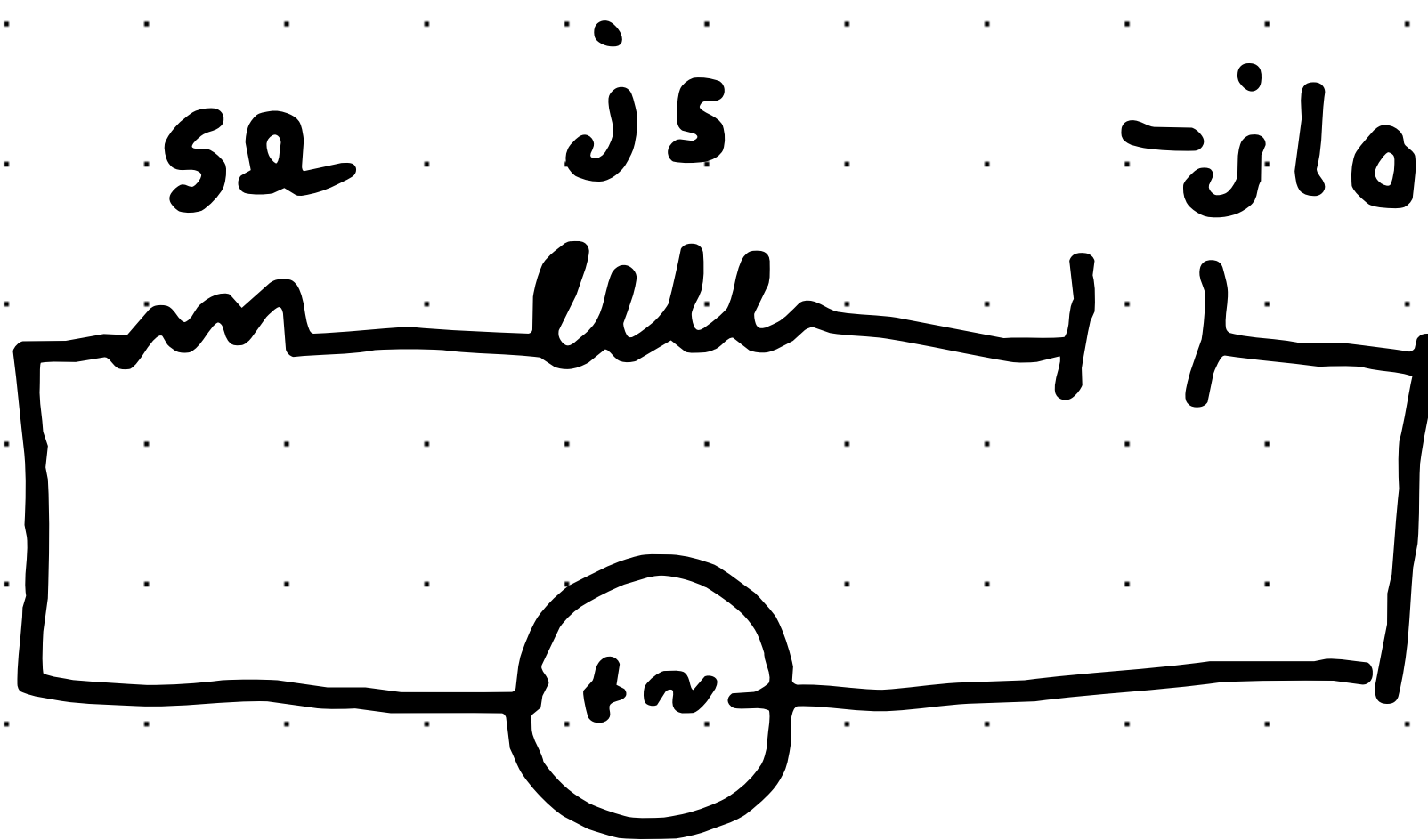

$$10 \angle 20^\circ$$

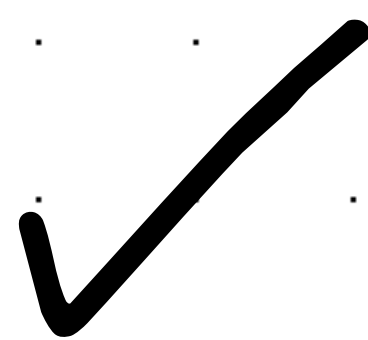

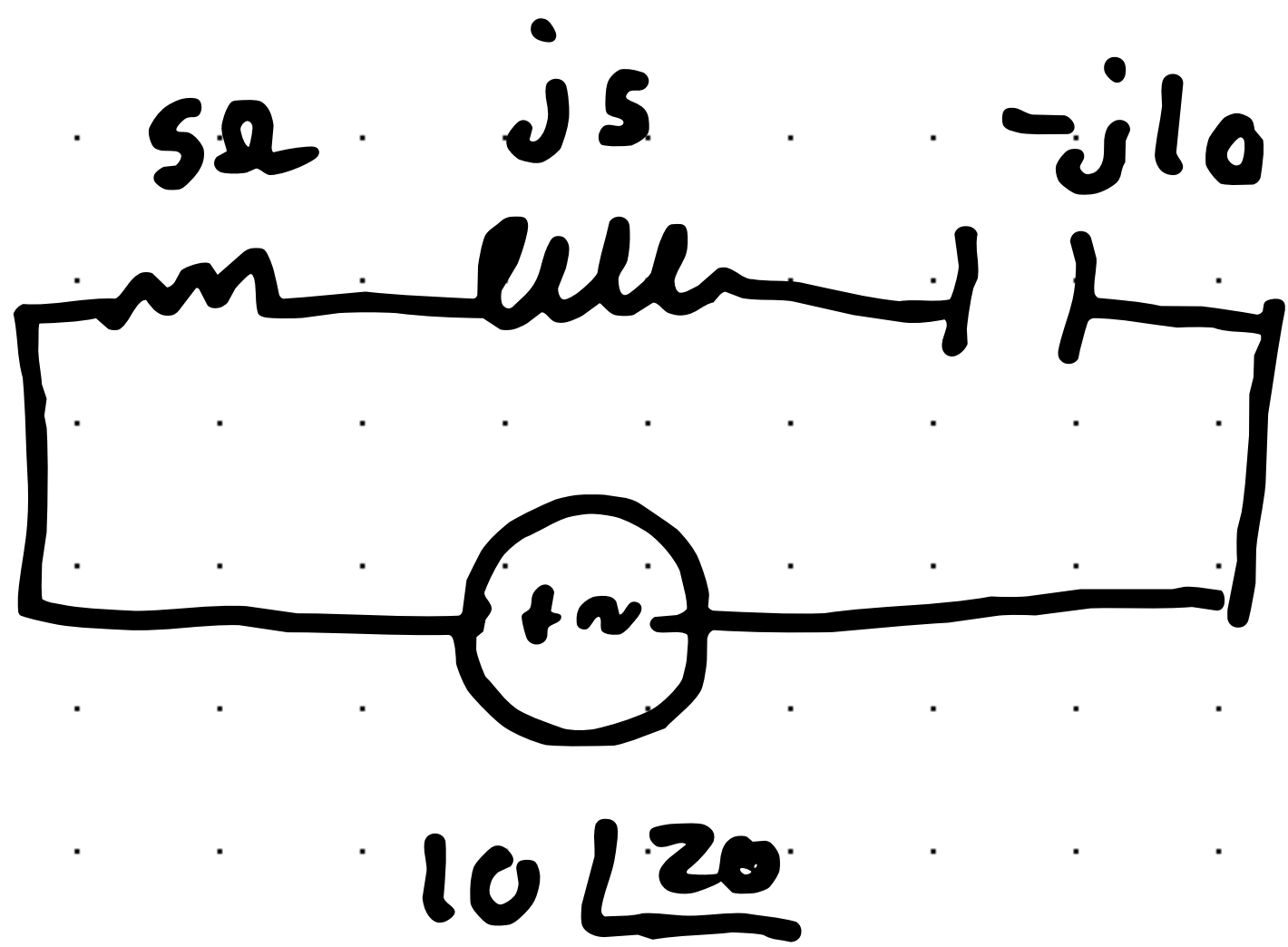

Here, we
look for the
total impedance

$$Z = 5 + j5 - j10$$

$$= \underline{5 - j5}$$

$$i = \frac{V}{Z} = \frac{10 \angle 20^\circ}{5 - j5}$$

① Here, either
do complex
conjugate,

$$= \frac{10 \angle 20^\circ}{\sqrt{5^2 + 5^2} \angle -\tan^{-1}\left(\frac{5}{5}\right)}$$

OR
convert to polar

$$= \frac{10 \angle 20^\circ}{5\sqrt{2} \angle -45^\circ} = \frac{10}{5\sqrt{2}} \angle (20^\circ - (-45^\circ))$$

$$= \underline{\frac{2}{\sqrt{2}} \angle 65^\circ}$$


Answer

* Convert back
to time domain

$$i(t) = \sqrt{2} \cos(1000t + 65^\circ) \text{ A}$$

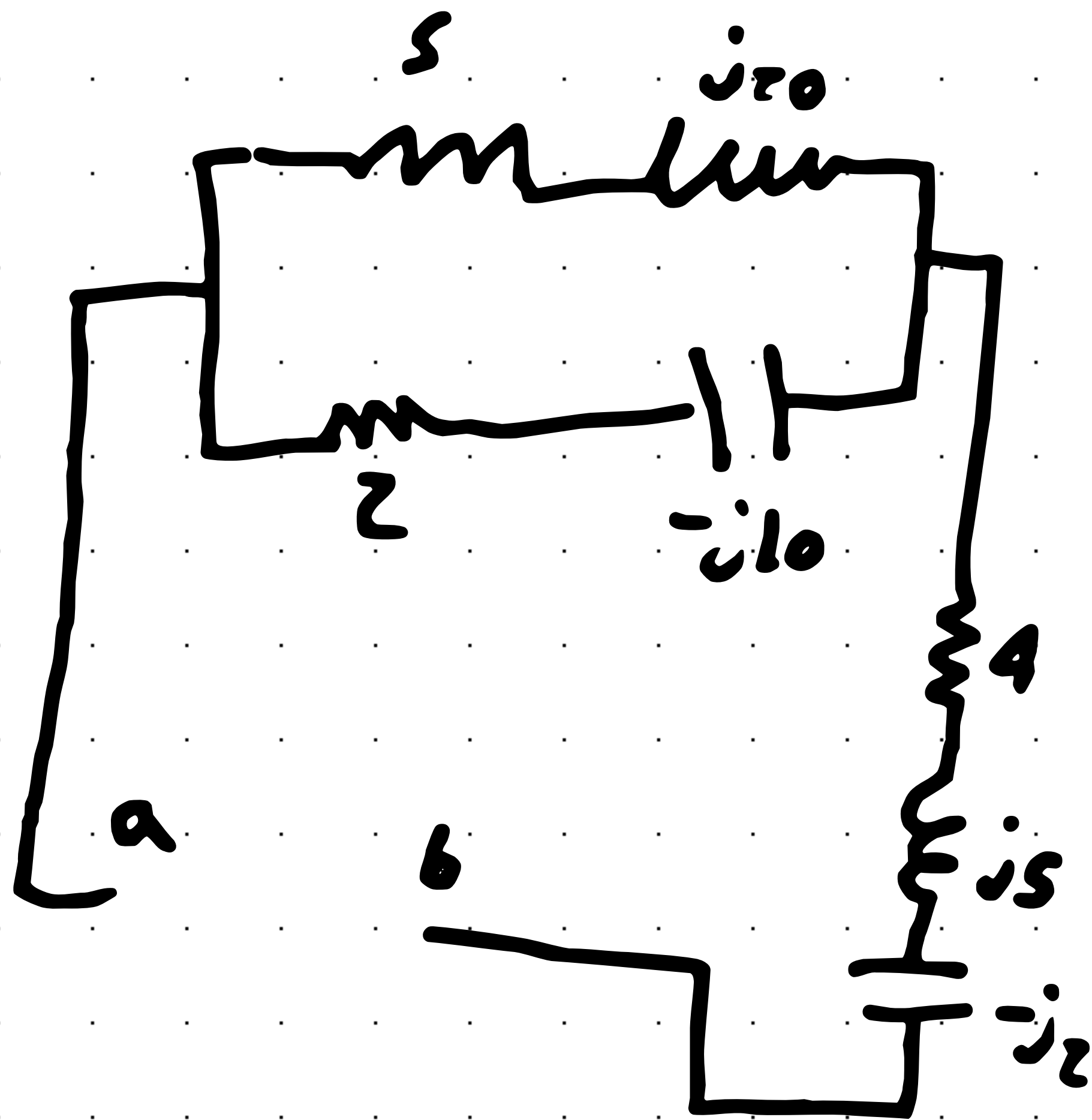Example

Calculate the total impedance between a and b



Solution

$$(5 + j20) // (2 - j10) \quad (\text{Series, run up top})$$

$$= \frac{(5 + j20)(2 - j10)}{5 + j20 + 2 - j10} = \frac{(10 + 200) + j(40 - 100)}{7 + j10}$$

$$= \frac{210 + j10}{7 + j10} = \frac{210 + j10}{7 + j10} \cdot \frac{(7 - j10)}{(7 - j10)}$$

$(j \neq j)$

$$= \frac{7(210) - 100 - j(2100 + 70)}{7^2 + 10^2}$$

Complex conjugate

$$= \frac{1370 - j2170}{149} = 9.19 - j14.56 \Omega$$

$(9.19 - j14.56)$ Series $(4 + j5 - j2)$


$$Z_{\text{total}} = 9.19 - j14.56 + 4 + j5 - j2$$

$$= 13.19 - j11.56 \Omega$$

→ Add Real to
Real, and Imaginary
to Imaginary

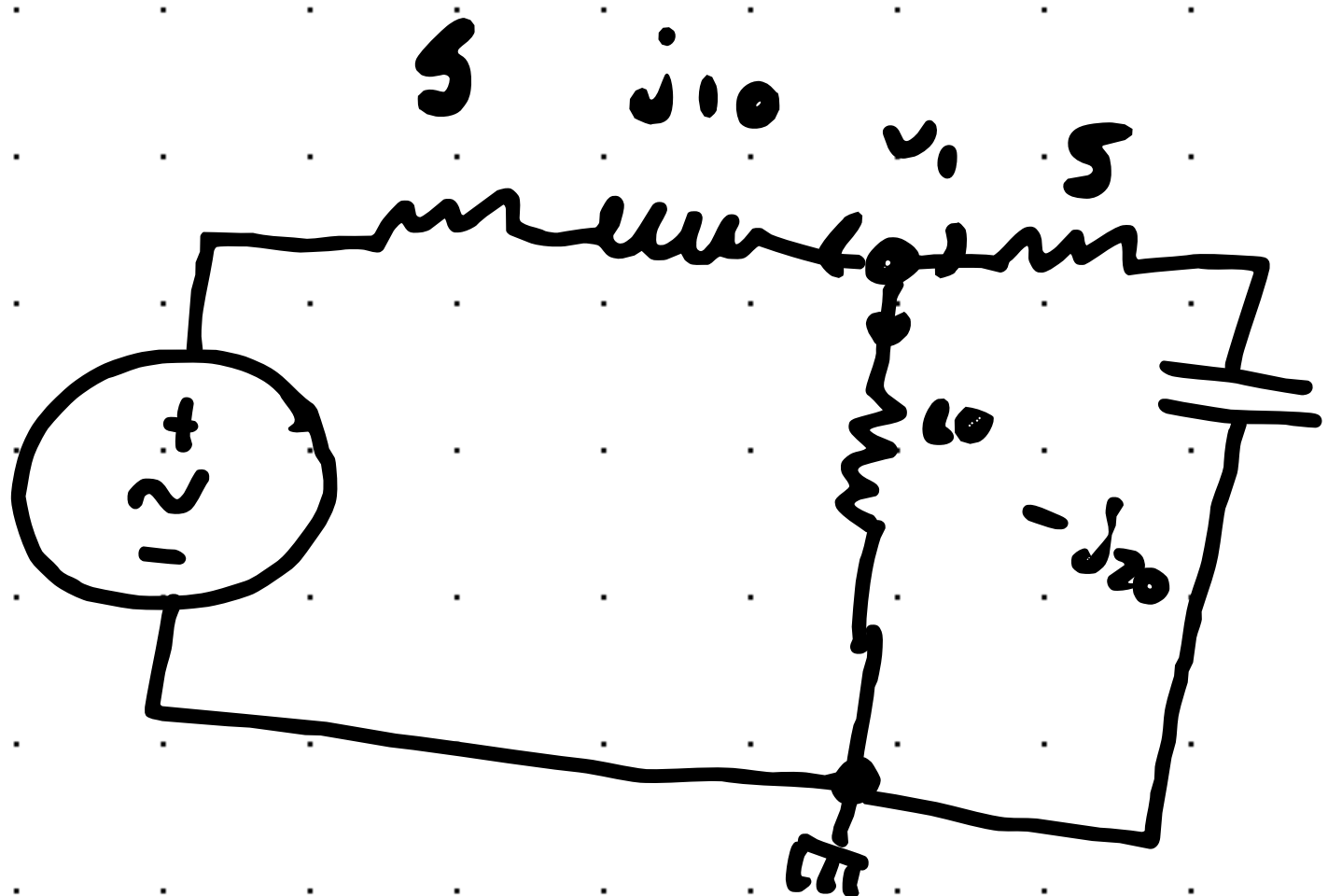Example

Set the two following relations
to calculate V_1



$$\sum I = 0$$

At ①

$$\frac{V_1 - 100 \angle 0^\circ}{5 + j10} + \frac{V_1}{10} + \frac{V_1}{5 - j20} = 0$$

Convert to polar

$$\frac{V_1 - 100 \angle 0^\circ}{\sqrt{5^2 + 10^2} \angle \tan^{-1}(\frac{10}{5})} + \frac{V_1}{10} + \frac{V_1}{\sqrt{5^2 + 20^2} \angle -\tan^{-1}(\frac{20}{5})} = 0$$

$$\frac{V_1 - 100}{11.2 \angle 63.4} + \frac{V_1}{10} + \frac{V_1}{20.6 \angle -76} = 0$$

$$\frac{\angle -63.4}{11.2} + \frac{V_1}{10} + \frac{V_1}{20.6 \angle -76} = 0$$

$$0 = \frac{1 \angle -63.4}{11.2} V_1 - \frac{100}{11.2} \angle -63.4 + \frac{1}{\omega} V_1 + \frac{1 \angle 76}{20.6} V_1$$

$$0.089 \angle -63.4 V_1 - 8.93 \angle -63.4 + 0.1 V_1 + 0.05 \angle 76 V_1$$


$$V_1 (0.089 \angle -63.4 + 0.1 + 0.05 \angle 76) = 8.93 \angle -63.4$$

head back to rectangular form to add...

$$V_1 (0.089 \cos(-63.4) + j0.089 \sin(-63.4) + 0.1 + 0.05 \cos 76 + j0.05 \sin 76)$$

$$= 8.93 \angle -63.4$$

Root Mean Square

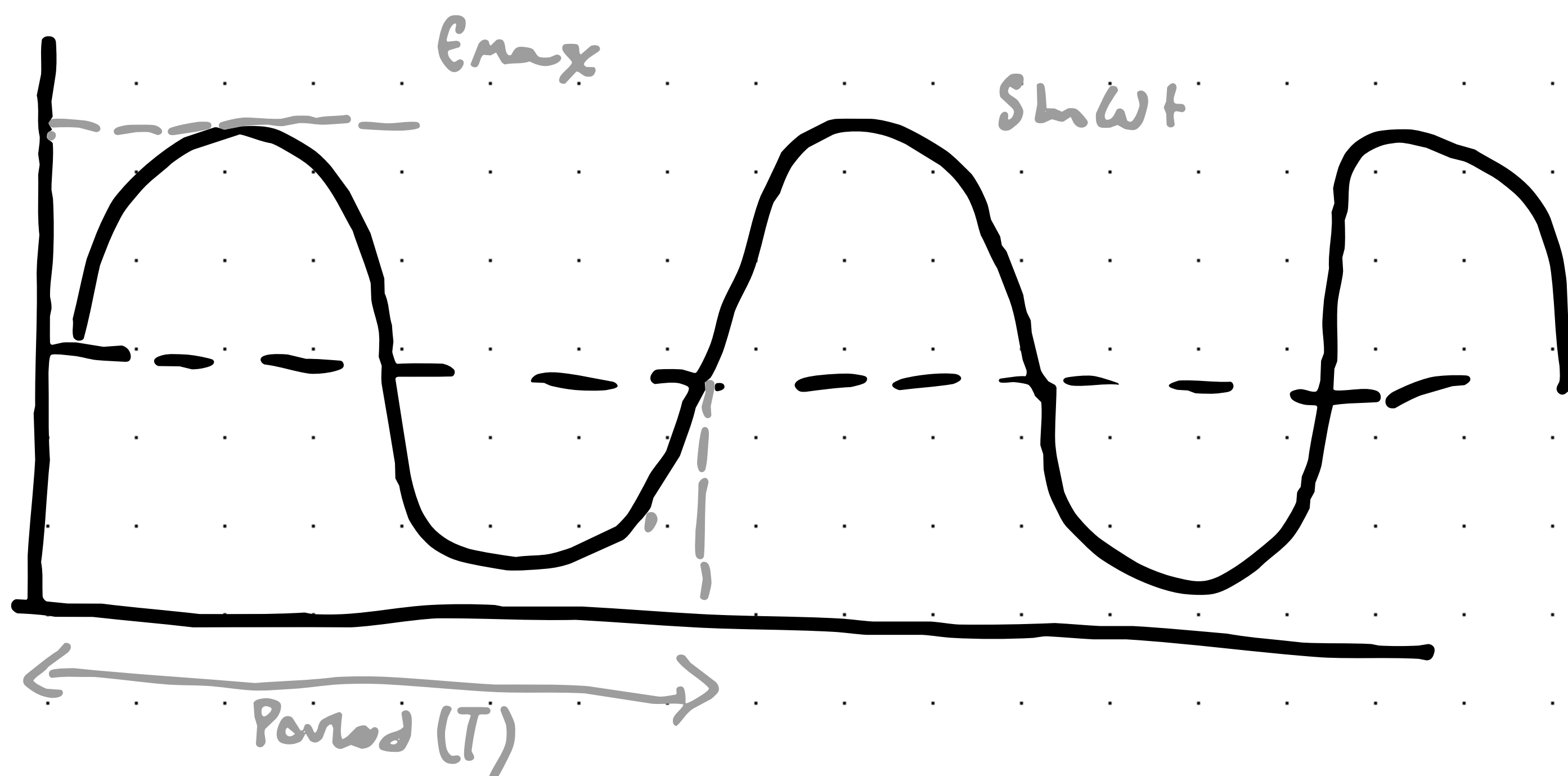

$$\text{Frequency} = \frac{1}{T}$$

$$\text{Root Mean Square} = \sqrt{\frac{1}{T} \int_0^T f^2(t) dt}$$

For Any Sinusoidal Function

$$\begin{aligned} \text{Root Mean Square} &= \frac{\text{The Amplitude (max)}}{\sqrt{2}} \\ &= \frac{f_{\text{max}}}{\sqrt{2}} \end{aligned}$$

R.M.S Examples

Example

$$V_1(t) = 50 \cos(\omega t) \rightarrow V_{1, \text{rms}} = \frac{50}{\sqrt{2}} \text{ V}$$


$$V_2(t) = 100 \cos(\omega t + 20^\circ) \rightarrow V_{2, \text{rms}} = \frac{100}{\sqrt{2}} \text{ V}$$

Complex Apparent Power

Real Power VS. Imaginary Power

Without Imaginary power, we would not be able to use the Real power.

For example, a fan.

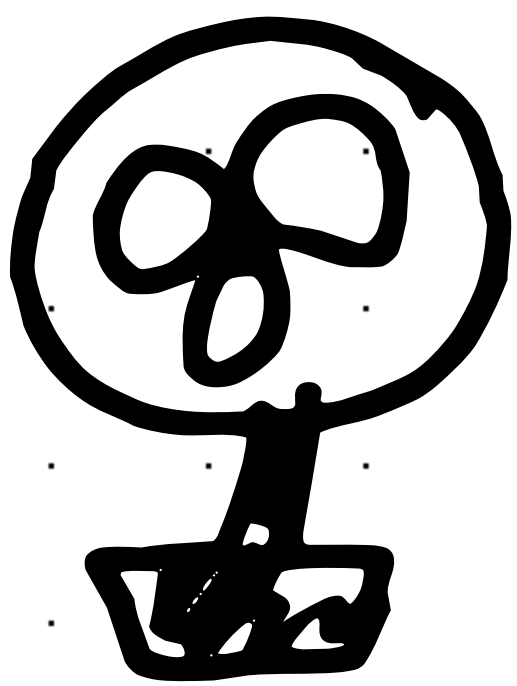

- A fan requires electrical (Real) power to provide current.
- Inside the fan, there is a motor, that contains a magnet.
- The Magnetic force does not spin the fan by itself, it needs current.
- But the opposite is also true. The real electrical power is used, but not possible without the magnet.

$$S = V_{rms} i_{rms} = P + jQ \quad \begin{matrix} (VA) \\ (Volt- \\ Amperes) \end{matrix}$$

Active Power (P)

P

$$P = \sum |i_{rms}|^2 R \quad \text{or} \\ = |i_{rms}| V_{rms} \cos(\phi_v - \phi_i)$$

Watts

Reactive Power
(Q)

$$Q = \sum |i_{rms}|^2 X_L - \sum |i_{rms}|^2 X_C$$

or

$$Q = |V_{rms}| |i_{rms}| \sin(\phi_v - \phi_i)$$

VAR

Volt-Amp-Reactive


$$\text{Power Factor} = \cos(\phi_v - \phi_i)$$

Ex $V(t) = 100 \cos(1000t + 20^\circ)$

$i(t) = 5 \cos(1000t - 40^\circ)$

* Note, both $i(t)$ and $V(t)$ must be the same. Otherwise, add 90° and convert.

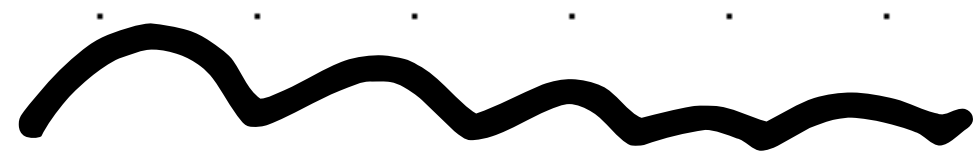Calculate the active power, reactive power, complex power and the impedance



$$V_{rms} = \frac{100}{\sqrt{2}} \angle 20^\circ$$

$$i_{rms} = \frac{5}{\sqrt{2}} \angle -40^\circ$$

Real power

$$\begin{aligned} P &= |V_{rms}| |i_{rms}| \cos(\Phi_v - \Phi_i) = \\ &= \frac{100}{\sqrt{2}} \left(\frac{5}{\sqrt{2}} \right) \cos(20^\circ - (-40^\circ)) = 125 \text{ watts} \end{aligned}$$

Reactive power

$$\begin{aligned} Q &= |V_{rms}| |i_{rms}| \sin(\Phi_v - \Phi_i) = \\ &= 216.5 \text{ VAR} \end{aligned}$$

Complex power

$$S = P + jQ$$

$$= 125 + j216.5$$

Impedance

$$Z = \frac{V}{I} = \frac{\frac{100}{\sqrt{2}} \angle 20^\circ}{\frac{5}{\sqrt{2}} \angle -40^\circ} = 20 \angle 60^\circ$$

$$= 20 \cos 60^\circ + j 20 \sin 60^\circ$$

$$= 10 + j17.32 \Omega$$

