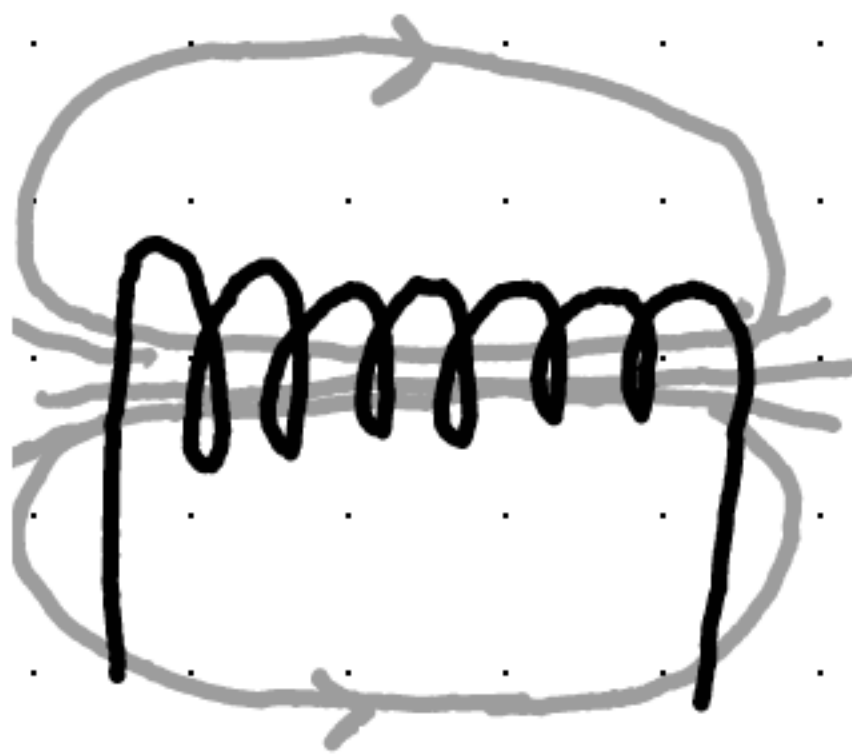


# Circuit Analysis : EEED 2001



The inductance is the property of an electric conductor by which the change in current produces an electromotive force (E.M.F)



When an electric current flows through the inductor's coil, it creates a magnetic field around it

## Faraday's Law:

When the magnetic flux changes with time, EMF (Volts) is induced

$$V = -N \frac{d\Phi}{dt}$$


↑ Number of turns

## Lenz's Law

Direction of an induced current is always such that the magnetic field created by that current opposes the change in the original magnetic field that caused it.

$$V = -L \frac{di}{dt}$$

↑ Self Inductance

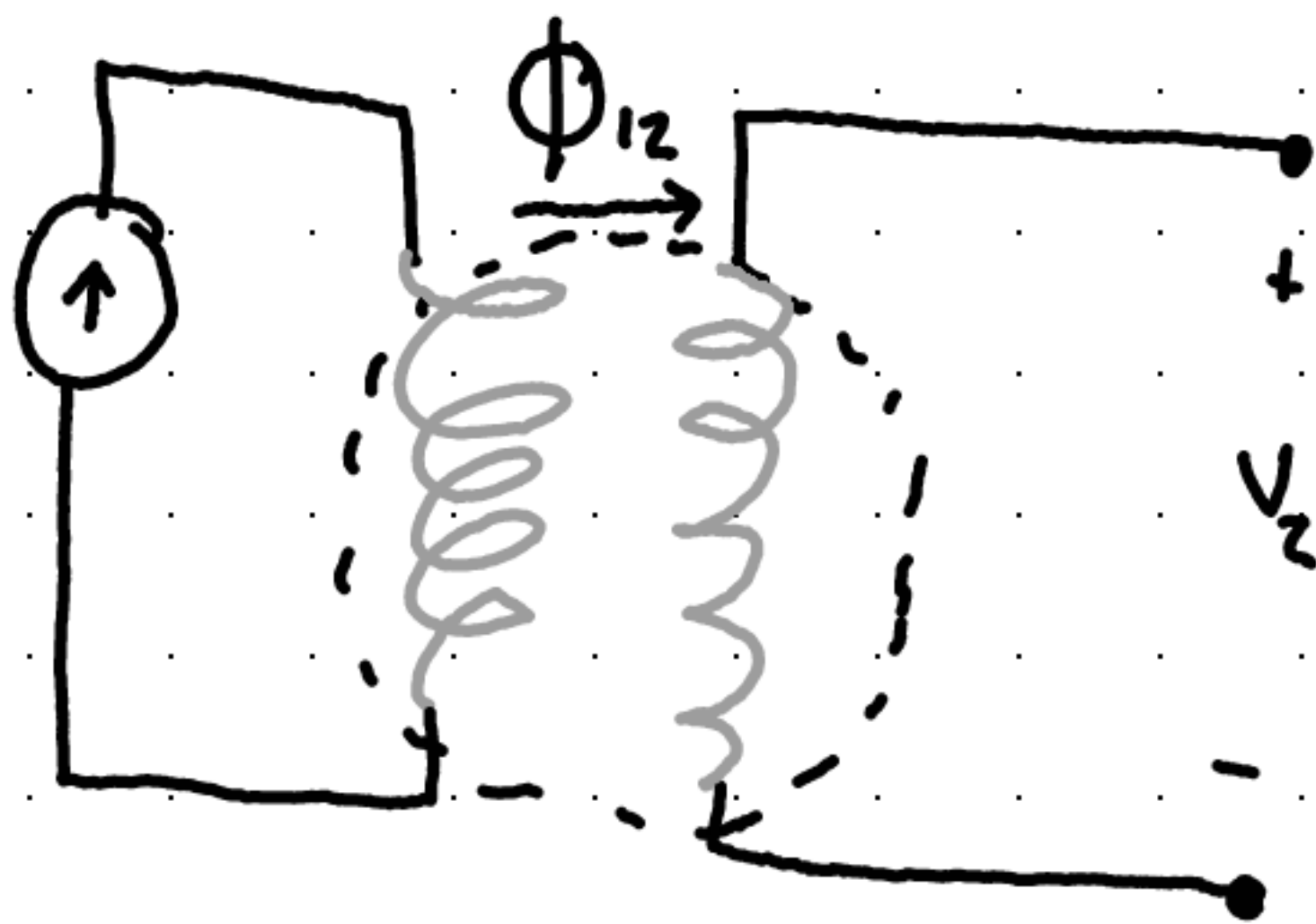

Number of Turns of Coil 2

$$M = \frac{N_2 \Phi_{12}}{i_1} = \frac{N_1 \Phi_{21}}{i_2}$$

Mutual Inductance

### The Coefficient of Coupling

$$K = \frac{\Phi_{12}}{\Phi_1} = \frac{\Phi_{21}}{\Phi_2}$$

$$0 \leq K \leq 1$$

Where:

$\Phi_1$  The total magnetic flux generated by the first coil

$\Phi_{12}$  The portion of  $\Phi_1$  that reaches the second coil

And finally enough!


$$M^2 = \frac{N_1 \Phi_1}{i_1} \times \frac{N_2 \Phi_2}{i_2} \times \frac{\Phi_{21}}{\Phi_2} \times \frac{\Phi_{12}}{\Phi_1}$$

$L_1 \times L_2 \times K \times K$

$$M = \sqrt{L_1 L_2 K^2}$$
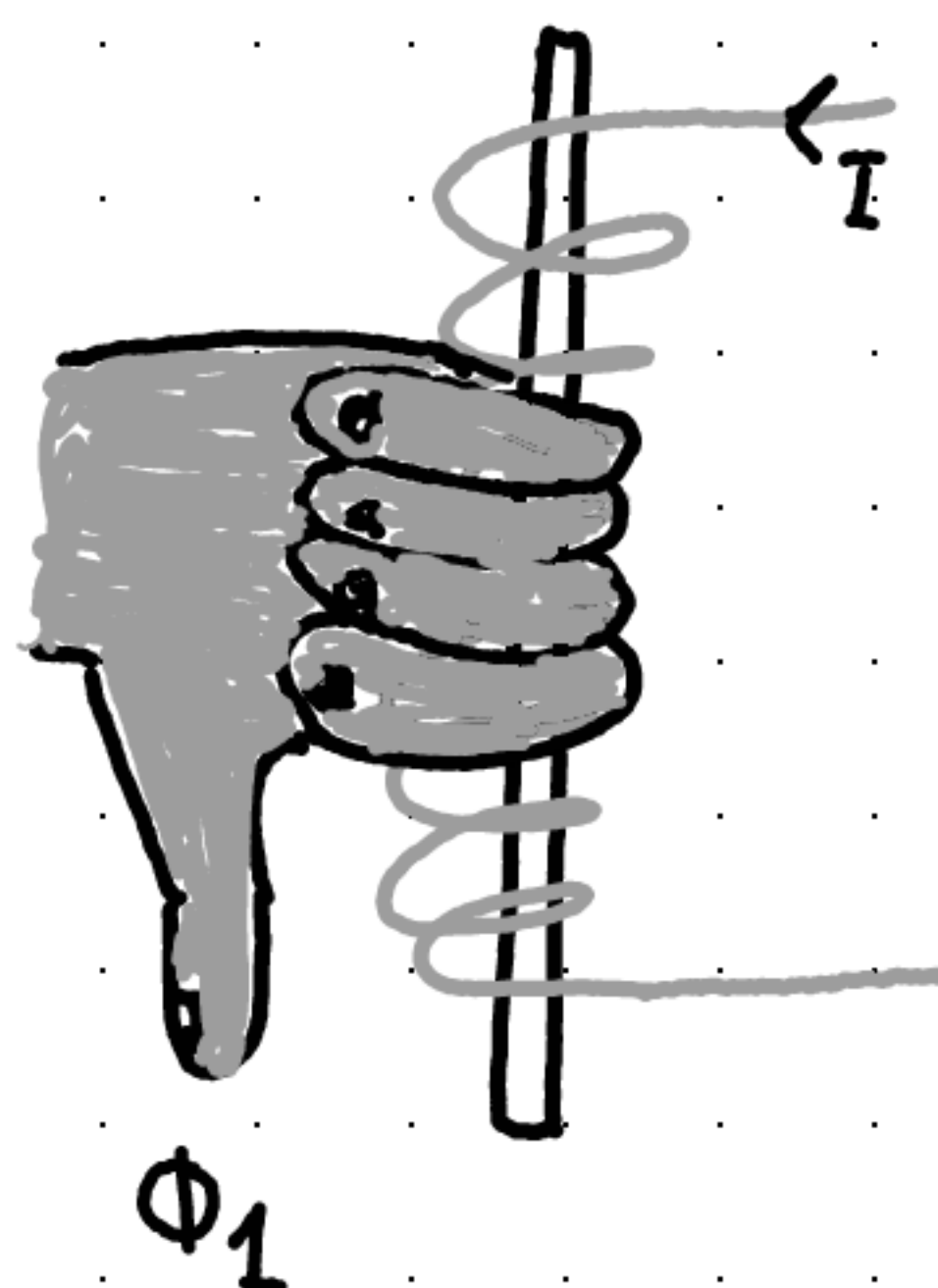
## Right Hand Rule!

- Fluxes flowing in the same direction **Add**
- Fluxes opposing **Subtract**




$$V = \left( \text{Self induced voltage} \right) \pm \left( \text{Mutual induced voltage} \right)$$

$$V_1 = \left( L \frac{di_1}{dt} \right) \pm \left( M \frac{di_2}{dt} \right)$$

The polarity of the voltage induced in the nearby coil depends on the coils winding!

## Dot Convention

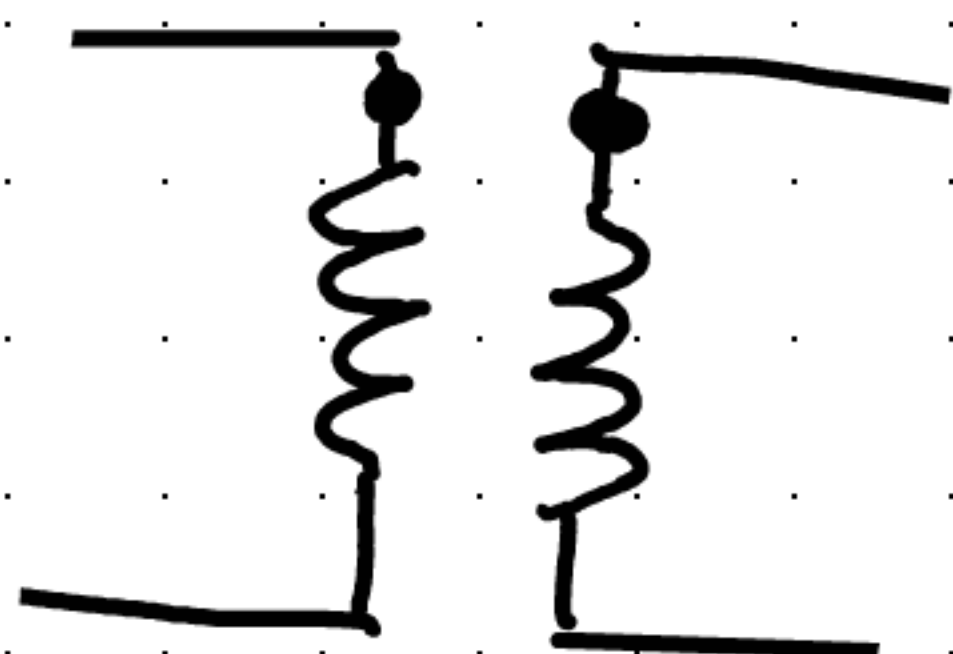

- If both currents enter the dot, you have

$$V = \left( L \frac{di_1}{dt} \right) + \left( M \frac{di_2}{dt} \right)$$

- If each current is doing something different

$$V = \left( L \frac{di_1}{dt} \right) - \left( M \frac{di_2}{dt} \right)$$

## Using Phasors


Time:

$$V_1 = \left( L \frac{di_1}{dt} \right) \pm \left( M \frac{di_2}{dt} \right)$$


Phasor:

$$V_1 = (j\omega L I_1) \pm (j\omega M I_2)$$

## Coupled Coils in Series

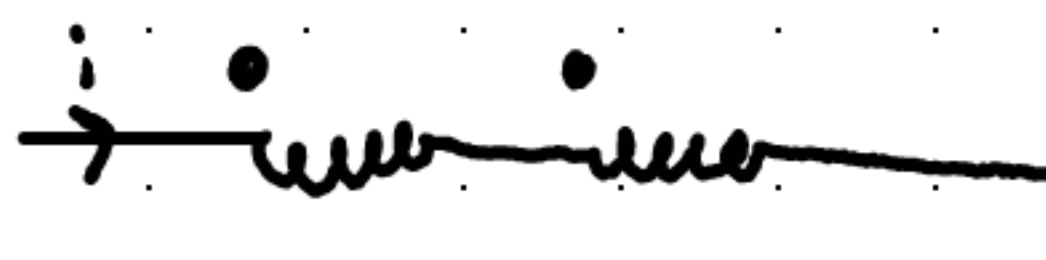 Series Aided Connection

$$L_{eq} = L_1 + L_2 + 2M$$

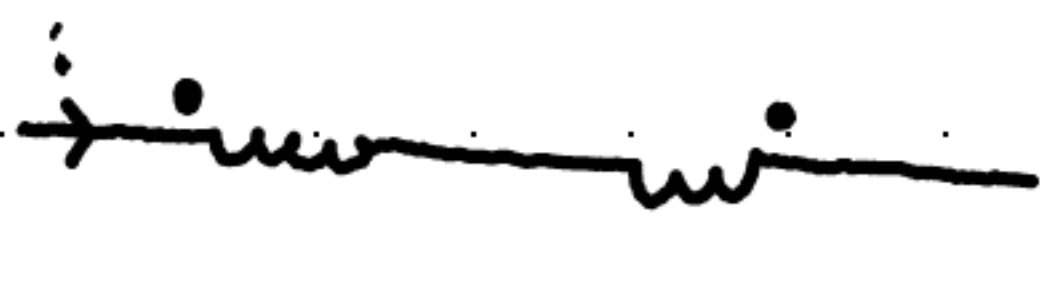 Series opposing Connection

$$L_{eq} = L_1 + L_2 - 2M$$

## Coupled Coils in parallel

 Parallel Aided Connection

$$L_{eq} = \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M}$$

 Parallel opposing Connection

$$L_{eq} = \frac{L_1 L_2 - M^2}{L_1 + L_2 + 2M}$$